
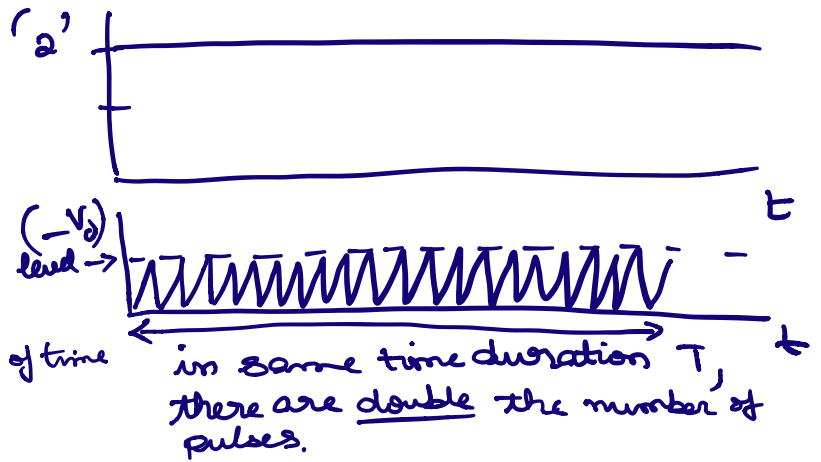
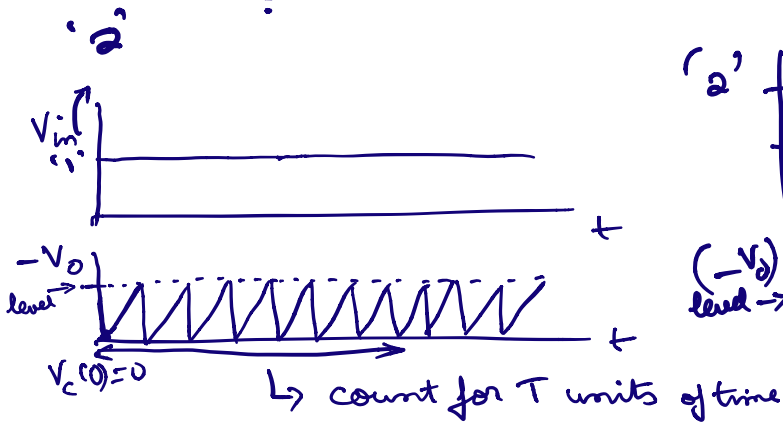


09.01.2019

Integrator-based ADC

_ ELL301

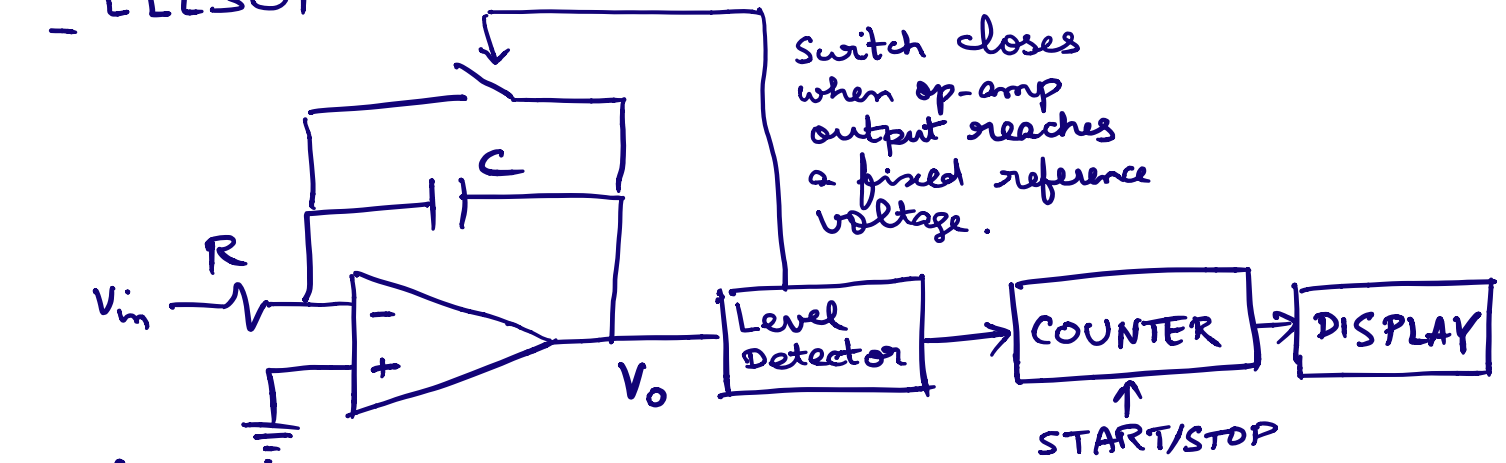


$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{1}{j\omega R C} = -\frac{1}{j\omega} \cdot \frac{1}{RC}$$

$$V_o(t) = \frac{1}{RC} \int V_i(t) dt \quad (\text{when switch S is open})$$


Question: How is this better/worse than the previous method?

Delta-Pulse-Modulation-based ADC


analog voltage to be digitized

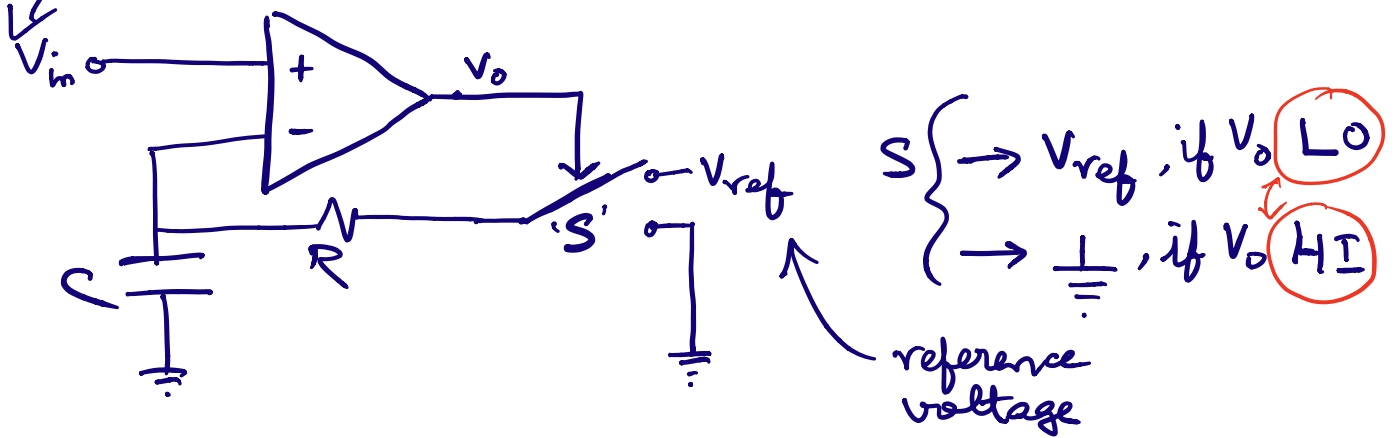

When $S \rightarrow V_{ref}$

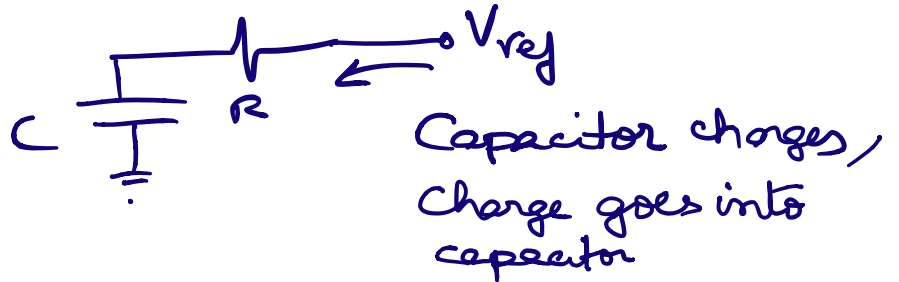


When $S \rightarrow \perp$

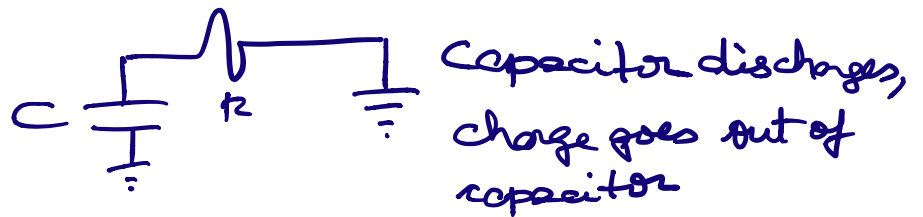

Assumption: V_{ref} should be larger than V_{in} .

Suppose $V_c(t=0) = 0$, and $V_{in} > 0$

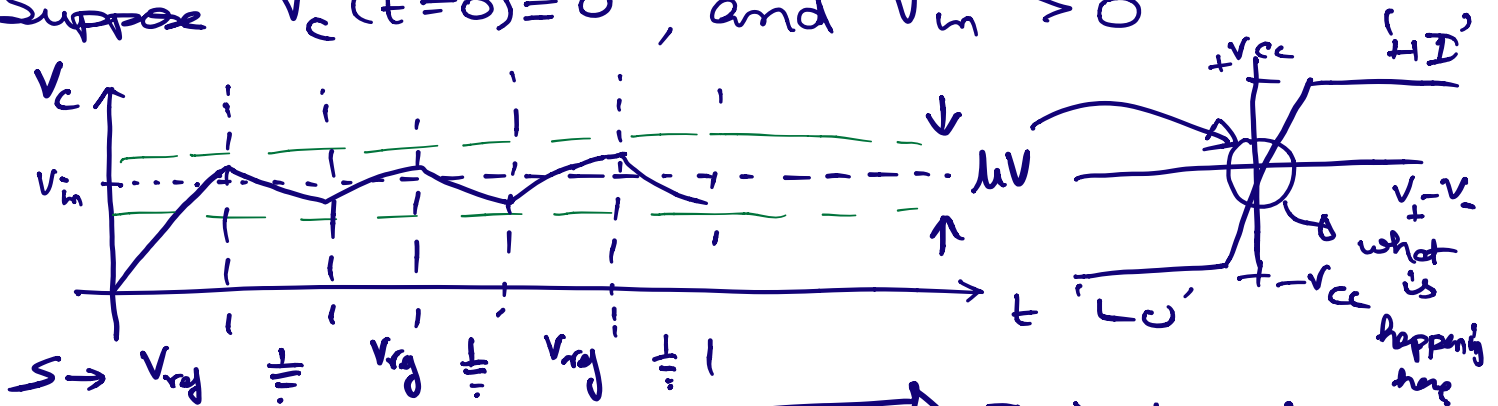

\rightarrow duration of time consider $\} = T$ \leftarrow Z is the time when $S \rightarrow V_{ref}$

charge going into capacitor, Q_{in}
 charge going out of capacitor, Q_{out}