

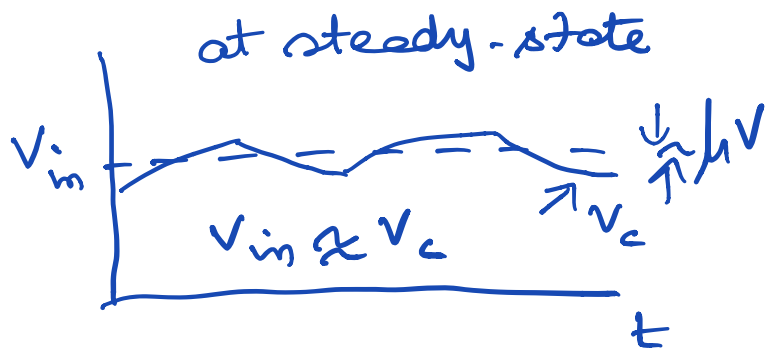
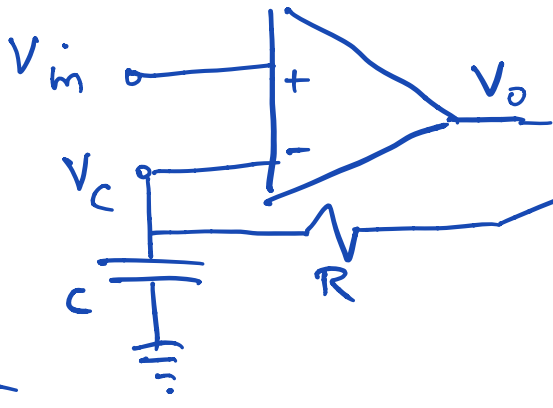
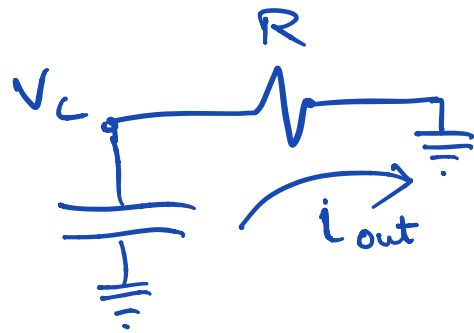


11.01.2019

ELL301

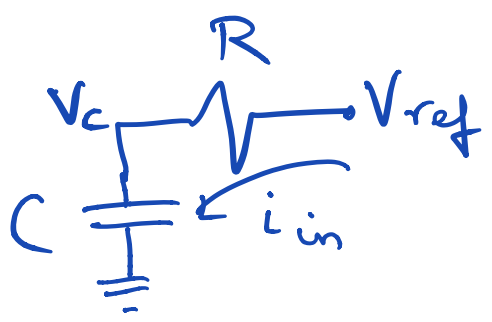

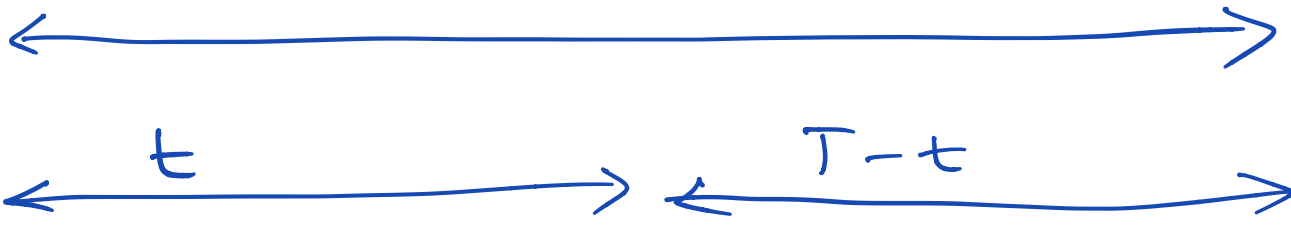$V_{ref}$  if  $V_o$  is HI  
 $\downarrow$   
 $\uparrow$  if  $V_o$  is LO



Claim: Measuring  $\frac{t}{T}$ , we should know  $V_{in}$  relative to  $V_{ref}$   
 Why?

How  $\rightarrow Q_{in} = Q_{out}$ , at steady-state  
 definition  $\checkmark$   $\rightarrow Q$ : charge  
 $\downarrow$  definition

$$i_{in} = \frac{V_{ref} - V_c}{R} \int i_{in} dt = \int \frac{V_{ref} - V_c}{R} dt$$

$$\int i_{out} dt = \int \frac{V_c}{R} dt \quad \left. \begin{array}{l} \text{as } i_{out} = \frac{V_c}{R} \\ \text{Approximation} \end{array} \right\}$$

Approx  $\int \frac{V_{ref} - V_{in}}{R} dt$  based on  $V_{in} \approx V_c$   
 as  $V_{in}$  constant  $\int \frac{V_{in}}{R} dt$  as  $V_{in}$  constant

$$\frac{V_{ref} - V_{in}}{R} t = \frac{V_{in}}{R} (T - t)$$

So,  $\left( \frac{V_{ref} - V_{in}}{R} \right) t = \frac{V_{in}}{R} (T - t)$

$$\Rightarrow \frac{V_{ref} - V_{in}}{V_{in}} = \frac{T - t}{t}$$

$$\Rightarrow \frac{V_{ref}}{V_{in}} - 1 = \frac{T}{t} - 1$$

$$\Rightarrow \frac{V_{in}}{V_{ref}} = \frac{t}{T}$$

2 things left,

① What if we don't make approximation?

② How to use  $\frac{V_{in}}{V_{ref}} = \frac{t}{T}$  to get digital version of  $V_{in}$ ?

Op. amp output

