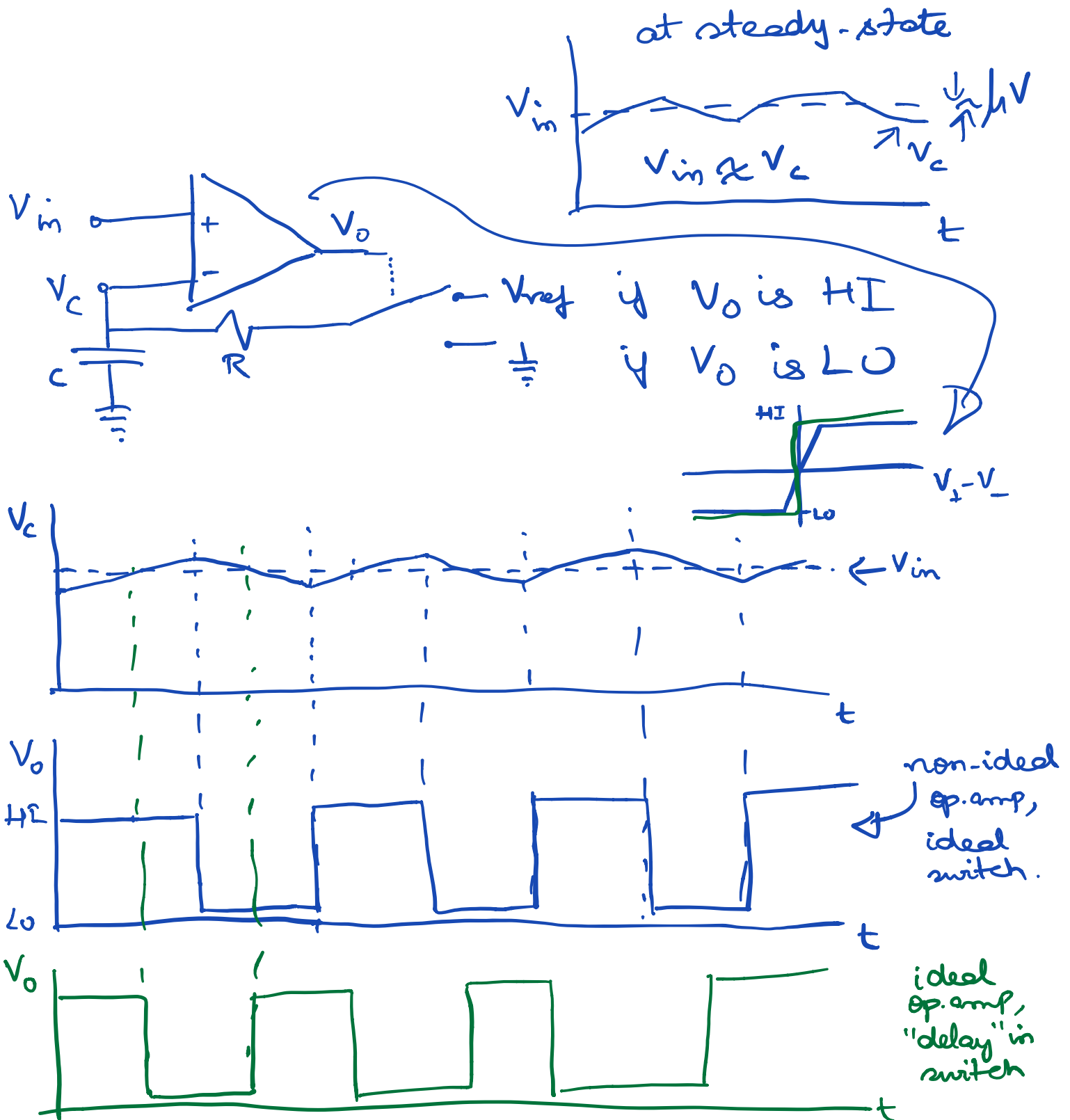


15.01.2019



ELL 301

Timing diagram of Delta-Pulse Modulated ADC (& how to convert analog V_{in} to digital)



From last lecture, $\frac{V_{in}}{V_{ref}} = \frac{t}{T}$, relative duration that the switch is in high state.

How to get t/T ?

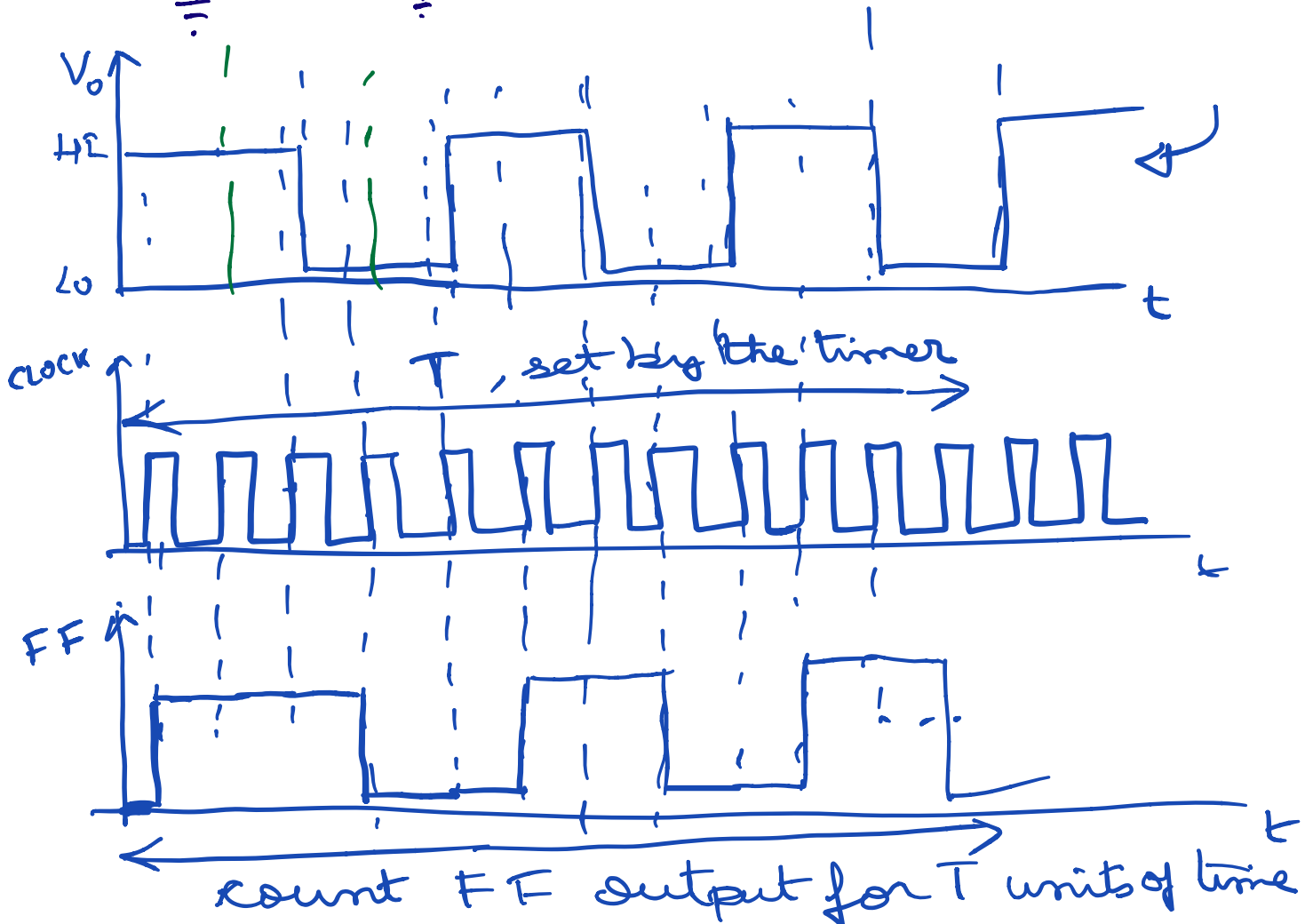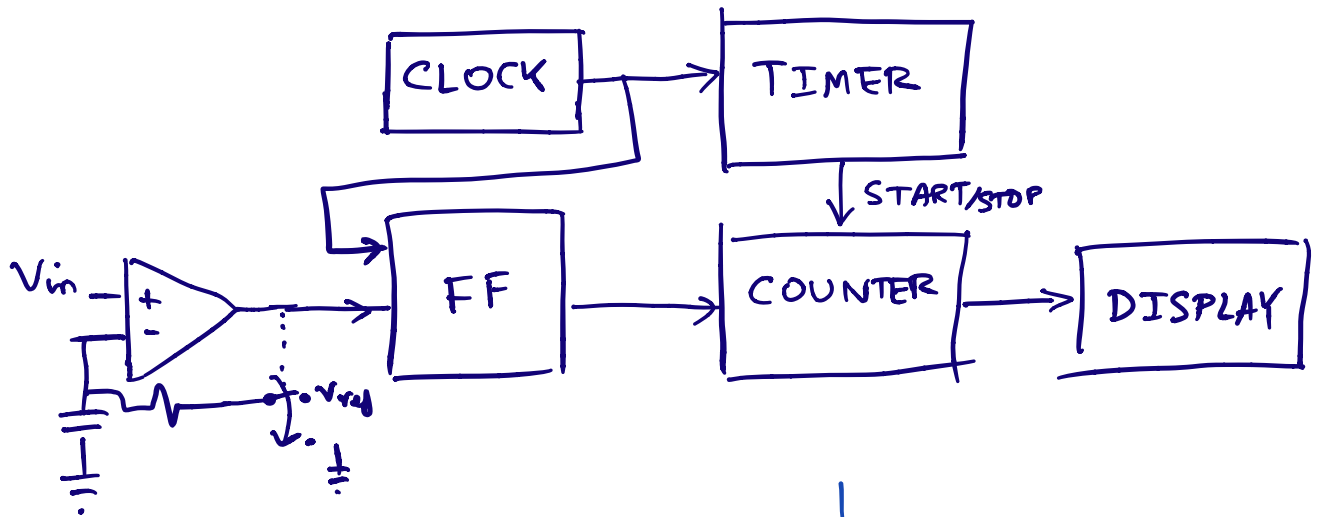


Does this give the ratio $\frac{t}{T}$?

In time T , there are $N = 12$ clock pulses

In time T , how many counts for the counter, $n = 3$
—??

As per above diagram,

alternate diagram

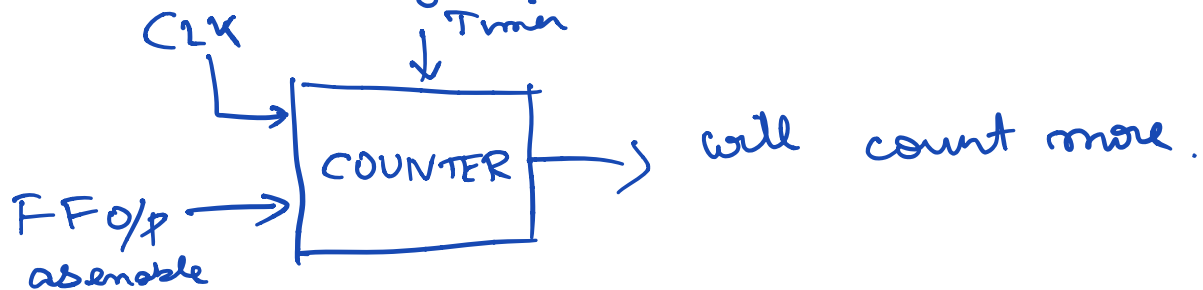

Question: Shouldn't it be counting

the total number of pulses in the

"HI" state to correspond to t ?