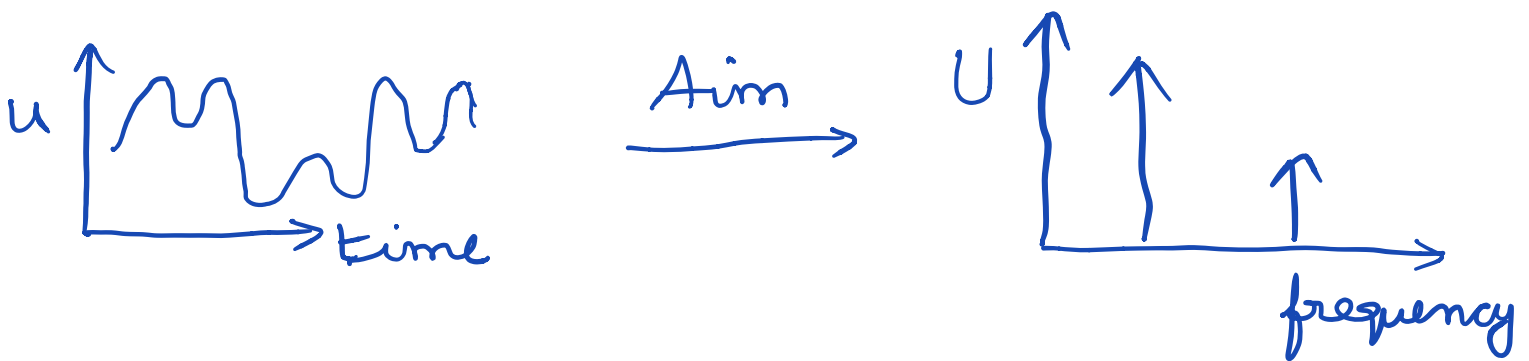


ELL301

22.01.2019


Some basic ideas for the working of a Spectrum Analyzer



Instrument to measure power at different frequencies. (apps also available)

Possible mechanisms?




① Purely digital scheme

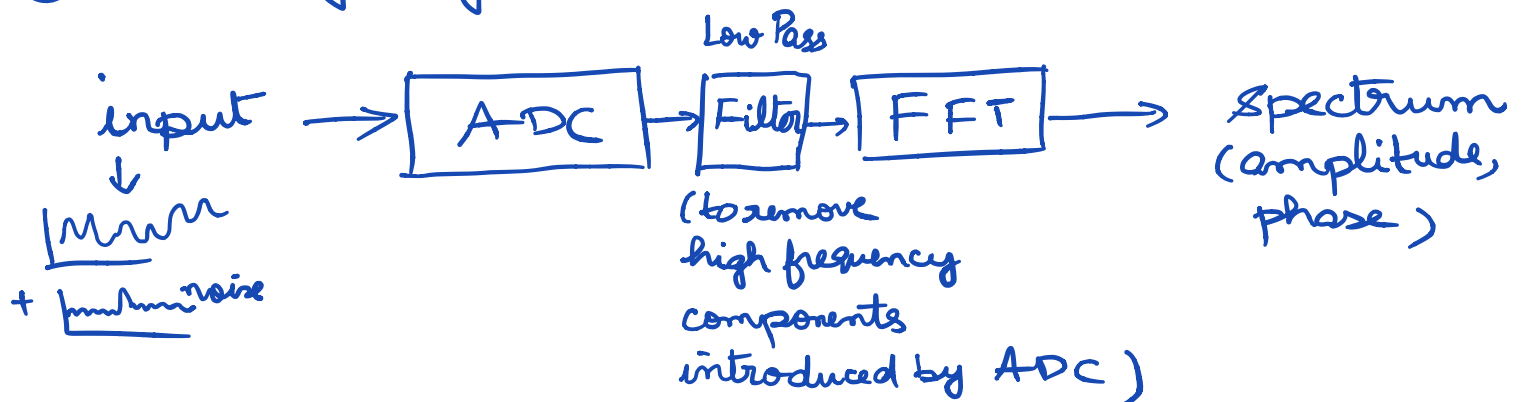



②





?

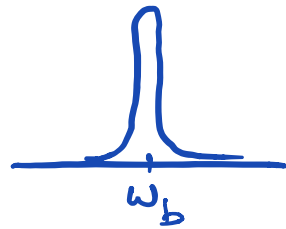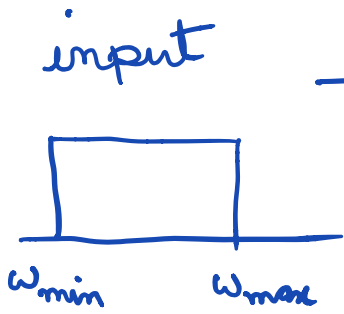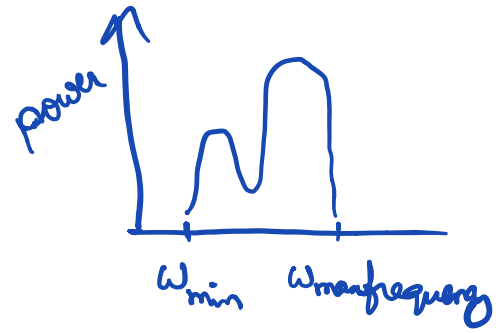


logarithmic amplifier, peak detector

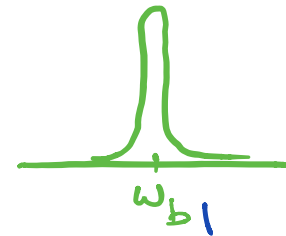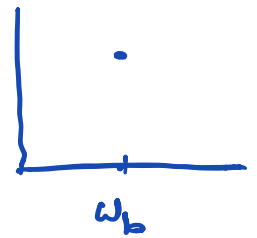


logarithmic amplifier, peak detector

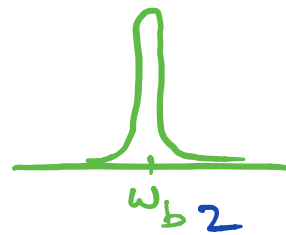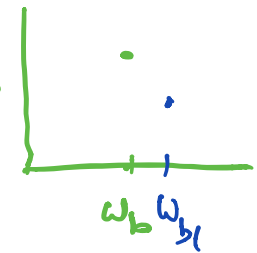


logarithmic amplifier, peak detector

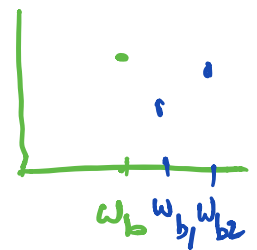

⋮

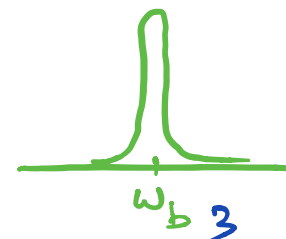

logarithmic amplifier, peak detector

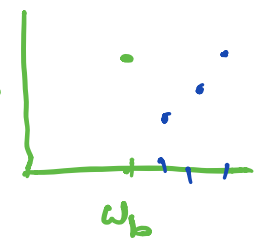


narrow

Many narrow bandpass filters may be used.

How to avoid multiple bandpass filters?
→ variable ω_b bandpass filters?

→ use of 'mixer' to translate input frequencies by different amounts.


(3) Superheterodyne - based

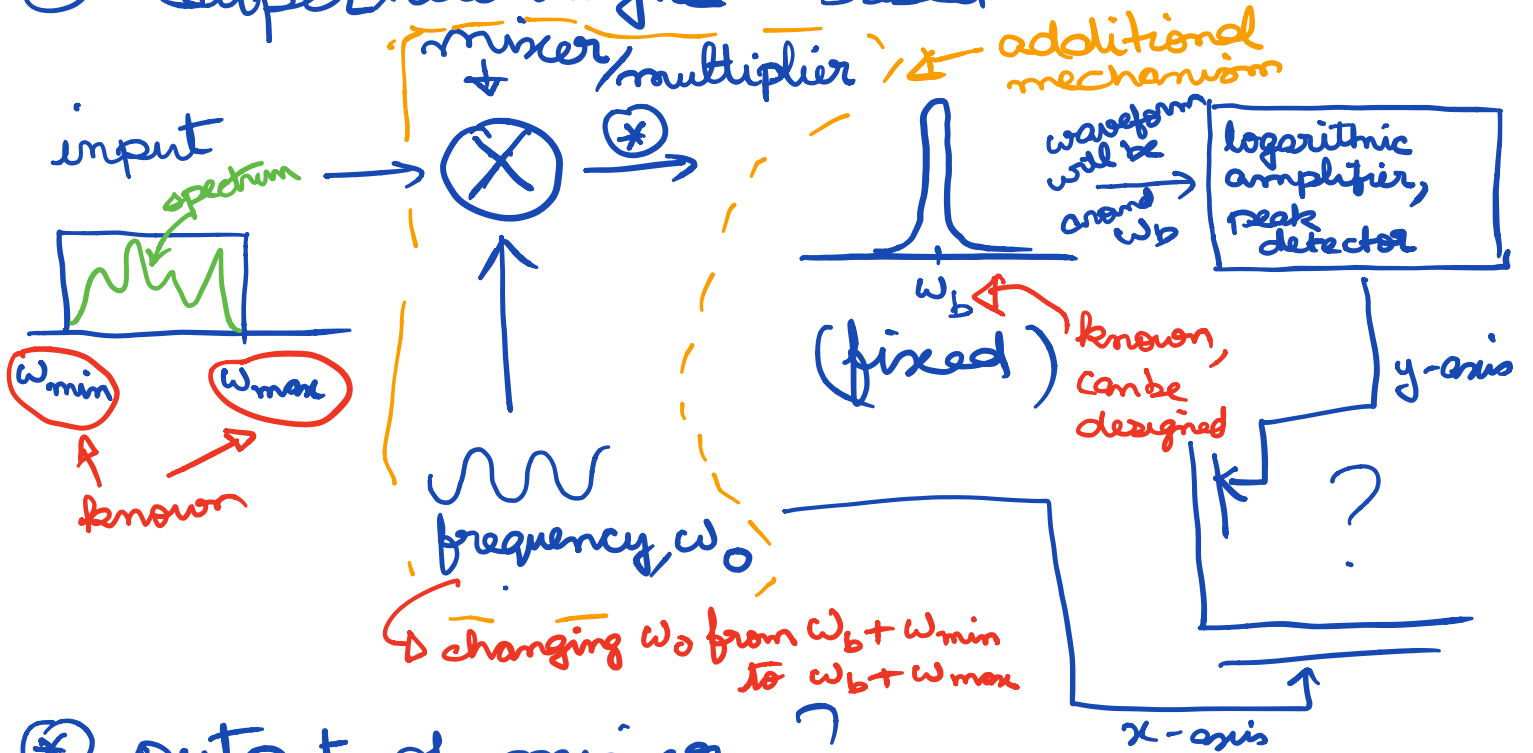

* output of mixer ?


$$\sin \omega t \times \sin \omega_0 t = \cos(\omega - \omega_0)t - \cos(\omega + \omega_0)t$$

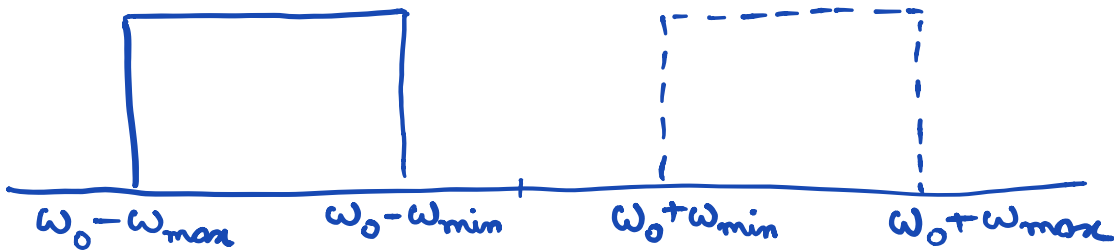$\omega \in [\omega_{min}, \omega_{max}]$



(assuming $\omega_0 > \omega_{max}$)

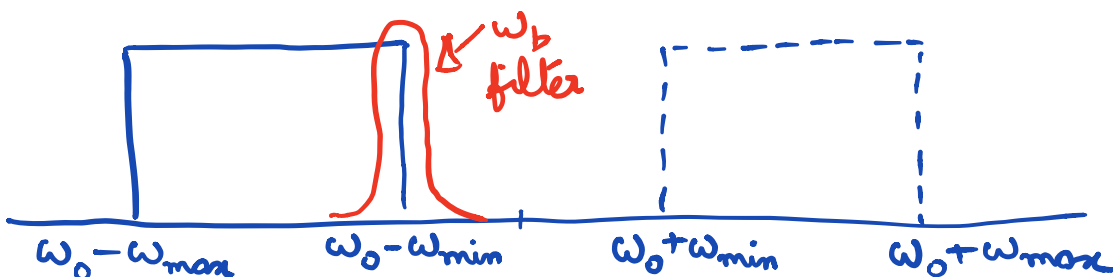
For what value of ω_0 , will following happen



$$\Rightarrow \omega_0 - \omega_{\min} = \omega_b$$

$$\Rightarrow \omega_0 = \omega_b + \omega_{\min}$$

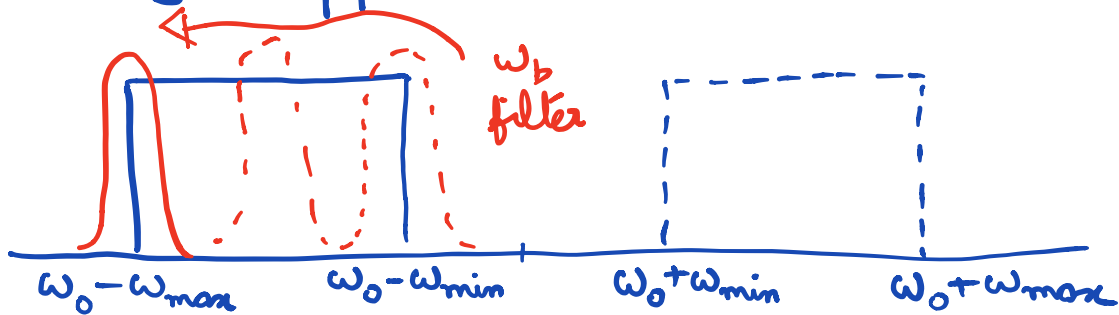As ω_0 increases, there is one value where following happens



this is at $\omega_0 - \omega_{\max} = \omega_b$

$$\omega_0 = \omega_b + \omega_{\max}$$

For spectrum,

Y-axis is from the amplifier / detector

X-axis is from the changing ' ω_0 ' frequency