

ELL301

26.02.2019

## Sensors & Transducers

Ammeter, Voltmeter, Wattmeter, Energy meter are also "sensors" of current, voltage, power, energy, respectively.

Here, we are looking at "sensors" like

- tachometer (velocity  $\rightarrow$  electronic circuit  $\rightarrow$  display)
- temperature (temperature  $\rightarrow$  resistance change  $\rightarrow$  " )
- force, pressure (force, pressure  $\rightarrow$  capacitance change  $\rightarrow$  " )
- humidity / moisture (humidity  $\rightarrow$  ?  $\rightarrow$  " )
- light (light  $\rightarrow$  current  $\rightarrow$  " )
- sound (sound  $\rightarrow$  current  $\rightarrow$  " )
- accelerometers (motion  $\rightarrow$  current  $\rightarrow$  " )
- . . .

We are talking about these sensors here. Why?

Predominantly, these sensing elements are interfaced with electronic circuits for ease of use.

What are the fundamental units?

Mass

Length

Time

K temperature

Cd luminosity


Ampere

mole

sensors / transducers :  
all of these, or their combinations, are converted into a unit containing 'A'.
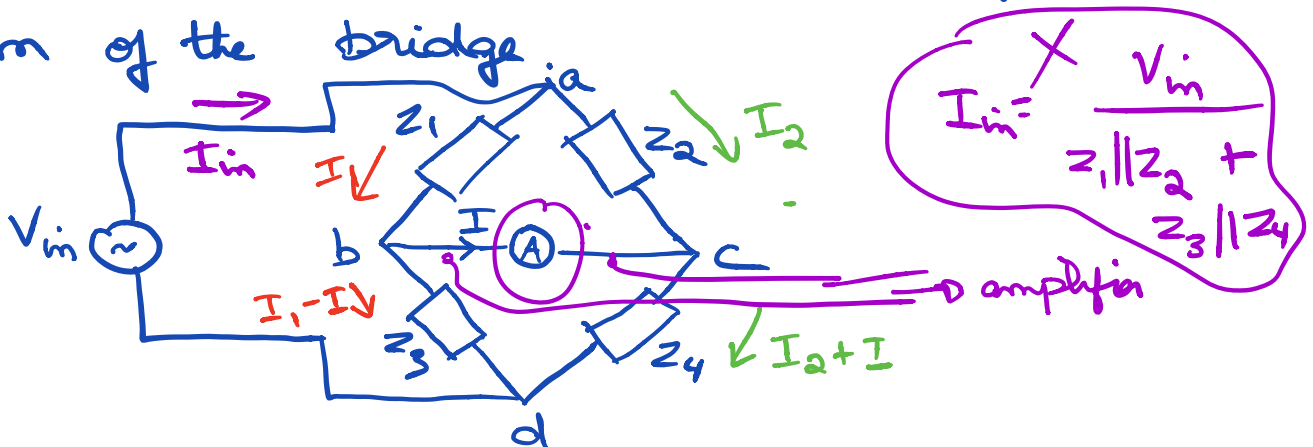
## Wheatstone Bridge

- often used as the first interface between the sensor and other electronic circuitry, i.e. the sensor is one of the arms of the bridge



What is  $I$ ?

What is relation between impedances for  $I=0$ ?

• If  $I=0$ ,  $V_b = V_c$

$$\Rightarrow \frac{z_3}{z_1+z_3} \cdot V_{in} = \frac{z_4}{z_2+z_4} V_{in} \quad (\text{voltage dividers})$$

$$\Rightarrow z_3(z_2+z_4) = z_4(z_1+z_3)$$

$$\Rightarrow z_2 z_3 = z_1 z_4$$

→ In general,  $I = V_{in} \left[ \frac{z_2 z_3 - z_1 z_4}{(z_1 z_2 (z_3 + z_4) + z_3 z_4 (z_1 + z_2))} \right]$  ??

Using this expression we want to find how  $I$  changes when  $z_1 \rightarrow z_1 + \Delta z_1$

$$-V_{in} + I_1 z_1 + (I_1 - I) z_3 = 0$$

$$-V_{in} + I_2 z_2 + (I_2 + I) z_4 = 0$$

$$\Rightarrow I_1 (z_1 + z_3) = V_{in} + I z_3$$

$$I_2 (z_2 + z_4) = V_{in} - I z_4$$

$$\Rightarrow I_1 = \frac{V_{in}}{z_1 + z_3} + I \frac{z_3}{z_1 + z_3}$$

$$I_2 = \frac{V_{in}}{z_2 + z_4} - I \frac{z_4}{z_2 + z_4}$$

$$\Rightarrow I_1 - I_2$$