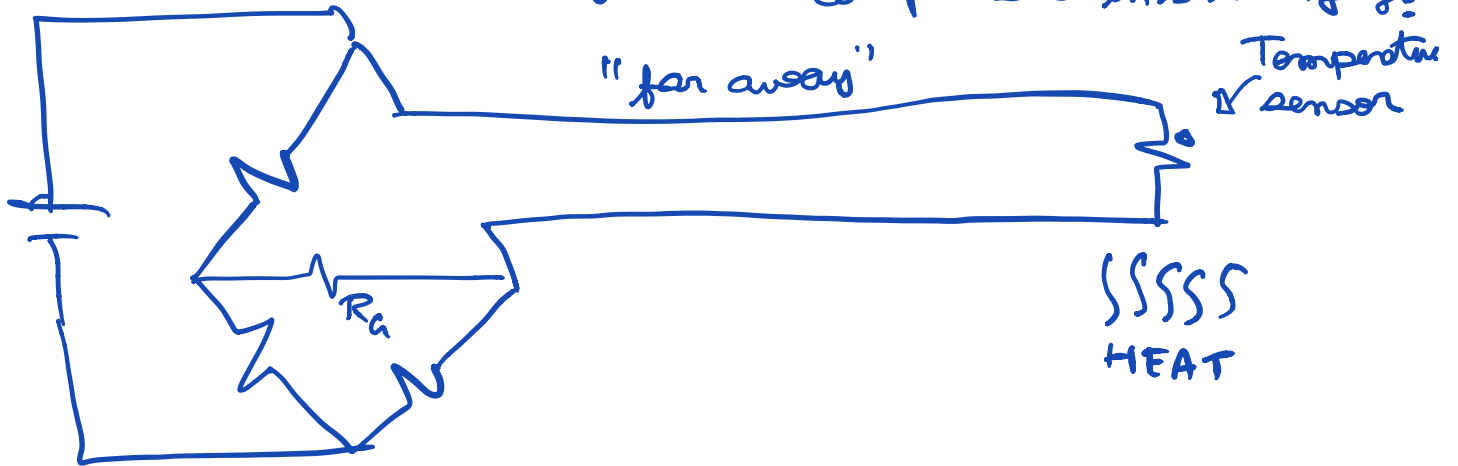



ELL301

22.03.2019

Long leads may introduce errors. How to compensate for their effect? (Just like temperature compensation in strain gauges)




One solution: Three-wire solution

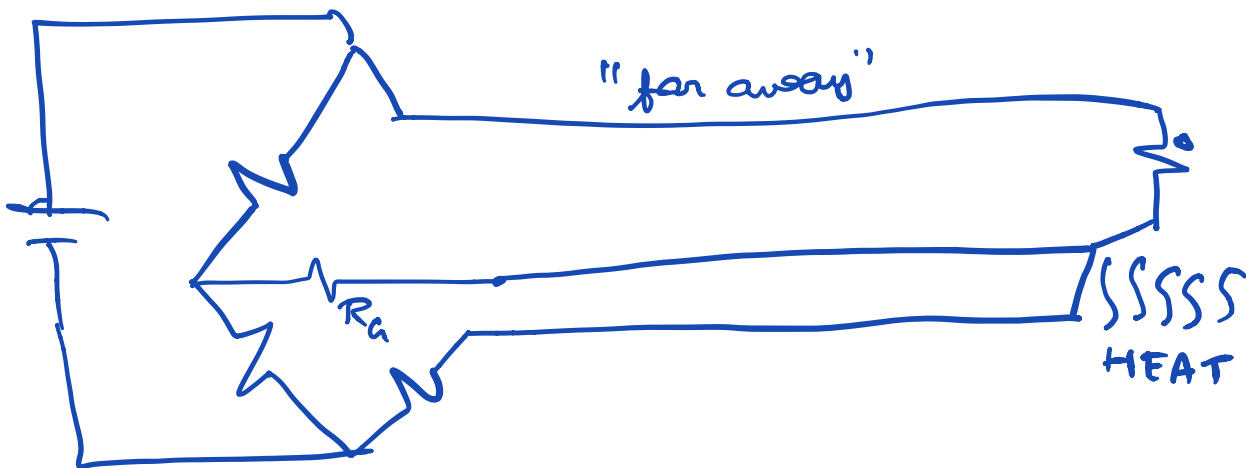


↑ Last time

Four-wire solution

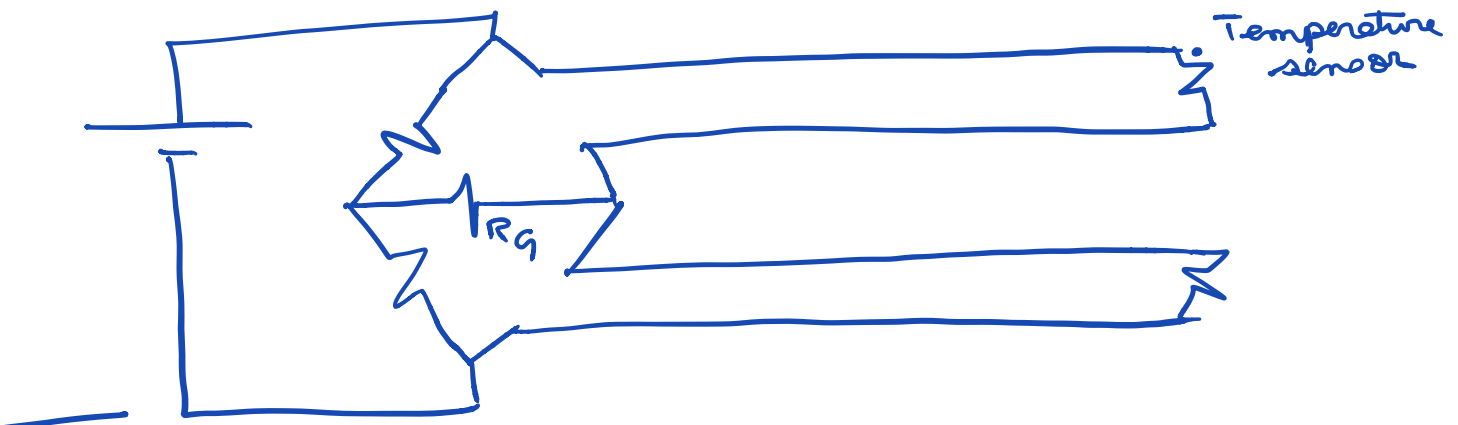


RTDs and Thermistors are examples of Thermo-resistive effect i.e resistances change with temperature

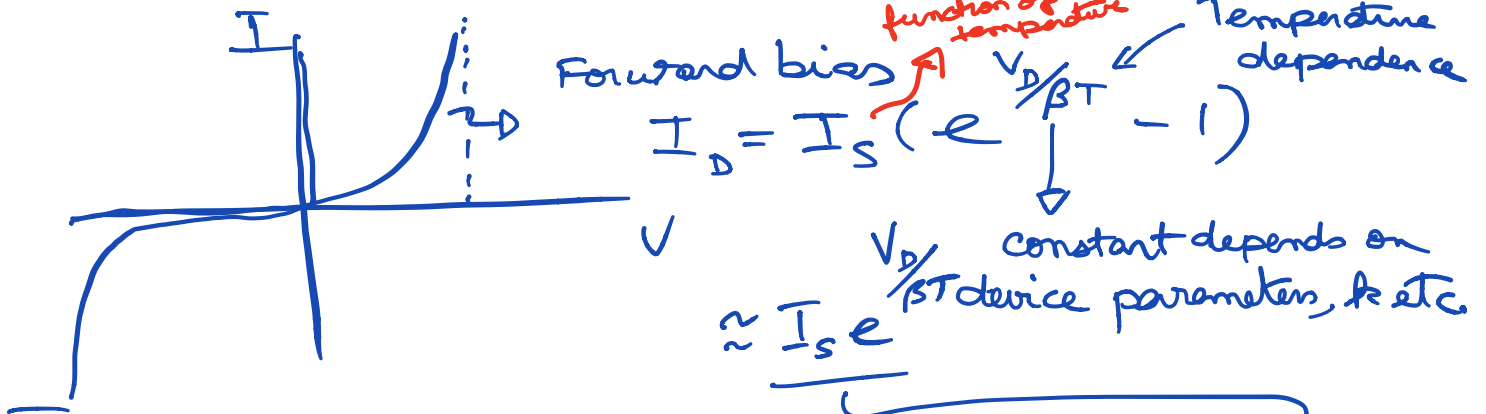— Operation of Diodes, transistors depends on temperature



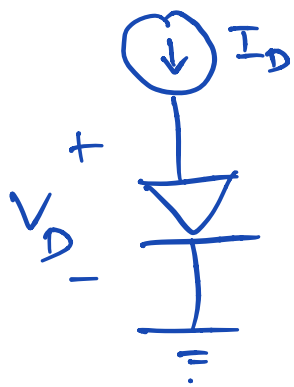How to use this in a temperature sensing application?




Diode is in forward bias, driven by a current source. If we can measure  $V_D$ , and  $I_D$  is set, then we can get  $T$ ?

$$T = \frac{V_D}{\beta} \left( \ln \frac{I_D}{I_S} \right)^{-1}$$

This gives an estimate of  $T$ , but  $I_S$  can also depend on temperature.

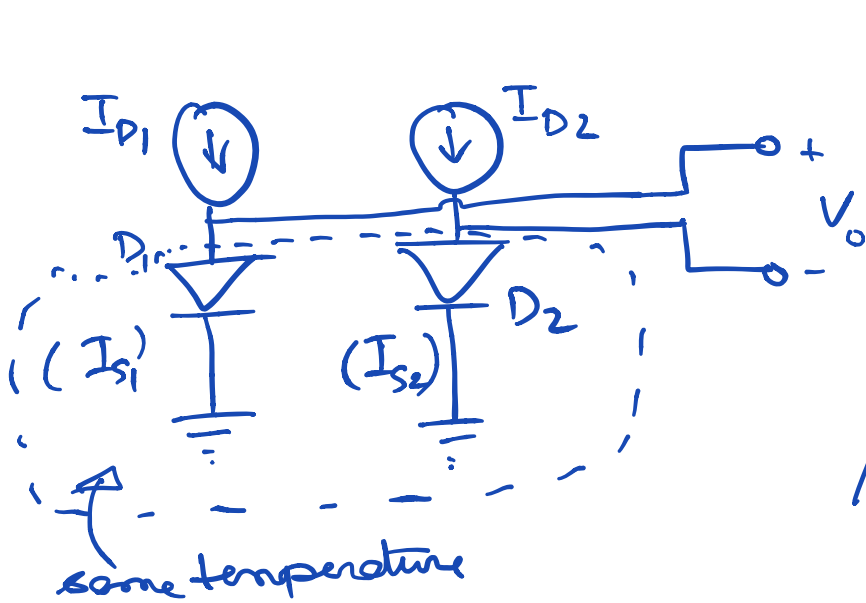One solution: to use a "difference", just like in previous sensors.



$$I_{D1} = I_{S1} e^{V_{D1}/\beta T}$$

$$\Rightarrow \ln \frac{I_{D1}}{I_{S1}} = \frac{V_{D1}}{\beta T}$$

$$\text{or } V_{D1} = \beta T \cdot \ln \frac{I_{D1}}{I_{S1}}$$

$$\text{//ly } V_{D2} = \beta T \cdot \ln \frac{I_{D2}}{I_{S2}}$$

$$\Rightarrow V_0 = V_{D1} - V_{D2}$$

$$= \beta T \cdot \ln \left( \frac{I_{D1}}{I_{D2}} \cdot \frac{I_{S2}}{I_{S1}} \right)$$

$$\Rightarrow T = \frac{V_0}{\beta} \cdot \left( \ln \left( \frac{I_{D1}}{I_{D2}} \cdot \frac{I_{S2}}{I_{S1}} \right) \right)^{-1}$$

We desire this term to be as close to each other as possible by "matching" the diode characteristics.

$$\text{Ideally, } \frac{I_{S2}}{I_{S1}} = 1$$

## PTAT

Proportional To Absolute Temperature

See: A Paul Brokaw, "How to make a Bandgap Voltage Reference in one easy lesson"