

3.2
a)

$$i = I_0 [e^{-V/V_T} - 1]$$

(1)

$$V_T = 0.026 \text{ V.}$$

Taylor series expansion of
 e^{-x} around ($x=0$) is

$$e^{-x} = 1 - x + \frac{x^2}{2} - \frac{x^3}{6} + \text{higher order terms.}$$

$$e^{-x} = 1 - x + \frac{x^2}{2} - \frac{x^3}{6} + \text{higher order terms.}$$

\therefore for small ($x = V/V_T$)

$$e^{-V/V_T} \approx 1 - \left(\frac{V}{V_T}\right) + \frac{\left(\frac{V}{V_T}\right)^2}{2} - \frac{\left(\frac{V}{V_T}\right)^3}{6}$$

$$\therefore i \approx I_0 \left[\left(-\frac{V}{V_T}\right) + \frac{\left(\frac{V}{V_T}\right)^2}{2} - \frac{\left(\frac{V}{V_T}\right)^3}{6} \right] \quad \rightarrow (1)$$

b) $V = A (\cos \omega_f t + \cos \omega_m t) \text{ vols.}$

$$A = 0.01 \text{ Volts.} \quad \rightarrow (2)$$

$$\begin{aligned} \therefore \left(\frac{V}{V_T}\right)^2 &= \left(\frac{A}{V_T}\right)^2 \left\{ \cos^2 \omega_f t + \cos^2 \omega_m t \right. \\ &\quad \left. + 2 \cos \omega_f t \cos \omega_m t \right\} \\ &= \left(\frac{A}{V_T}\right)^2 \left\{ 1 + \cos 2\omega_f t + \cos 2\omega_m t \right. \\ &\quad \left. + \cos (\omega_f + \omega_m)t + \cos (\omega_f - \omega_m)t \right\} \end{aligned} \quad \rightarrow (3)$$

$$\begin{aligned}
 \left(\frac{V}{V_f}\right)^3 &= \left(\frac{A}{V_f}\right)^3 \left\{ \cos 2\omega_0 t + \cos \omega_0 t \right\}^3 \quad (2) \\
 &= \left(\frac{A}{V_f}\right)^3 \left\{ \cos^3 2\omega_0 t + \cos^3 \omega_0 t \right. \\
 &\quad \left. + 3 \cos^2 2\omega_0 t \cos \omega_0 t + 3 \cos 2\omega_0 t \cos^2 \omega_0 t \right\}
 \end{aligned}$$

using the identities,

$$\cos^2 \theta = \frac{\cos 2\theta + \cos 2\theta}{4},$$

we get:

$$\begin{aligned}
 \left(\frac{V}{V_f}\right)^3 &= \left(\frac{A}{V_f}\right)^3 \left\{ \frac{3}{4} \cos 2\omega_0 t + \frac{3}{4} \cos \omega_0 t \right. \\
 &\quad \left. + \frac{\cos 6\omega_0 t}{4} + \frac{\cos \omega_0 t}{4} \right. \\
 &\quad \left. + \frac{3}{2} \cos \omega_0 t + \frac{3}{4} \cos(2\omega_0 t + \omega_0 t) \right. \\
 &\quad \left. + \frac{3}{4} \cos \omega_0 t (\omega_0 t - 2\omega_0 t) \right. \\
 &\quad \left. + \frac{3}{2} \cos 2\omega_0 t + \frac{3}{4} \cos(2\omega_0 t + \omega_0 t) \right. \\
 &\quad \left. + \frac{3}{4} \cos \omega_0 t (\omega_0 t - \omega_0 t) \right\}
 \end{aligned}$$

— (4)

$$i = I_0 \left[(-V_{RF}) + \frac{(V_{RF})^2}{2} - \frac{(V_{RF})^3}{6} \right] \quad (3)$$

using ②, ③ and ④ in ① we get

$$\frac{i(t)}{I_0} \approx (\text{constant}) \left(\left(\frac{-A}{V_F} \right) - \left(\frac{3}{8} \right) \left(\frac{A}{V_F} \right)^3 \right)$$

$$+ (\text{constant}) \left(\left(\frac{-A}{V_F} \right) - \left(\frac{3}{8} \right) \left(\frac{A}{V_F} \right)^3 \right)$$

$$+ \frac{1}{2} (\cos m\omega_F t + \cos m\cdot 2\omega_F t) \left(\frac{A}{V_F} \right)^2$$

$$+ \frac{1}{2} \left(\frac{A}{V_F} \right)^2 + \frac{1}{2} \left(\frac{A}{V_F} \right)^2 (\cos m(\omega_F + f_c)t + \cos m(\omega_F - f_c)t)$$

$$- \frac{1}{24} \left(\frac{A}{V_F} \right)^3 (\cos(2m\cdot 3f_c)t + \cos(m\cdot 3f_c)t)$$


$$- \frac{1}{8} \left(\frac{A}{V_F} \right)^3 (\cos m(\omega_F + 2\omega_F)t + \cos m(\omega_F - 2\omega_F)t + \cos m(2\omega_F - \omega_F)t + \cos m(2\omega_F + \omega_F)t)$$

$$+ \cos m(2\omega_F + \omega_F)t$$

Spectrum $i(t)/I_0$

(c)

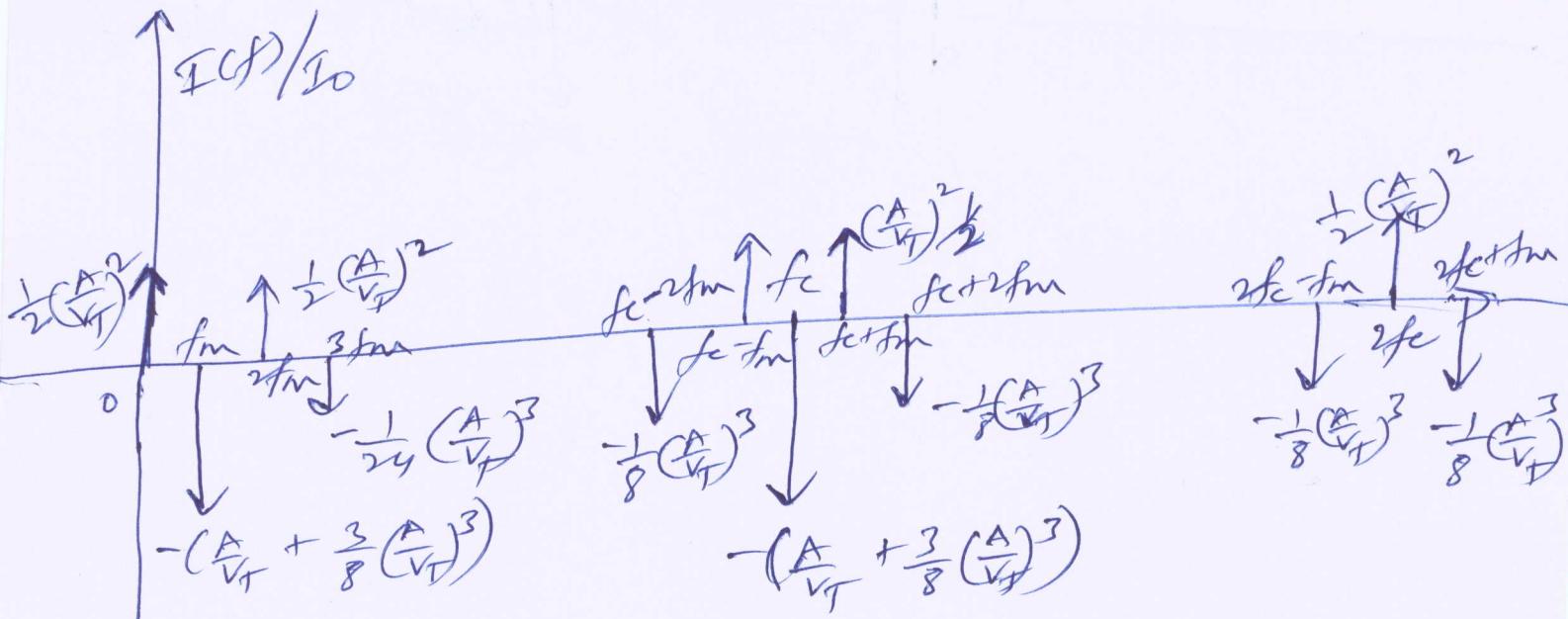$I(t)/I_0$ (only positive frequencies shown)




There are also signal components at $3fc$ (not shown in the above figure)

(c)

The AM signal in $i(t)/I_0$ is essentially the signal components at $f = fc, fc-fm$ and $fc+fm$.

With $fc = \omega_{kN}$, $fm = 1\text{kHz}$, the following band pass filter would be sufficient to filter out the AM signal from $i(t)$.

(3)

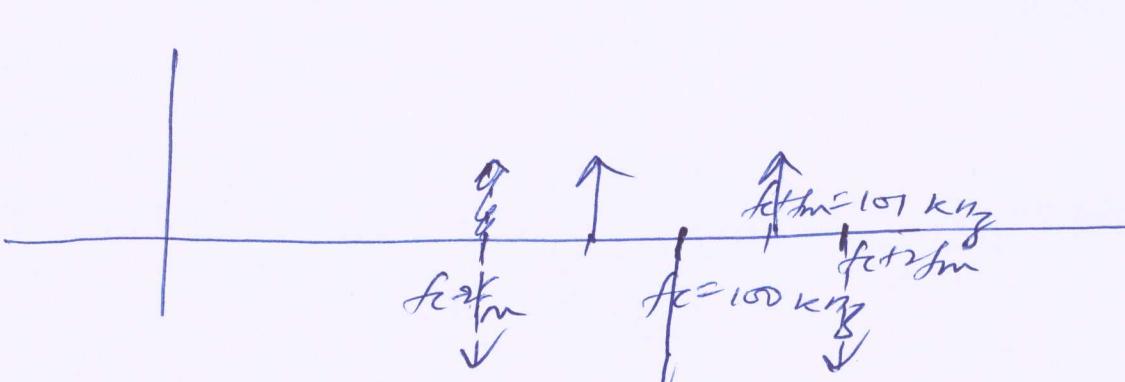

The nearest non-AM component is at $f = (f_c - 2f_m)$ and $(f_c + 2f_m)$.

The designed bandpass filter should therefore pass all signals in the frequency band $[f_{c-2fm}, f_{chm}]$


$$= [99 \text{ kHz}, 101 \text{ kHz}]$$

and reject ~~other~~ signals at other frequencies.

$$\therefore H(f) = \begin{cases} 0, & f > 101.5 \text{ kHz} \\ 1, & 98.5 \leq f \leq 101.5 \text{ kHz} \\ 0, & -98.5 \leq f < 98.5 \text{ kHz} \\ 1, & -101.5 \leq f \leq -98.5 \text{ kHz} \\ 0, & f < -101.5 \text{ kHz} \end{cases}$$

 $H(f)$

similarly on
the negative side

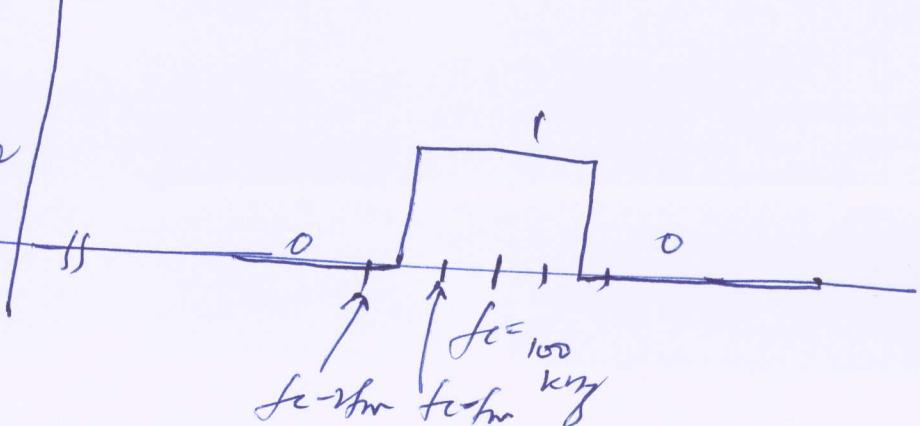



(6)

$$s(t) = I_0 \left(\frac{1}{2} \left(\frac{A}{V_T} \right)^2 \cos \text{infet} + \frac{1}{2} \left(\frac{A}{V_T} \right)^2 \right)$$

$$s(t) = I_0 \left(\frac{1}{2} \left(\frac{A}{V_T} \right)^2 \cos \text{m (infet)} + \frac{1}{2} \left(\frac{A}{V_T} \right)^2 \cos \text{m (fc-infet)} \right)$$

$$\left. - \left[\left(\frac{A}{V_T} \right)^2 + \left(\frac{3}{8} \right) \left(\frac{A}{V_T} \right)^3 \right] \cos \text{mfc} \right)$$

$$= -I_0 \left(\text{fc mfc} \cos \text{mfc} \cdot \left(\frac{A}{V_T} \right)^2 \cdot \frac{1}{4} \right.$$

$$\left. + \left[\left(\frac{A}{V_T} \right)^2 + \left(\frac{3}{8} \right) \left(\frac{A}{V_T} \right)^3 \right] \cos \text{mfc} \right)$$

$$= -I_0 \left[\left(\frac{A}{V_T} \right)^2 + \left(\frac{3}{8} \right) \left(\frac{A}{V_T} \right)^3 \right] \cos \text{mfc} \quad \begin{matrix} \leftarrow \text{carrier} \\ \downarrow \text{signal} \end{matrix}$$

$$\left. \left\{ 1 - \frac{\left(\frac{A}{V_T} \right)^2 \cos \text{mfc}}{\left[\left(\frac{A}{V_T} \right)^2 + \left(\frac{3}{8} \right) \left(\frac{A}{V_T} \right)^3 \right]} \right\} \right)$$

$$= -I_0 \left[\left(\frac{A}{V_T} \right)^2 + \left(\frac{3}{8} \right) \left(\frac{A}{V_T} \right)^3 \right] \cos \text{mfc}$$

$$\left. \left\{ 1 - \frac{\cos \text{mfc}}{\left(\frac{A}{V_T} \right)^2} \right\} \right)$$


percentage modulation

$$= 100 \times \frac{\left(\frac{A}{V_T} \right)^2}{\left[\left(\frac{A}{V_T} \right)^2 + \left(\frac{3}{8} \right) \left(\frac{A}{V_T} \right)^3 \right]}$$

$$= 9.11\%$$

(3-1)

7

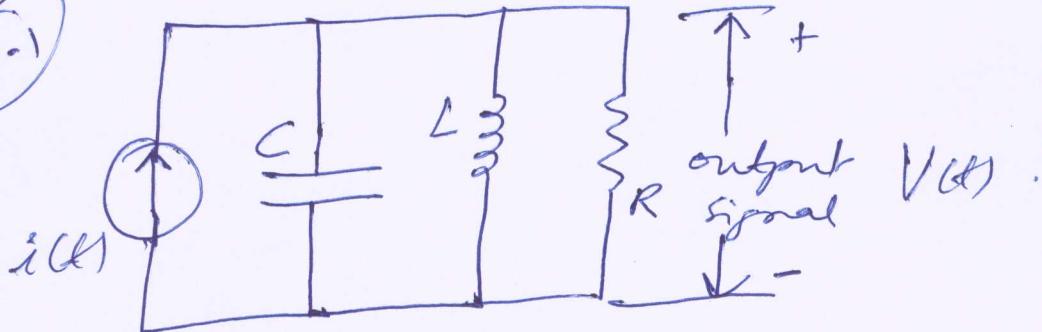

Combined impedance (2)

$$\begin{aligned} \frac{1}{Z} &= j\omega C + \frac{1}{j\omega L} + \frac{1}{R} \\ &= jmfc + \frac{1}{jmfl} + \frac{1}{R} \\ &= \frac{R + jmfl - 4\pi^2 f^2 RLC}{jmfl R} \end{aligned}$$

$$\therefore Z = \frac{jmfl R}{R(1 - (mfl)^2 C) + jmfl} \quad (1)$$

$$i(t) = E_0 f$$


~~Since $i(t) = E_0 f$~~

$$\begin{aligned} \therefore \frac{V(t)}{I(t)} &= Z(t) = \frac{jmfl R}{R(1 - (mfl)^2 C) + jmfl} \\ &= \frac{R \cdot jmfl}{R(1 - (mfl)^2 C) + jmfl} \end{aligned}$$

$$\frac{V(t)}{I_{eff}} = \frac{R}{\left(1 - \frac{jR}{mfl}(1 - (mfl)^2 C)\right)}$$

$$\therefore \text{Power gain} = \frac{|V(A)|^2}{|Z(g)|^2} = |Z(g)|^2$$
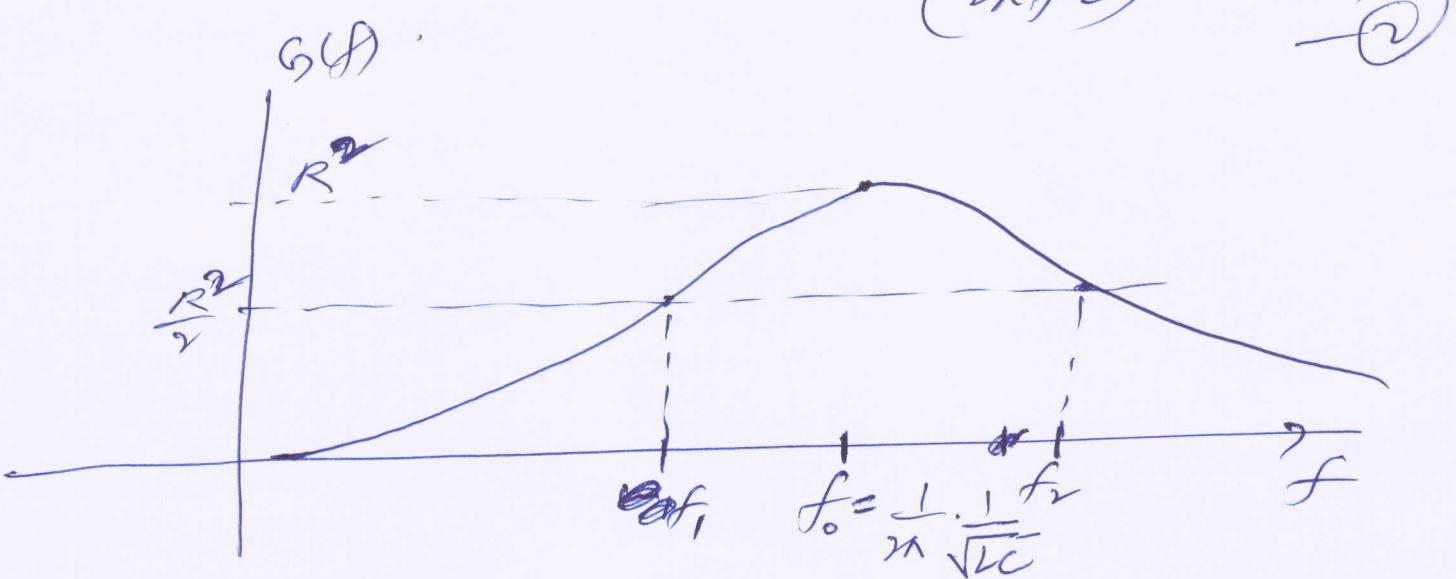
$$= \frac{R^2}{1 + R^2 \left[1 - (\pi f)^2 LC \right]^2} = G(f).$$



~~Next we find we observe that -~~

$$f_0 = \arg \max_f G(f) = \frac{1}{\pi} \cdot \frac{1}{\sqrt{LC}} \quad \text{and}$$

$$G(f_0) = R^2.$$

Note that $\lim_{f \rightarrow \infty} G(f) = \lim_{f \rightarrow 0} G(f) = 0$, so

it is a bandpass filter. (2)

Next we are interested in finding the bandwidth (3-dB) of this bandpass filter.

The Q-factor of this bandpass filter is defined as

$$Q = \frac{\omega_0}{\Delta\omega}, \quad \text{---} \quad (9)$$

$$= \frac{m f_0}{m \Delta f} = \frac{f_0}{\Delta f}, \quad \text{where } \Delta f \quad (9)$$

ω_0 is the center bandwidth and Δf is the 3-dB bandwidth of the filter.

The 3-dB bandwidth is defined as the difference $f_2 - f_1$,

where $f_2 > f_0 > f_1$ are such that

$$10 \log_{10} \frac{S(f_2)}{S(f_0)} = 10 \log_{10} \frac{S(f_1)}{S(f_0)} = -3 \text{ dB},$$

$$\text{i.e., } S(f_2) = S(f_1) = \frac{S(f_0)}{2}.$$

"e)" we need to solve for f such that

$$\frac{R^2 (1 - (mf)^2 LC)^2}{(mf)^2} = 1$$

$$\text{or } 1 - (mf)^2 LC = \pm \frac{mfL}{R}.$$

\therefore we have the two solutions.

$$\text{Since } f_0 = \frac{1}{\sqrt{m}} \cdot \frac{1}{\sqrt{2\pi}} \quad (10)$$

$$(mf_0)^2 = k_e \quad \begin{matrix} \text{we examine the} \\ \text{equation} \\ \text{first.} \end{matrix}$$

$$1 - (f_{lk})^2 = + \frac{\cancel{2} \cancel{1} f_0 L}{R} (f_{lk}).$$

$$\therefore (f_{lk})^2 + \left(\frac{mf_0 L}{R}\right)(f_{lk}) \neq 1 \Rightarrow$$

$$\frac{f_{lk}}{f_0} = \frac{-mf_0 L}{R} \pm \sqrt{\left(\frac{mf_0 L}{R}\right)^2 + 4}$$

This gives us

$$\frac{f_1}{f_0} = \frac{\sqrt{\left(\frac{mf_0 L}{R}\right)^2 + 4} - \frac{mf_0 L}{R}}{2} \quad (11)$$

Taking the negative equation

$$1 - (mf_0 L)^2 = - \frac{mf_0 L}{R}$$

we get

$$1 - (f_{lk})^2 = - \frac{mf_0 L}{R} (f_{lk})$$

$$\text{i.e., } (f_{lk})^2 + \frac{mf_0 L}{R} (f_{lk}) - 1 = 0.$$

which gives us

$$\frac{f_2}{f_0} = \frac{\frac{mf_0 L}{R} + \sqrt{4 + \left(\frac{mf_0 L}{R}\right)^2}}{2} \quad (12)$$

using ⑥ and ⑦ in ⑤ we have (11)

$$\frac{\Delta f}{f_0} = \frac{f_2 - f_1}{f_0} = \left(\frac{f_2}{f_0}\right) - \left(\frac{f_1}{f_0}\right)$$

$\in \theta \left(\frac{\text{end } L}{R} \right)$

$$\therefore \theta = \frac{f_0}{\Delta f} = \frac{R}{(m \cdot f \cdot L)} = 175. \quad \rightarrow ⑧$$


It is also given that the filter is tuned to the carrier frequency $f_c = 1 \text{ MHz}$.

To examine the filter output i.e.,

$$m(t) = A \cos \omega t (1 + 0.5 \cos 2\pi f_m t)$$

where $f_c = 1 \text{ MHz}$ and

$$f_m = 5 \text{ kHz}.$$

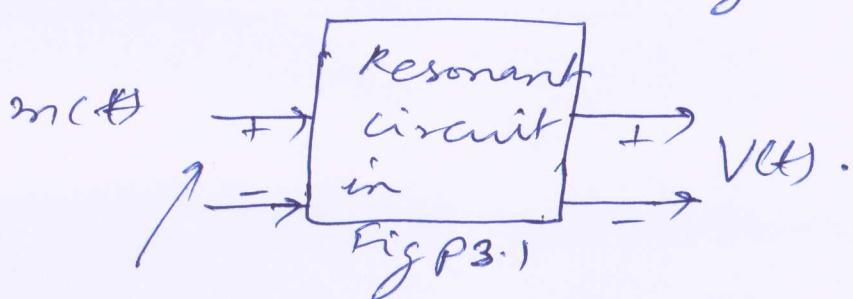

input is applied as a current source.

The phase response of the resonant circuit
is

$$\frac{V(f)}{Z(f)} = \left| \frac{V(f)}{I(f)} \right| e^{j\phi(f)}$$

$$\begin{aligned} \cos \phi(f) &= \frac{1}{\sqrt{1 + \left(\frac{R}{2\pi f L}\right)^2 (1 - (2\pi f)^2 C)^2}} \\ &= \frac{1}{\sqrt{1 + \left(\frac{R}{2\pi f_0 L}\right)^2 \cdot \frac{1}{(f/f_0)^2} (1 - (f/f_0)^2)^2}} \end{aligned}$$
— (19)

$$\begin{aligned} \sin \phi(f) &= \frac{\left(\frac{R}{2\pi f_0 L}\right) \cdot \frac{1}{(f/f_0)} (1 - (f/f_0)^2)}{\sqrt{1 + \left(\frac{R}{2\pi f_0 L}\right)^2 \cdot \frac{1}{(f/f_0)^2} (1 - (f/f_0)^2)^2}} \end{aligned}$$

\therefore using the fact that

$$\left(\frac{R}{2\pi f_0 L}\right) = 175 \text{ and } f_0 = 10^6 \text{ Hz, we have}$$

$$\begin{aligned} \therefore \text{for } f_2 &= f_0 + \Delta f = (10^6 + 5 \times 10^3) \text{ Hz} \\ &= 1.005 \times 10^6 \text{ Hz.} \end{aligned}$$

$$\cos \phi(f_2) = 0.9971$$

$$\sin \phi(f_2) = -0.08677$$

$$\therefore \phi(f_2) \approx \cancel{-13^\circ}$$

(13)

Similarly.

$$f = f_0 - f_m = 0.995 \times 10^6 \text{ Hz}$$

using equation (9) we get-

$$\cos \phi(f) = 0.9952$$

$$\sin \phi(f) = 0.8688$$

$$\therefore \phi(f) \approx \frac{\pi}{3}$$

∴ Magnitude response

$$\left| \frac{V(f)}{I(f)} \right| = \frac{R}{\sqrt{1 + \left(\frac{R}{mL}\right)^2 \cdot \frac{1}{(f/f_0)^2} (1 - (f/f_0)^2)^2}}$$

$$\therefore \left| \frac{V(f_0)}{I(f_0)} \right| \approx \frac{R}{2} \quad (0.9971 R \text{ to be precise})$$

and

$$\left| \frac{V(f)}{I(f)} \right| \approx \frac{R}{2} \quad (0.9952 R \text{ to be precise})$$

∴ the output of the resonant circuit is

$$v(t) = \frac{R}{2} \cos(\omega_0 t + \phi_0) + \frac{R}{2} \cos(\omega_0 t + \phi_0 - \frac{\pi}{3})$$

(19)

The input to the resonant circuit is a AM signal



with 50% modulation, i.e.,

$$m(t) = A \cos m(f_t + f_m)t$$


$$f_c = 1 \text{ MHz} \quad f_m = 5 \text{ kHz}$$

$$\begin{aligned} \therefore m(t) &= A \cos m(f_t + f_m)t \\ &\quad + \frac{A}{4} \cos m(f_c - f_m)t \\ &\quad + \frac{A}{4} \cos m(f_c + f_m)t \end{aligned} \quad \text{--- (10)}$$

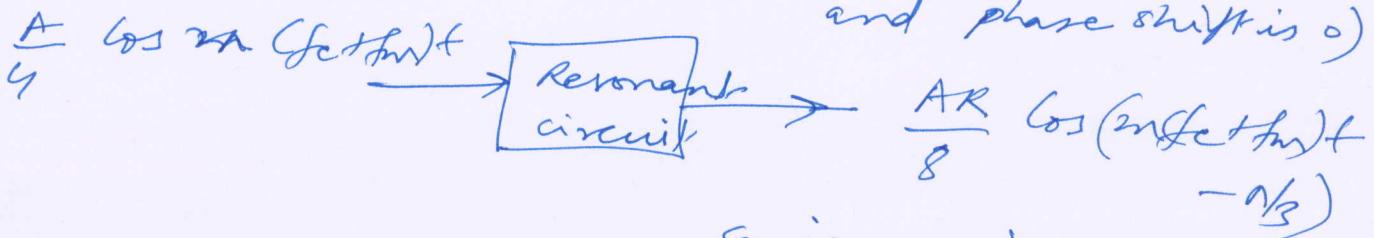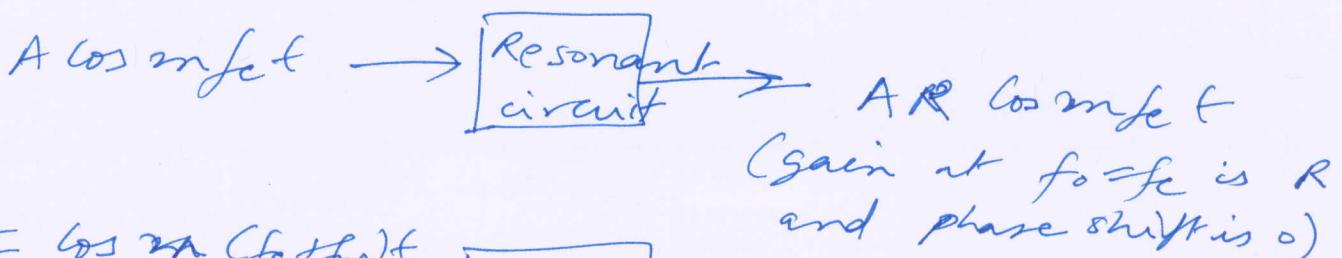The output to m(t) is the ~~time~~ sum of ~~over~~ the outputs to all the three signal terms in (10).



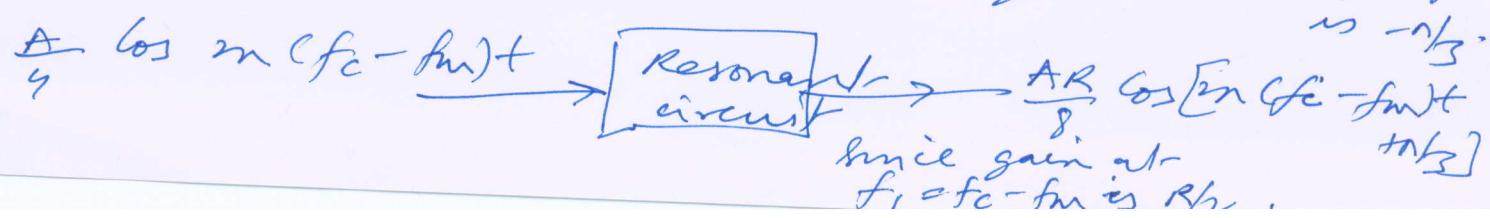Since gain at $f_c - f_m = f_2$ is $\frac{R}{2}$ and phase shift is $-\frac{\pi}{3}$.



∴ The output of the resonant circuit is

(13)

$$S(t) = AR \cos \omega t$$

$$+ \frac{AR}{8} \cos [\omega_m (f_c + f_m)t - \frac{\pi}{3}]$$

$$+ \frac{AR}{8} \cos \cancel{\omega_m} (\omega_c - \omega_m)t + \frac{\pi}{3}$$

$$= AR \cos \omega t$$

$$+ \frac{AR}{8} [2 \cos \omega t \\ \cos (\omega_m t - \frac{\pi}{3})]$$

$$= AR \cos \omega t \left[1 + \frac{1}{4} \cos (\omega_m t - \frac{\pi}{3}) \right]$$

This is also an AM signal, but whose percentage modulation is $\frac{1}{4}$.

Note that the percentage modulation has dropped due to the ^{higher} filtering loss/gain of the signal components at $(f_c + f_m)$ and $(f_c - f_m)$ when compared to the filter loss/gain at $f = f_c$.

(3.5)

(16)

$$x(t) = A_c [1 + \mu \cos(\omega_{\text{mf}} t)] \cos(\omega_{\text{rf}} t).$$

$$\mu \ll 1, f_c \gg f_{\text{mf}}.$$

a) The output of the ideal envelope detector is

$$v(t) = A_c / |1 + \mu \cos(\omega_{\text{mf}} t)|.$$

Note that $v(t)$ is periodic with period $T = \frac{1}{f_{\text{mf}}}$.

$$v(t) = v(t+T).$$

∴ the Fourier series representation of $v(t)$ is given by

$$v(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(n\omega_{\text{mf}} t) + \sum_{n=1}^{\infty} b_n \sin(n\omega_{\text{mf}} t).$$

$$b_n = \frac{1}{2f_{\text{mf}}} \int_{-\frac{1}{2f_{\text{mf}}}}^{\frac{1}{2f_{\text{mf}}}} v(t) \sin(n\omega_{\text{mf}} t) dt.$$

$$a_n = 2f_{\text{mf}} \int_{-\frac{1}{2f_{\text{mf}}}}^{\frac{1}{2f_{\text{mf}}}} v(t) \cos(n\omega_{\text{mf}} t) dt.$$

Since $V(t) = V(-t)$, by Q3 . (12)

$$a_n = 2f_m A_c \int_0^{\frac{T}{2m}} |1 + \mu \cos \omega_0 t| \cos(n\omega_0 t) dt$$

Note that

$$1 + \mu \cos \omega_0 t > 0$$

for

$$\cos \omega_0 t > -\frac{1}{\mu}$$

~~cos~~

~~sin~~

i.e.

$$\frac{\pi}{2} + \delta < 2\omega_0 t < \frac{3\pi}{2} - \delta$$

where $\sin \delta = \frac{1}{\mu}$. (assuming $\mu > 1$)

let $w = \omega_0 t$, then $dt = \frac{dw}{\omega_0}$

$$a_n = \frac{A_c}{\pi} \left[\int_0^{2n} |1 + \mu \cos w| \cos(nw) dw \right]$$

$$= \frac{A_c}{\pi} \left[\int_0^{\frac{\pi}{2} + \delta} (1 + \mu \cos w) \cos nw dw \right.$$

$$+ \int_{\frac{\pi}{2}}^{2n} (1 + \mu \cos w) \cos nw dw$$

$$- \int_{\frac{3\pi}{2} - \delta}^{\frac{3\pi}{2} - \delta} (1 + \mu \cos w) \cos nw dw \left. \right]$$

$$+ \int_{\frac{\pi}{2} + \delta}^{2n} (1 + \mu \cos w) \cos nw dw \left. \right]$$

(18)

for n_{21} . (using μ_{22} , $\alpha=1/6$)

$$q_1 = \frac{2A_C}{\pi} \left(\frac{1}{3} + \frac{\sqrt{3}}{2n} \right).$$

$$q_0 = \frac{A_C}{3} + \frac{4A_C}{n} \sin\left(\frac{2n}{3}\right)$$

The second harmonic is given by

$$q_2 = \frac{A_C \sqrt{3}}{n}.$$

\therefore The ratio of the second harmonic amplitude to the fundamental harmonic amplitude in VAC is

$$\frac{q_2}{q_1} = \frac{\sqrt{3}/n}{\frac{2}{3} + \frac{\sqrt{3}}{n}} = \frac{\sqrt{3}}{\sqrt{3} + \frac{2}{3}} = \frac{3\sqrt{3}}{3\sqrt{3} + 2}$$

Note that since $|m| > 1$, we get harmonic distortion. Also note that there is no harmonic distortion if $|m| < 1$.

(17)

3.6

$$V_2(t) = q_1 V_{1c} \cos t + q_2 V_{1c}^2 \cos^2 t.$$

$$V_1(t) = A_c [1 + k_a m(t)] \cos m(t).$$

$$\begin{aligned} V_2(t) &= q_1 A_c \cos m(t) \\ &\quad + q_2 A_c k_a m(t) \cos m(t) \end{aligned}$$

$$\begin{aligned} &\quad + q_2 A_c^2 (1 + k_a m(t))^2 \cos^2 m(t) \\ &= \underbrace{q_1 A_c \cos m(t)}_{T_1} + \underbrace{q_2 A_c k_a m(t) \cos m(t)}_{T_2} \\ &\quad + \frac{q_2 A_c^2}{2} (1 + \cos m(t)) (1 + k_a m(t))^2 \end{aligned} \quad \text{--- (1)}$$

If $m(t)$ is band limited to $[-\omega, \omega]$

and $f_c \gg \omega$ such that

$f_c - \omega > 2\omega$, then we can use a low pass filter with

frequency response $H(f) = \begin{cases} 1, & |f| < 2\omega \\ 0, & \text{otherwise} \end{cases}$

to retrieve $(1 + k_a m(t))^2$; i.e.,

$$V_2(t) \rightarrow \boxed{h(t)} \rightarrow \frac{\alpha A_c^2}{2} (1 + k_{\text{an}} \epsilon)^2 \quad (20)$$

To see this note that (see ① for T_1, T_2)

$$T_1(\omega) = a, A_c \cos \omega t$$

$$\text{has } T_1(f) = \frac{a, A_c}{2} (\delta(f-f_c) + \delta(f+f_c))$$

(i.e., has power at $f = \pm f_c$).

Similarly $T_2(\omega)$ has power only
in the band $(f_c - \omega, f_c + \omega)$


the term $\frac{\alpha A_c^2}{2} \cos(\epsilon \pi f t) (1 + k_{\text{an}} \epsilon)^2$
has power in the band
 $(2f_c - 2\omega, 2f_c + 2\omega)$.

The useful term

$\frac{\alpha A_c^2}{2} (1 + k_{\text{an}} \epsilon)^2$ has
power in the band
 $(-\omega, \omega)$.

Therefore by putting a filter with
passband $(-\omega, \omega)$ and assuming
that the other signal terms

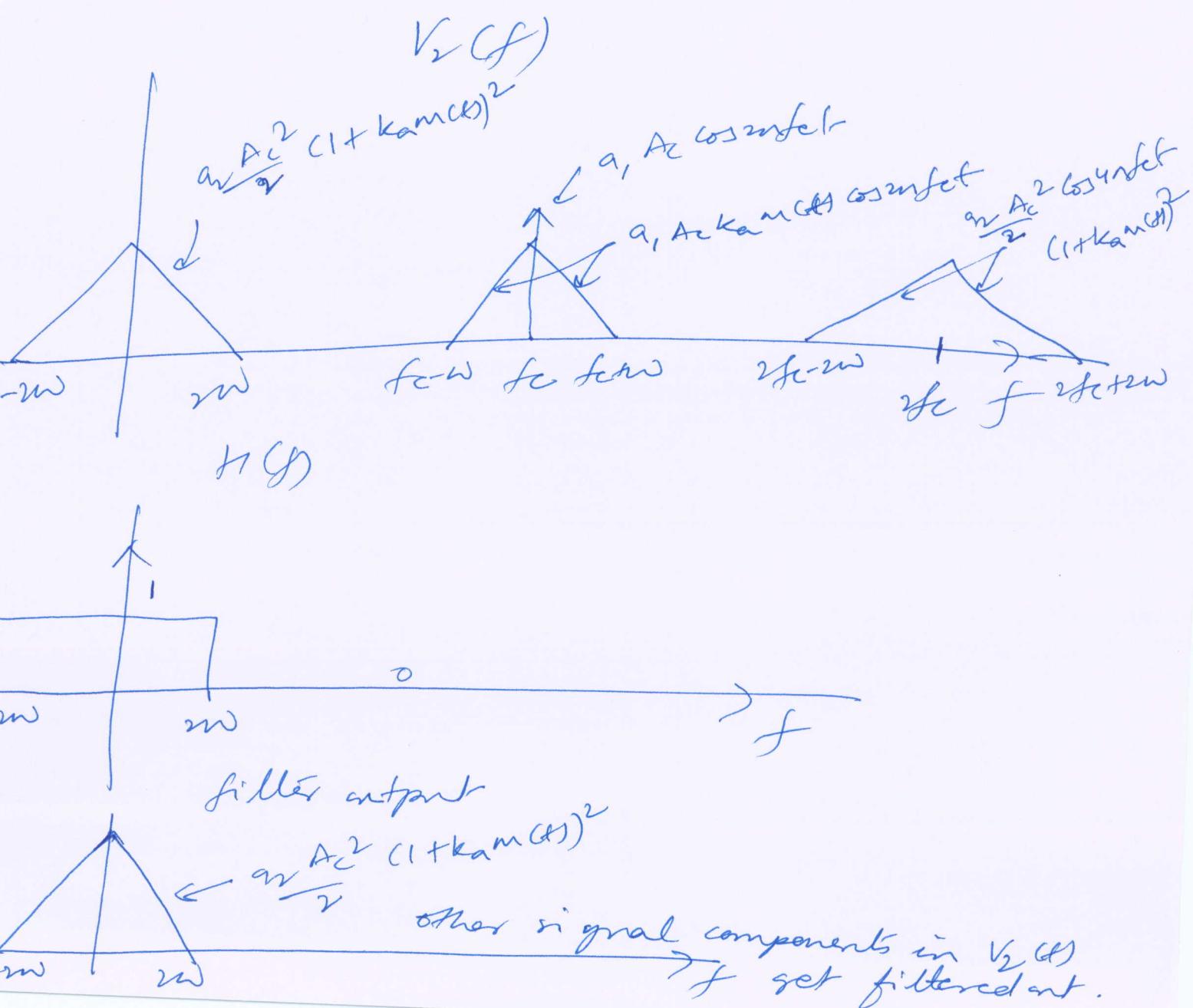don't overlap with the useful term in the frequency domain (i.e., for this to be satisfied $f_c - \omega > 2\omega$, i.e. $f_c > 3\omega$) we can get $\frac{\omega}{2} A_c^2 (1 + k_m(\omega))^2$ at the filter output.




(22)

The next question is how to extract
 the message signal $m(t)$ from
 the filter output $\frac{\omega^2 A_c^2}{2} (1 + k_m m(t))^2$.

If $|k_m m(t)| < 1$ for all t , then

$$1 + k_m m(t) > 0$$

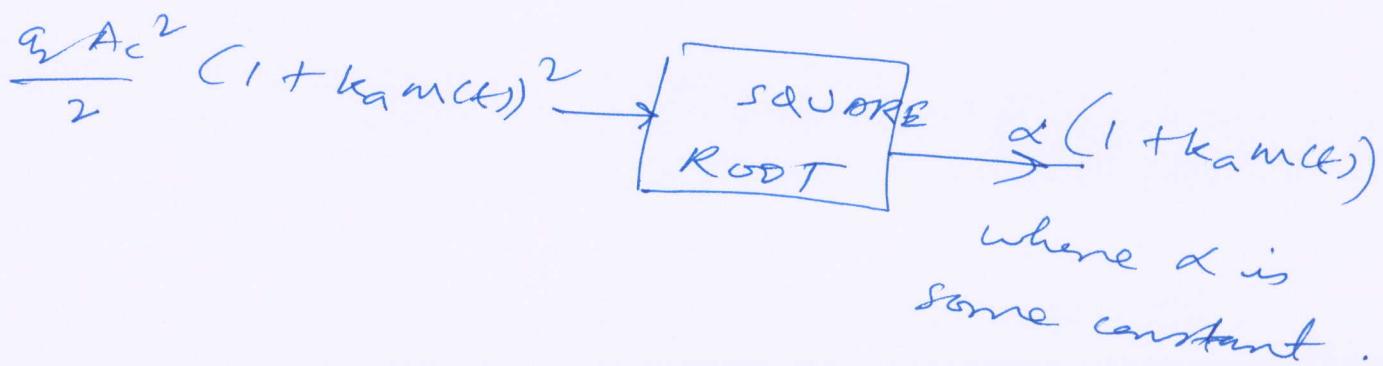\therefore a square root circuit will
 have as its output.




3.8

(23)

Assuming perfect synchronization at the receiver, the coherent receiver for the DSB-SC signal is


Ac m(e) cosinfet

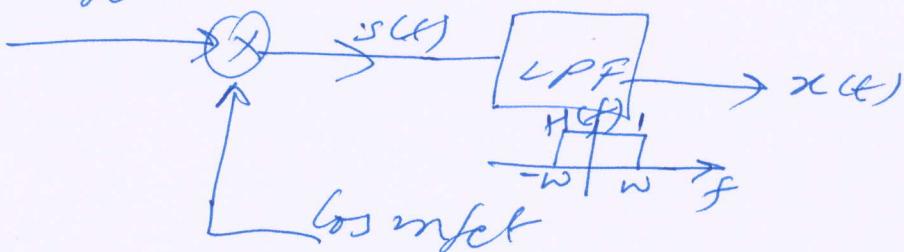

$$\delta(e) = A_c m(e) \cos^2 \text{infet}$$

$$= \frac{A_c m(e)}{2} (1 + \cos 4\pi f t)$$
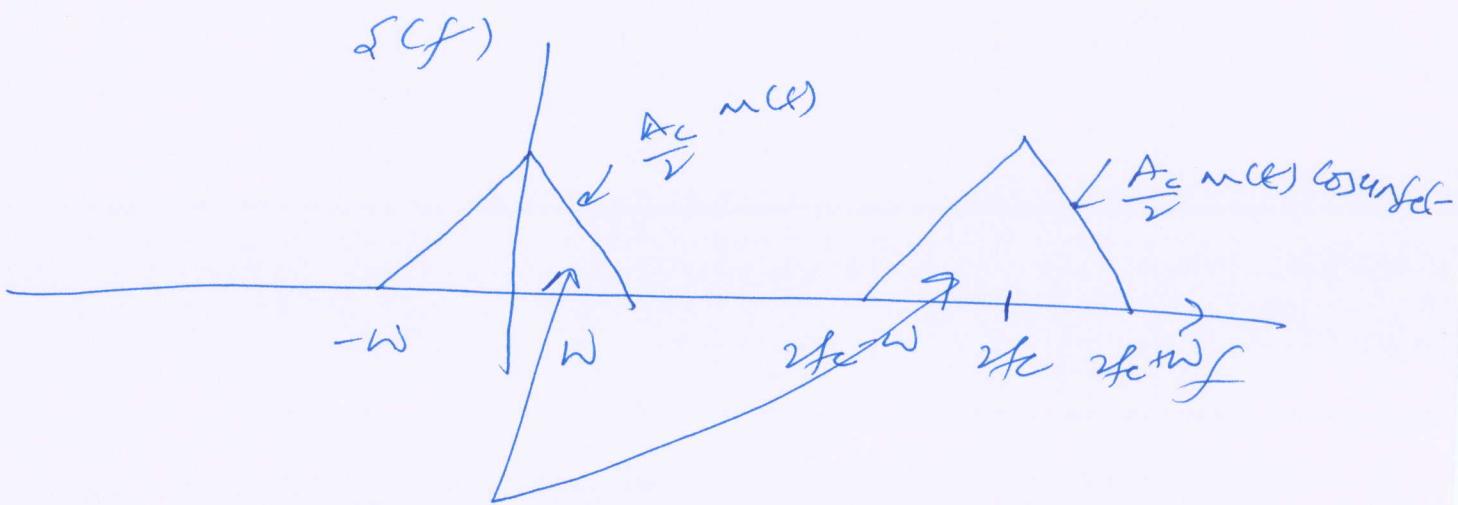
$$= \frac{A_c m(e)}{2} + \frac{A_c m(e)}{2} \cos 4\pi f t$$



for the receiver to detect $m(e)$ correctly, the bands $[-w, w]$ and $[2fc-w, 2fc+w]$ must be disjoint, i.e., $2fc-w > w$ or $fc > w$.
 ∴ the lowest frequency fc which allows correct detection is $fc = w = 1 \text{ kHz}$.


Prob. 3.8 continued.

(24)


a)

when $f_c = 1.25 \text{ kN}$.



$\delta(f)$.

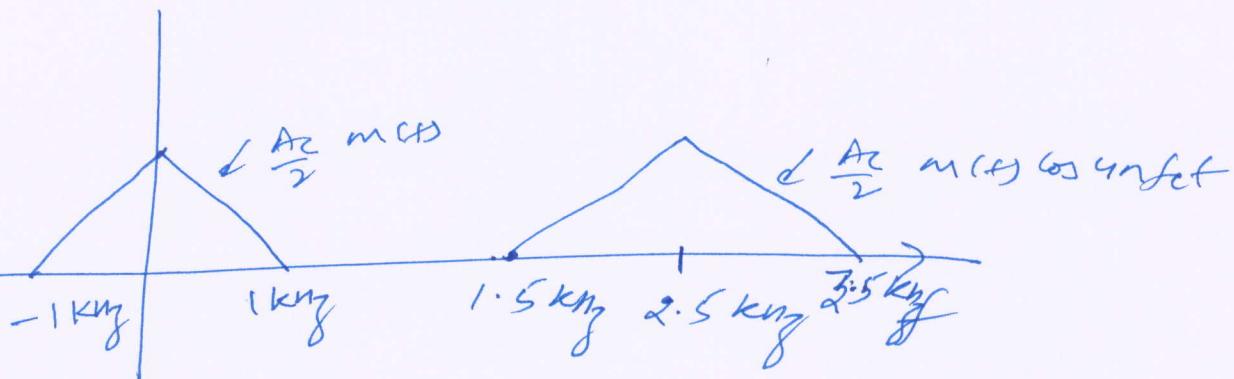

$X(f)$

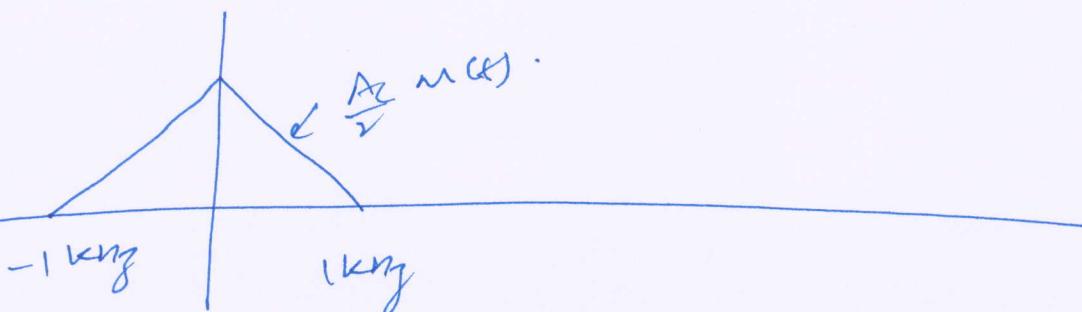

when $f_c = 0.75 \text{ kN}$ we have

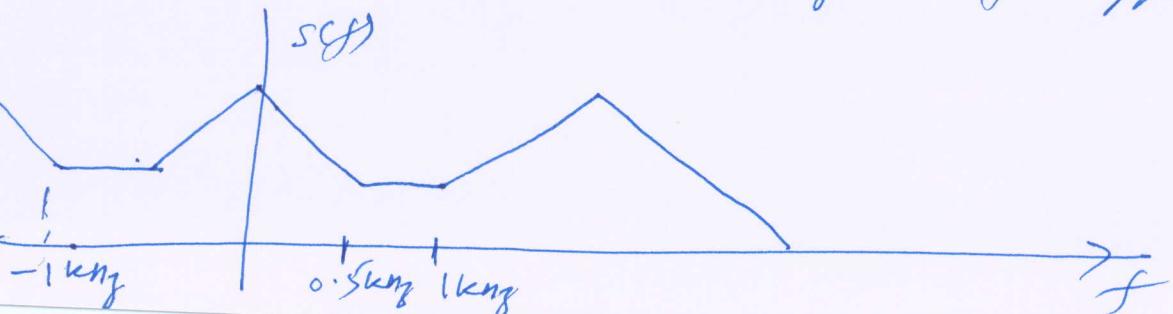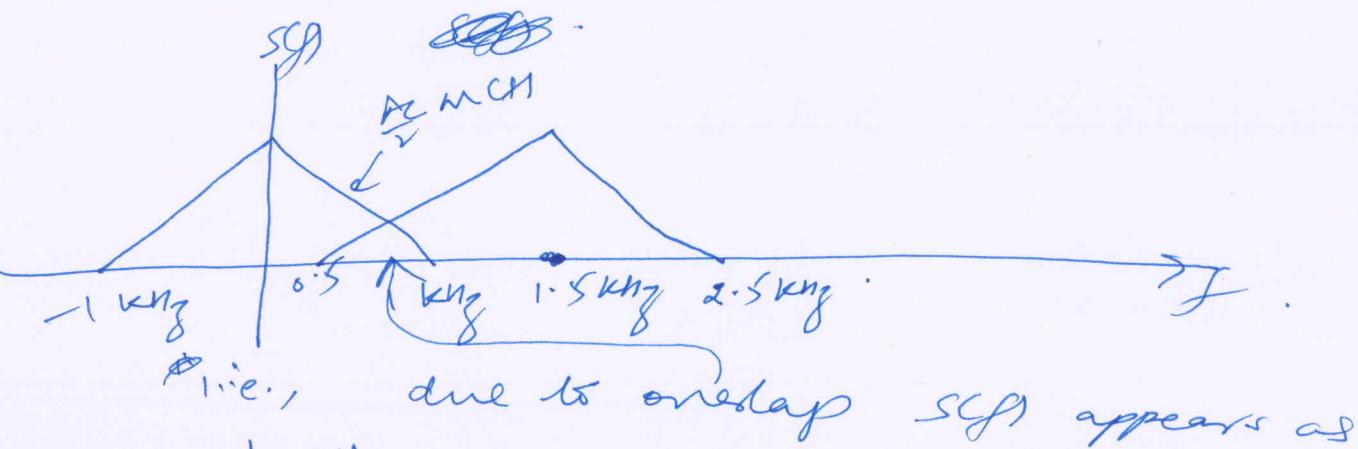


and therefore

(25)

$$\text{for } f_c = 0.25 \text{ kHz}$$

$$X(f) = S(f) + S(-f).$$

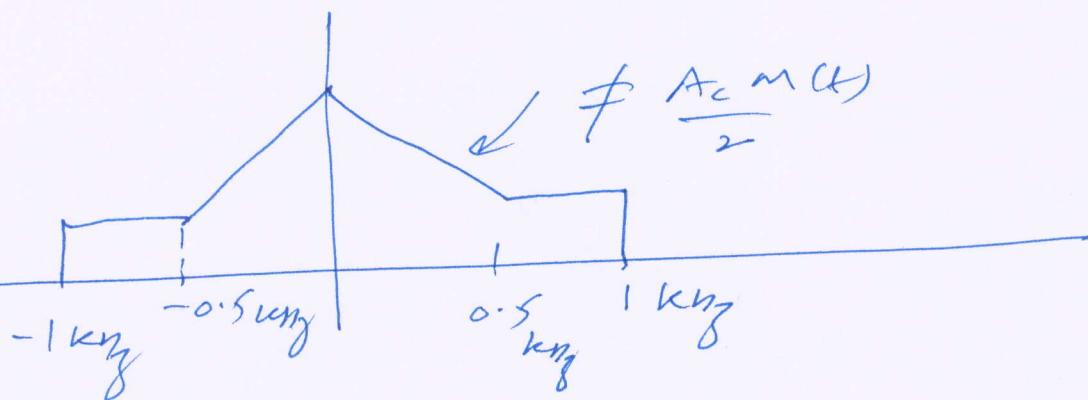

which is clearly not the
spectrum of $\frac{A_c m(t)}{2}$.

Therefore for $f_c = 0.25 \text{ kHz} < \omega$

the coherent detector is unable
to detect the message signal.