
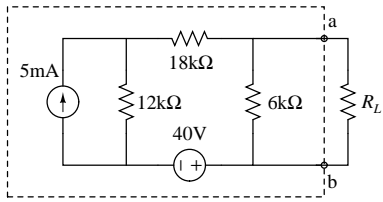


Indian Institute of Technology, Delhi
EEL 101: Fundamentals of Electrical Engineering
Tutorial 3, 29th January, 2008

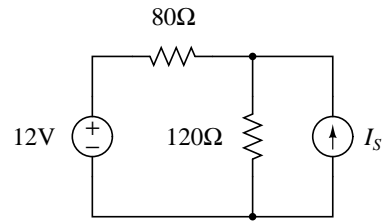
1. For the circuit in Fig. (a), replace the circuit in the box by its Thevenin equivalent. Find v_{ab} for $R_L = 3k\Omega$. What value of R_L receives maximum power from the circuit? What value of R_L makes the current in the $6\text{ k}\Omega$ resistor to be 0.1 mA ?
2. For the circuit in Fig. (b), find I_S such that the current in the 120Ω resistor is zero.
3. Using a Thevenin equivalent circuit, find R in Fig. (c) such that i is 0.5 A .
4. Using node voltage analysis find the voltage across the $20\text{ k}\Omega$ resistor in Fig. (d).
5. Solve for i in Fig. (e) using the loop-current method.
6. Find the power in the $100\ \Omega$ resistor in Fig. (f) using any method of your choice.




(a)




(b)

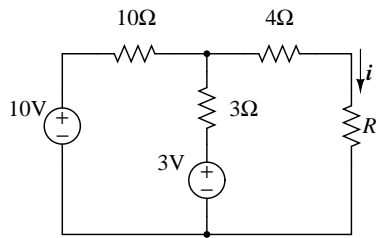


(c)

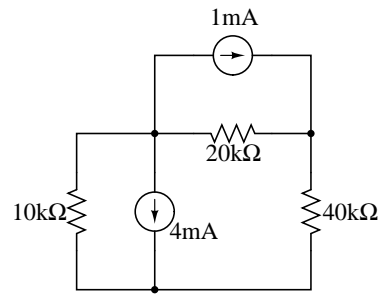

(d)

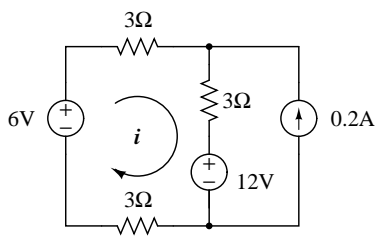

(e)

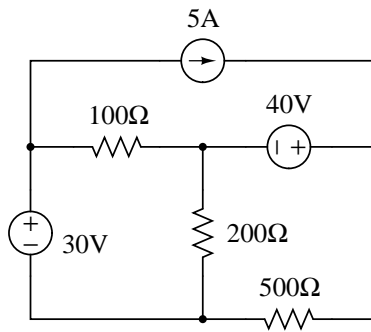

(f)