
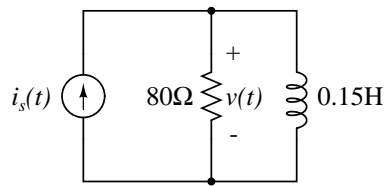


Indian Institute of Technology, Delhi
EEL 101: Fundamentals of Electrical Engineering
Tutorial 4, 29th January, 2008

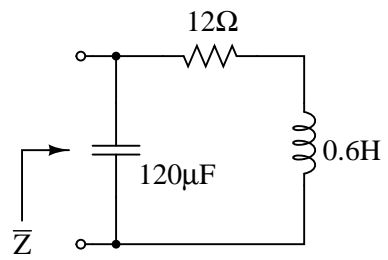
1. What will be the corresponding phasor, V , for $v(t) = 60 \cos(100\pi t - 120^\circ)$?
2. What time function is represented by $I = 6 + j9\mu\text{A}$, if the frequency is 400 Hz?
3. For the circuit in Fig. (a), solve for $v(t)$ when $i_s(t) = 0.8 \cos(1000t - 20^\circ)\text{A}$.
4. Determine the input impedance, \bar{Z} of the circuit shown in Fig. (b), if the frequency is 60 Hz.
5. Solve for $i(t)$ in Fig. (c), if $v(t) = 10 \cos(1000t)\text{Volts}$.
6. Transform the circuit in Fig. (d) to its Norton equivalent form.
7. By proper choice of X_C and X_L , the 10Ω resistor in Fig. (e) can be transformed to “look” like a 50Ω resistance at a specified frequency. Find X_C and X_L , such that at 1 kHz the input impedance, \bar{Z} , is 50Ω . What are the corresponding inductance and capacitance values?
8. Find $v_{ab}(t)$ in Fig. (f), if $v_1(t) = 100 \cos(120\pi t)$ Volts, and $v_2(t) = 80 \sin(120\pi t)$ Volts.




(a)




(b)

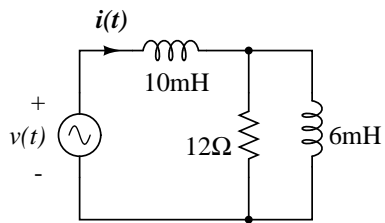


(c)

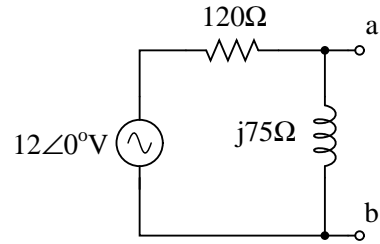

(d)

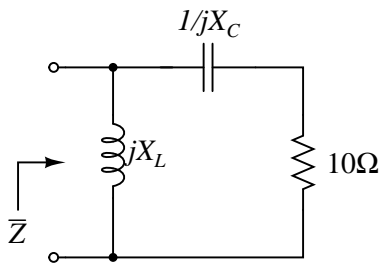

(e)

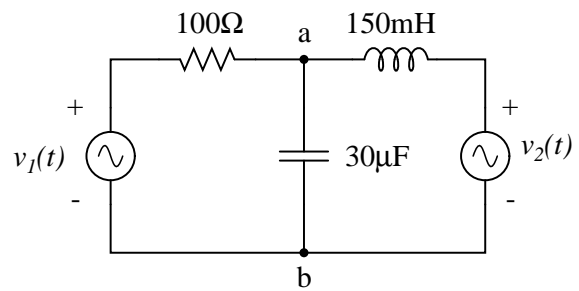

(f)