 


```

library ieee ;
use ieee.std_logic_1164.all;

entity seq_design is
port(
    a:          in std_logic;
    clock:      in std_logic;
    reset:      in std_logic;
    x:          out std_logic
);
end seq_design;
    
```

"RTL"



```

architecture FSM of seq_design is
    -- define the states of FSM model


    type state_type is (S0, S1, S2, S3);
    signal next_state, current_state: state_type;
    
```

```

begin
    -- cocurrent process#1: state registers
    state_reg: process(clock, reset)
    begin
        if (reset='1') then
            current_state <= S0;
        elsif (clock'event and clock='1') then
            current_state <= next_state;
        end if;
    end process;
    
```

always


posedge
clock

 

```

-- cocurrent process#2: combinational logic
comb_logic: process(current_state, a)
begin
    
```

inputs

 


```

-- use case statement to show the
-- state transistion
    
```

```

case current_state is
    when S0 =>
        x <= '0';
        if a='0' then
            next_state <= S0;
        elsif a='1' then
            next_state <= S1;
        end if;
    when S1 =>
        x <= '0';
        if a='0' then
            next_state <= S1;
        elsif a='1' then
            next_state <= S2;
        end if;
    when S2 =>
        x <= '0';
        if a='0' then
            next_state <= S2;
        elsif a='1' then
            next_state <= S3;
        end if;
    when S3 =>
        x <= '1';
        if a='0' then
            next_state <= S3;
        elsif a='1' then
            next_state <= S0;
        end if;
end case;
    
```

 

S3, 1 $\xrightarrow{?}$ x = 1
NS = held

S3 \rightarrow x = held

```
        when others =>
            x <= '0';
            next_state <= S0;
        end case;
    end process;
end FSM;
```

```

module state_machine (
    output y_out,
    input x_in, clock, reset
);
reg [1:0] current_state, next_state;
parameter S0=2b'00, S1=2b'01, S2=2b'10, S3=2b'11;

always @(posedge clk, negedge reset)
    if (reset == 0) current_state <= S0;
    else current_state <= next_state;

always @(x_in, current_state)
    case(current_state)
    S0: if(x_in) next_state <= S1; else next_state <= S0;
    S1: if(x_in) next_state <= S2; else next_state <= S0;
    S2: if(x_in) next_state <= S3; else next_state <= S0;
    S3: if(x_in) next_state <= S3; else next_state <= S0;
    default: next_state <= S0;
    endcase

always @(current_state)
    case(current_state)
    S0: y_out <= 0;
    S1: y_out <= 0;
    S2: y_out <= 0;
    S3: y_out <= 1;
    endcase
endmodule

```

