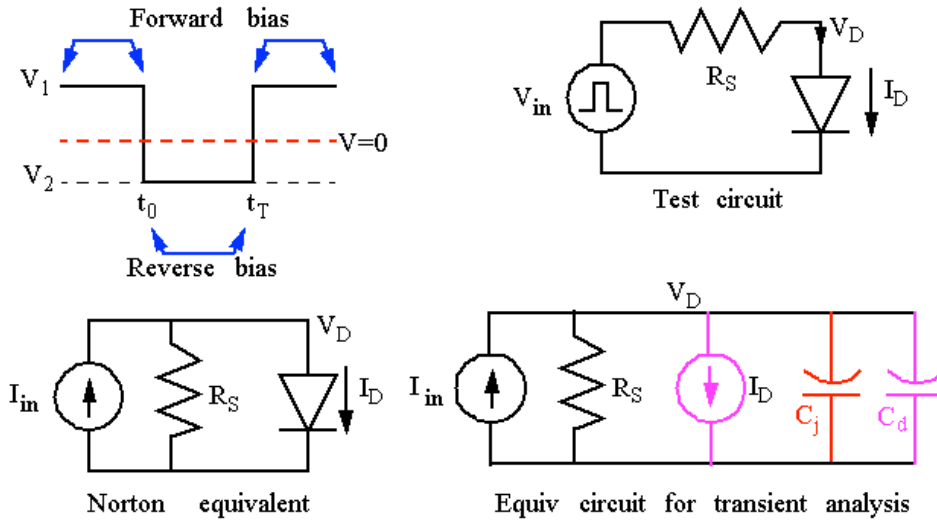


## Switching Time of a Diode

- *Switching Time of a diode is the time it takes to switch the diode between two states (ON and OFF states).*



- *Assume  $R_S$  is large enough that all current flows through diode in forward bias conditions.*

### Switching Time of a Diode

- *For Forward Bias:*
  - *Current source  $I_D$  is an ideal diode current source:  $I_D = I_S (e^{V_D / \phi_T} - 1)$*
  - *$C_j$  represents the space-charge ( junction capacitance ).*
  - *$C_d$  represents the excess minority carrier charge ( diffusion capacitance ).*
  - *(Note that both of these are small-signal capacitances; to be applicable large-signal analysis, average capacitance values must be used).*
- *For Reverse bias:*
  - *Eliminate the current source  $I_D$  and the diffusion capacitance  $C_d$ .*
- *Transient response requires finding a solution to:*

$$I_{in} = I_D(t) + (C_d + C_j) \frac{dV_D(t)}{dt}$$


$$I_{in} = I_S (e^{V_D(t) / \phi_T} - 1) + (C_d + C_j) \frac{dV_D(t)}{dt}$$

## Switching Time of a Diode

- *Transient response:*

- *The exponential and the non-linear dependence of  $C_d$  and  $C_j$  on  $V_D$  make this difficult to do by hand.*

- *Consider the simulated response:*

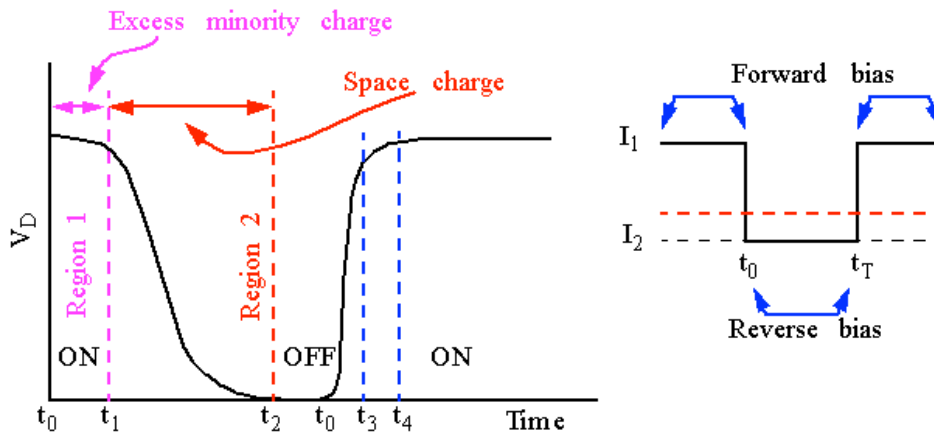

## Switching Time of a Diode

- *Turn-off Transient.*

- *The turn-off transient, has two operation intervals.*

- **Region 1 :**


- *Diode is on.*
  - *$I_2$  removes excess minority charge .*
  - *Voltage drop is small allowing  $C_j$  to be ignored since space-charge remains ~constant.*

- **Region 2 :**

- *$I_D \approx 0$  (diode off).*
  - *Space-charge changes while building a reverse-bias over the diode.*
  - *Therefore,  $C_j$  dominates performance.*
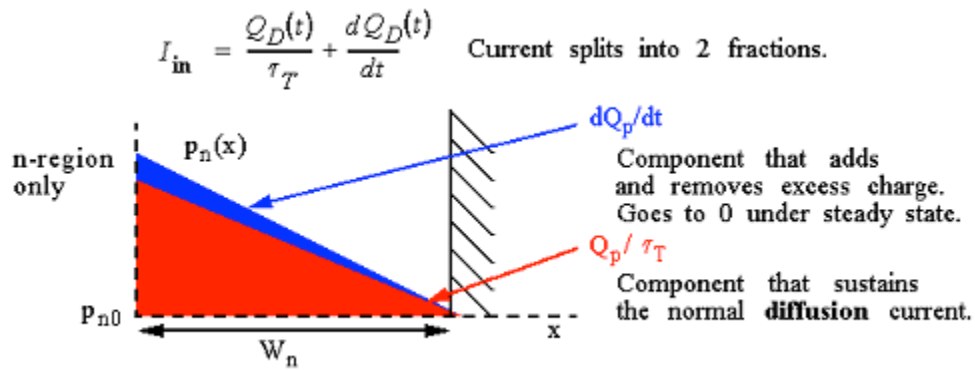
### Derivation of Turn-off Transient.

- **Region 1** : Removal of excess minority charge .
  - Charge-control expression:



The term  $\frac{dQ_D(t)}{dt}$  represents the current due to the removal of injected carriers from the base region and the term  $\frac{Q_D(t)}{\tau_T}$  represents the normal Diffusion current where  $\tau_T$  is the Base transit time.

○ Solving this differential equation assuming that:

$$Q_D = I_1 \tau_T \text{ at time } t = 0 \text{ or the initial value of } Q_D \text{ and } I_{in} = I_2$$

Where  $I_1 \approx \frac{(V_1 - V_D)}{R_S}$  is the current under forward bias and  $I_2 = \frac{V_2}{R_S}$

- Yields:  $Q_D(t) = \tau_T [I_2 + (I_1 - I_2)e^{-t/\tau_T}]$
- The turn-off time is derived by solving for the time  $t = t_1$  ( $Q_D$  evaluates to 0):

$$t_1 = \tau_T \ln \left[ \frac{(I_1 - I_2)}{-I_2} \right]$$

- **Region 2** : Changing the Space Charge.

- Diode is off, circuit evolves toward steady state.

$$V_D (t = \infty) = V_2 = I_2 R_S$$

- During this time, a reverse voltage is built over the diode.
- Therefore, space charge has to be provided.

- The change in excess minority charge can be ignored as well as the reverse bias diode current  $I_d$ .
- This leaves us with a simple RC circuit (red capacitor model shown earlier).

$I_2 = \frac{V_D(t)}{R_S} + C_j \frac{dV_D}{dt}$   $C_j$  is the average junction capacitance over the voltage range of interest.

- Assuming the value of  $V_D$  at time  $t = t_1$  is 0, the solution is the well-known exponential:

$$V_D(t) = I_2 R_S \left[ 1 - e^{-\frac{(t-t_1)}{R_S C_j}} \right]$$

- The 90% point is reached after 2.2 time-constants of  $R_S C_j$ .

$$t_2 - t_1 = 2.2 R_S C_j$$

- **Derivation of Turn-on Transient.**

- Similar considerations hold for the turn-on transient.
- Space Charge :
  - The transient waveform for the diode voltage (assume  $t = 0$ ):

$$V_D(t) = R_S \left[ I_1 - (I_2 - I_1) e^{-\frac{t}{R_S C_j}} \right]$$

$$t_3 = R_S C_j \ln \left[ \frac{I_1 - I_2}{I_1} \right] \quad \text{Assuming } V_D = 0$$

- Excess charge :

$$Q_D(t) = I_1 \tau_T \left[ 1 - e^{-\frac{(t-t_3)}{\tau_T}} \right]$$

- It takes 2.2 time constants for  $Q_D$  to reach 90% of its final value.

$$t_4 - t_3 = 2.2 \tau_T$$