

Indian Institute of Technology, Delhi
EEL 201: Digital Electronic Circuits
Quiz, 19th November, 2008

Each question or fill-in-the-blank carries 1 mark. A wrong answer will warrant -0.3 marks. Total is 20.

A. Consider the following piece of Verilog code:

```
module quiz (output myoutput1, output myoutput2, input myinput1,
input myinput2, input clk);
reg myoutput1;
reg [2:0] myoutput2;
reg [3:0] current_state, next_state;
reg internal_var1, internal_var2;

always @(posedge clk)
    current_state <= next_state;

always @(myinput1, current_state)
begin
    if(myinput1 == 1) next_state <= current_state + 1;
    else next_state <= current_state - 1;
    myoutput1 <= ~current_state[3];
end

always @(myinput2, current_state)
    if(myinput2 == 1) internal_var1 <= current_state[1];
    else internal_var1 <= current_state[0];


assign internal_var2 = current_state[3] & myinput1;

always @(internal_var1, myinput1, current_state)
    if(internal_var1) myoutput2 <= 3'b001;
    else if (current_state == 3'b010) myoutput2 <= 3'b110;

endmodule
```

1. The number of edge-triggered flip-flops that will be synthesized in the above code are _____.
2. The data-types of myinput1 and myinput2 are _____ and _____ respectively.
3. The number of level sensitive flip-flops that will be inferred from the code is _____. (Excluding the edge-triggered flip-flops).
4. myoutput1 is a _____ type output.
5. The combinational logic described in the third always statement can also be described in which of the following ways?
 - (a) `internal_var1 = current_state[1] & myinput2`
 - (b) `internal_var1 = current_state[0] & ~myinput2`
 - (c) `internal_var1 = (a) + (b)`
 - (d) `internal_var1 = ~((a) & (b))`
6. The output myoutput1 should be declared as a wire, and not as a reg. (True/False?)
7. internal_var2 should be declared as a wire, and not as a reg. (True/False?)

 B. Consider the following circuit diagram:



8. If $A=1, B=0, C=0$, the device M1 is _____, the device M2 is _____, the device M3 is _____. (On/Off?)

9. If $A=1, B=1, C=0$, the device M1 is _____, the device M2 is _____, the device M3 is _____. (On/Off?)

10. The circuit implements the function:

(a) $X = \overline{(A + B)C}$

(b) $X = \overline{(A + C)B}$

(c) $X = \overline{AC + B}$

(d) $X = \overline{(A + C)B}$

C. Answer the following questions:

11. A PLD contains:

- (a) Programmable OR gates
- (b) Programmable AND gates
- (c) Programmable XOR gates
- (d) (a), (b) and (c)

12. In addition to all the gates and flip-flops available in a CPLD, an FPGA will also contain _____.

13. In a particular FPGA, the set-up and hold times of all the flip-flops are 10 pico-seconds, and 20 pico-seconds respectively. In my design, the total worst case gate-delay of all the combinational logic between the “Q” outputs of the flip-flops, and the “D” inputs of the flip-flops is 170 pico-seconds. The maximum clock frequency that I can possibly use is _____ Hz.

14. I am designing an integrated circuit with several edge-triggered flip-flops, all timed by the same 3 GHz clock. The maximum phase difference, between the clocks of two edge-triggered flip-flops, that I can tolerate is 45° . Assume that the signals travel at the speed of light (in vacuum = 3×10^8 m/s). The maximum length of the wire used for the clock signal is _____.

15. For TTL (transistor-transistor-logic), a BJT (bipolar-junction transistor) can be viewed as a _____-controlled switch.