

ELECTRICAL ENGINEERING DEPARTMENT
EEL 204 ANALOG ELECTRONIC CIRCUITS
TUTORIAL SHEET 2

January 18, 2011

- Q1. An amplifier shown in Fig. 1 has a transistor with $100 \leq \beta \leq 300$. The transistor has $V_{BE} = 0.7V$. If R_{BB} is $1K\Omega$, find the maximum possible symmetrical swing. Find R_1 , R_2 , R_C and R_E given that $I_{CQ} = 5mA$. What is the maximum deviation from the design specification of I_{CQ} ?

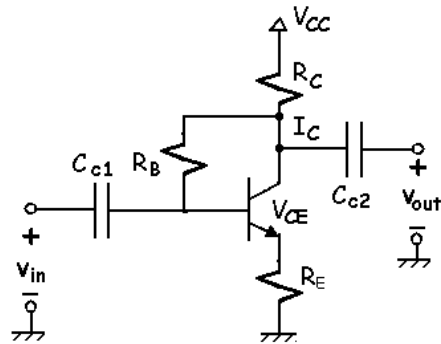


Fig. 2

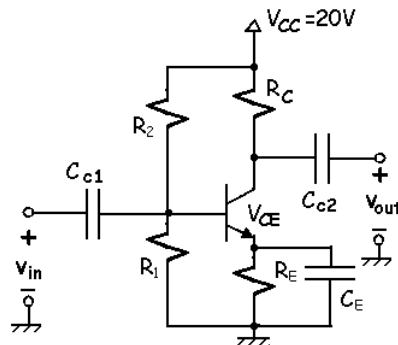


Fig. 1

- Q2. For the amplifier configuration in Fig. 1, starting from $I_C = \beta I_B + (\beta + 1)I_{CBO}$ obtain a relationship for the collector current. The transistor $I_{CBO} = 0.1\mu A$ and the temperature ranges between $-25^\circ C$ to $75^\circ C$. How will the maximum swing over the temperature range affect the maximum possible symmetrical swing? The change in I_{CBO} is modeled as $\Delta I_{CBO} = I_{CBO}(\exp(0.07\Delta T) - 1)$.
- Q3. Find out the relationship for I_{CQ} in the amplifier configuration shown in Fig.2 and identify the condition to obtain I_{CQ} independent of variations in β . Given that $V_{CC} = 12V$, $I_{CQ} = 5mA$, obtain R_B , R_C and R_E for maximum symmetric swing at the output. Also obtain the gain of the amplifier.

- Q4. For the Common Emitter Amplifier in Fig. 3 given that $\beta = 100$, $I_C = 1mA$, $V_{BE} = 0.75V$ and $C_E \rightarrow \infty$, find
1. The value of the resistance R_{E1}
 2. The value of the resistance R_C
 3. The gain (V_o/V_s)
 4. The maximum peak to peak swing achievable for an undistorted sinusoidal output.

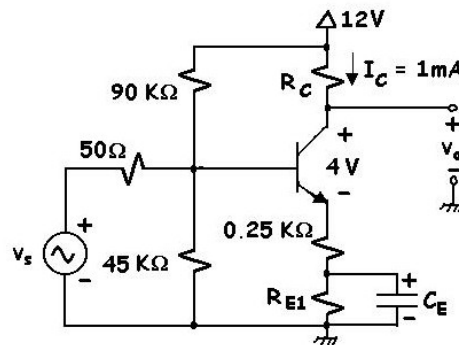


Fig. 3