

Indian Institute of Technology, Delhi
EEL 204: Analog Electronic Circuits
Tutorial 7, March 21, 2011

For all the BJTs, assume all devices have β of 100, r_o is 100 k Ω . Find the input resistance, the output resistance and the voltage gain from the input to the output in all four circuits.

