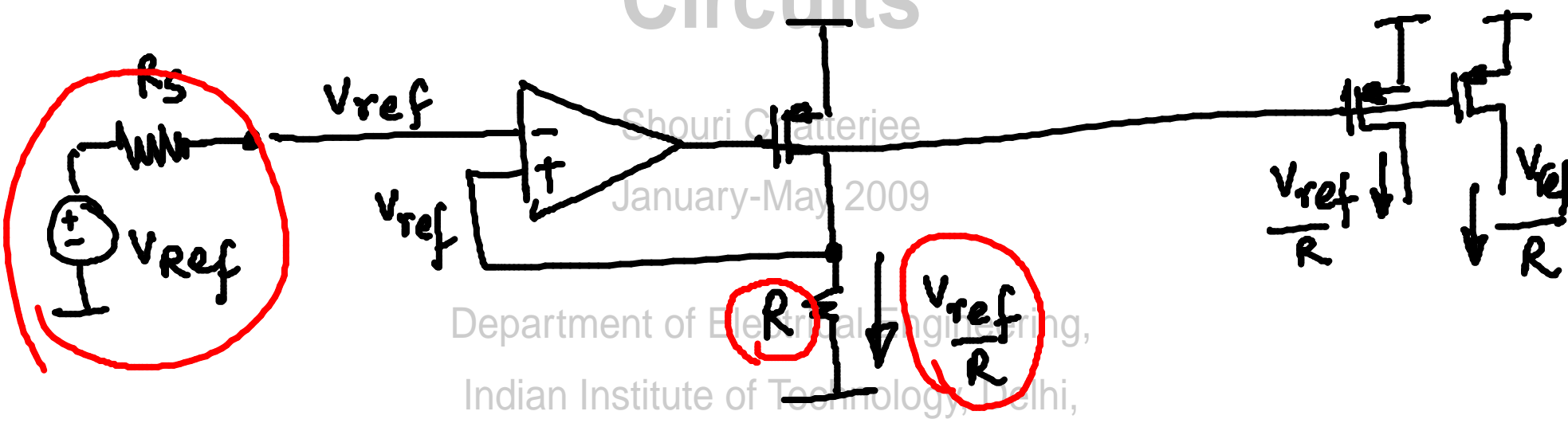


One current source of known value

→ temperature

→ power supply

→ process variations




Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016



1.12 eV

Bandgap Voltage Reference

BJT, EEL782: Analog Integrated Circuits

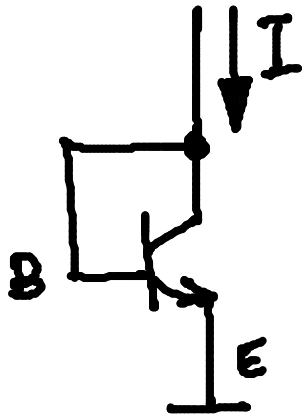

$$I_E = I_S \exp\left(\frac{V_{BE}}{\eta V_T}\right)$$

V_{BE} $f(T)$

$$\frac{\partial V_{BE}}{\partial T} = ?$$

$$I = I_S \exp\left(\frac{V_{BE}}{\eta V_T}\right)$$

$$V_{BE} = \eta V_T \ln\left(\frac{I}{I_S}\right)$$

$$\frac{\partial V_{BE}}{\partial T} = \eta \cdot \frac{k}{q} \ln\left(\frac{I}{I_S}\right) + \eta V_T \cdot \frac{I_S}{I} \cdot \left(-\frac{I}{I_S^2}\right) \cdot \frac{\partial I_S}{\partial T}$$

$$= \eta \cdot \frac{k}{q} \ln\left(\frac{I}{I_S}\right) - \eta \frac{V_T}{I_S} \cdot \frac{\partial I_S}{\partial T}$$

$$I_s = bT^{4+m} \exp(-E_g/kT)$$

$$\frac{\partial I_s}{\partial T} = b(4+m)T^{3+m} \exp(-E_g/kT)$$

$$+ bT^{4+m} \exp(-E_g/kT) \cdot \left(+ \frac{E_g}{kT^2} \right)$$

$$= \frac{(4+m)I_s}{T} + \left(\frac{E_g}{kT^2} \right) I_s$$

$$\frac{\partial V_{BE}}{\partial T} = \eta \cdot \left(\frac{k}{q} \right) \ln\left(\frac{I}{I_s}\right) - \eta V_T \left\{ \frac{4+m}{T} + \frac{E_g}{kT^2} \right\}$$

$$= \frac{V_{BE}}{T} - \eta \frac{k}{q} \left\{ 4+m + \frac{E_g}{kT} \right\} = \frac{\eta k}{q} \left[\ln\left(\frac{I}{I_s}\right) \right]$$

1.5
44.8

$$\eta \frac{kT}{q} \cdot \ln\left(\frac{I}{I_s}\right) = 0.6 \text{ V}$$

50




EEL 782: Analog Integrated Circuits

Shourri Chatterjee
January-May 2009

Department of Electrical Engineering,
Indian Institute of Technology, Delhi,

Hauz Khas, New Delhi 110016

$T \uparrow$ $V_{BE} \downarrow$

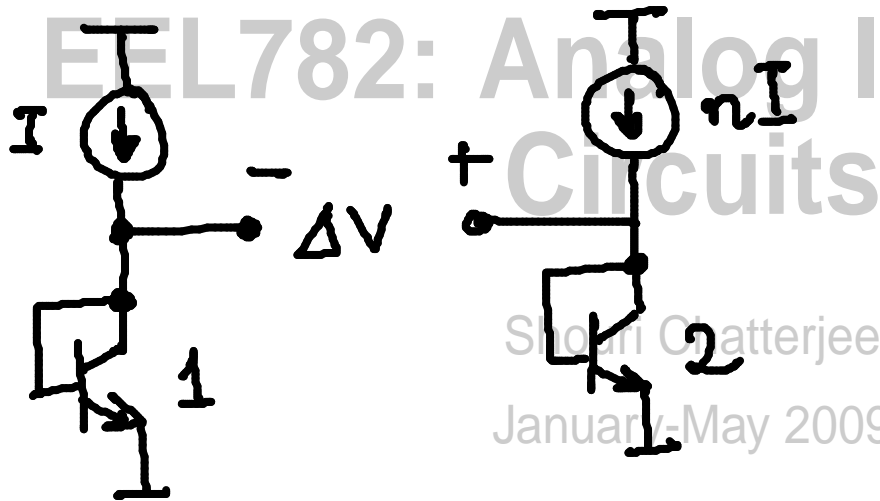


$$V_{BE_1} = \eta V_T \ln\left(\frac{I}{I_S}\right)$$

$$V_{BE_2} = \eta V_T \ln\left(\frac{nI}{I_S}\right)$$

$$\Delta V = V_{BE_2} - V_{BE_1} = \eta V_T \ln(n)$$
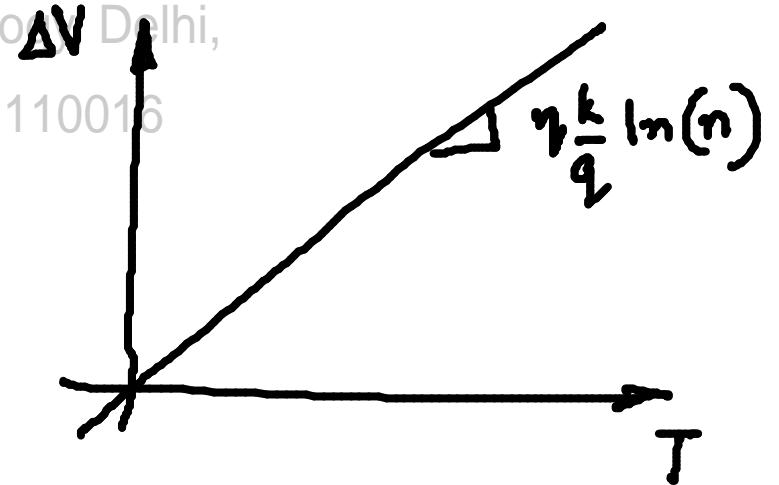
$$\frac{\partial \Delta V}{\partial T} = \eta \frac{k}{q} \ln(n)$$




PTAT



Shashi Chatterjee
January-May 2009

Department of Electrical Engineering,
Indian Institute of Technology Delhi,
Hauz Khas, New Delhi 110016

EEL782: Analog Integrated Circuits

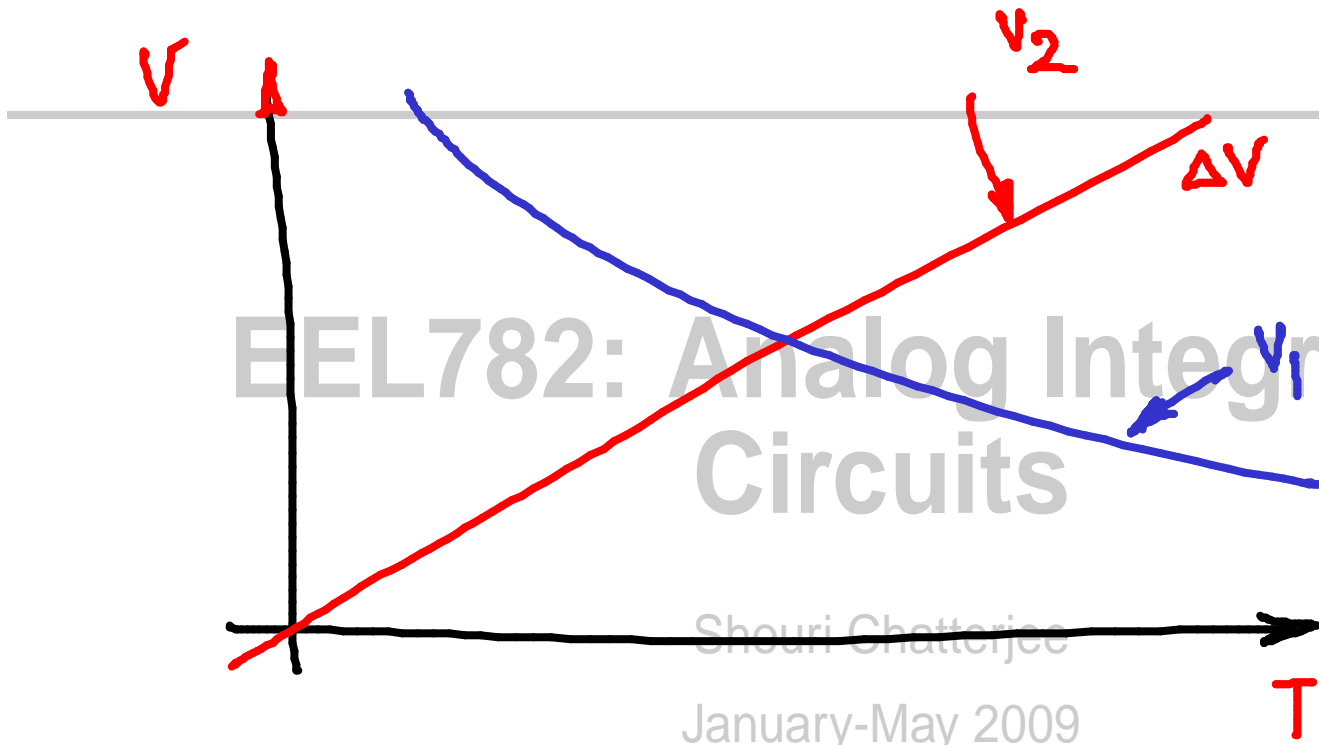

EEL782: Analog Integrated Circuits

Shouri Chatterjee
January-May 2009

$$V_{ref} = \alpha V_1 + \beta V_2$$

$$\frac{\partial V_{ref}}{\partial T} = \alpha \frac{\partial V_1}{\partial T} + \beta \frac{\partial V_2}{\partial T}$$

Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016

