


EEL782: Analog Integrated Circuits

(A) $v_x^- = \frac{v_{out}^+}{2}$

(B) $v_x^+ = \frac{v_{out}^-}{2}$


(1) $v_{out}^+ - v_{out}^- = 2(v_x^- - v_x^+)$

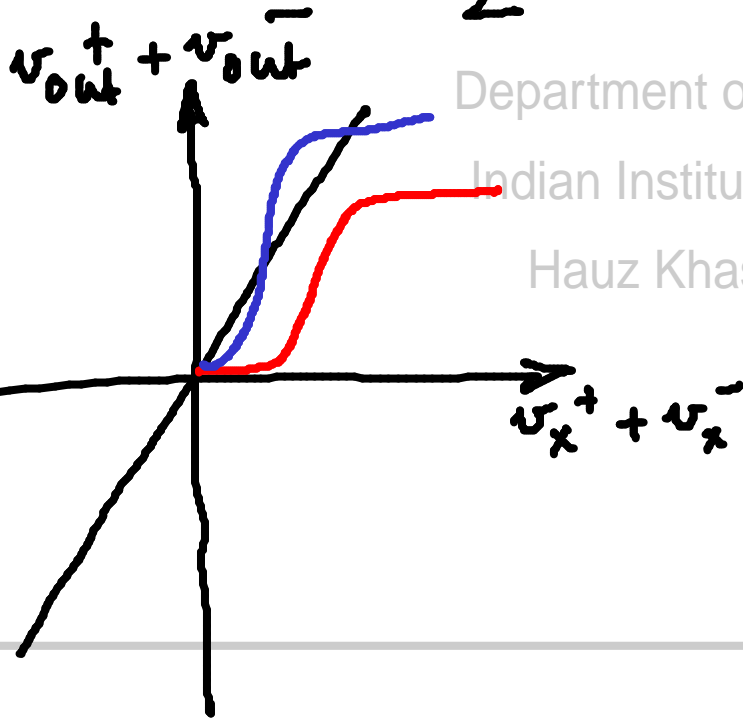(2) $v_{out}^+ + v_{out}^- = 2(v_x^- + v_x^+)$




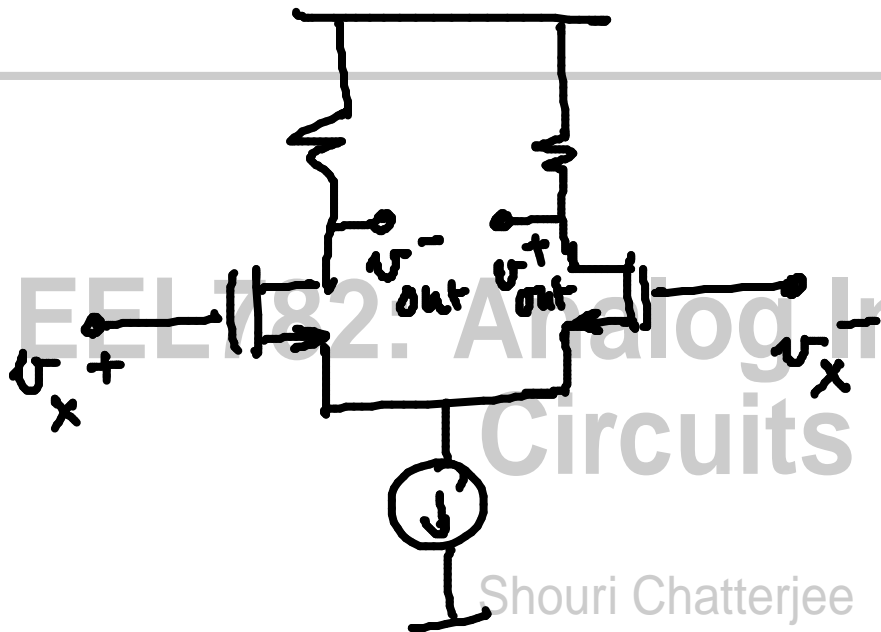Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016






Shouri Chatterjee
January-May 2009

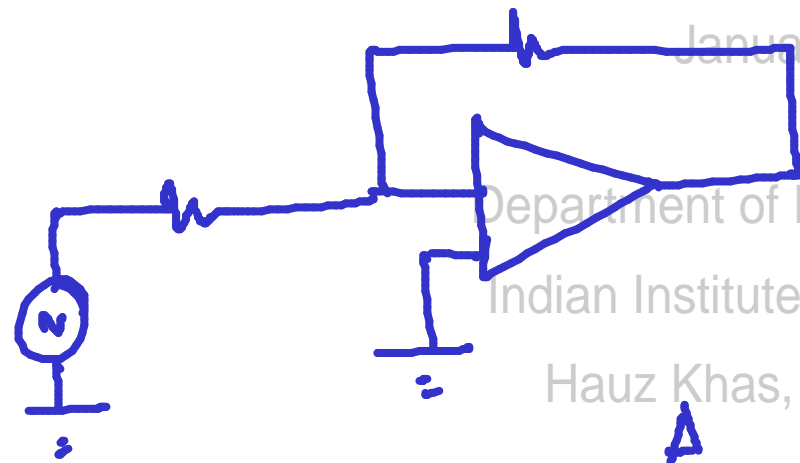

$$\frac{A}{(1 + s/\omega_1)(1 + s/\omega_2)(1 + s/\omega_3)}$$

$$1 + \frac{A}{C} = \frac{A}{(C) + A}$$

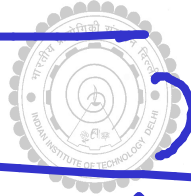

$$\frac{v_{out}^+ + v_{out}^-}{v_x^+ + v_x^-}$$

$$\frac{v_{out}^+ - v_{out}^-}{v_x^+ - v_x^-}$$

$$\frac{v_{out}^+ - v_{out}^-}{v_x^+ + v_x^-}$$

$$\frac{v_{out}^+ + v_{out}^-}{v_x^+ - v_x^-}$$

EEL782: Analog Integrated Circuits

Shouri Chatterjee

January-May 2009

Department of Electrical Engineering

Indian Institute of Technology, Delhi,

Hauz Khas, New Delhi 110016

