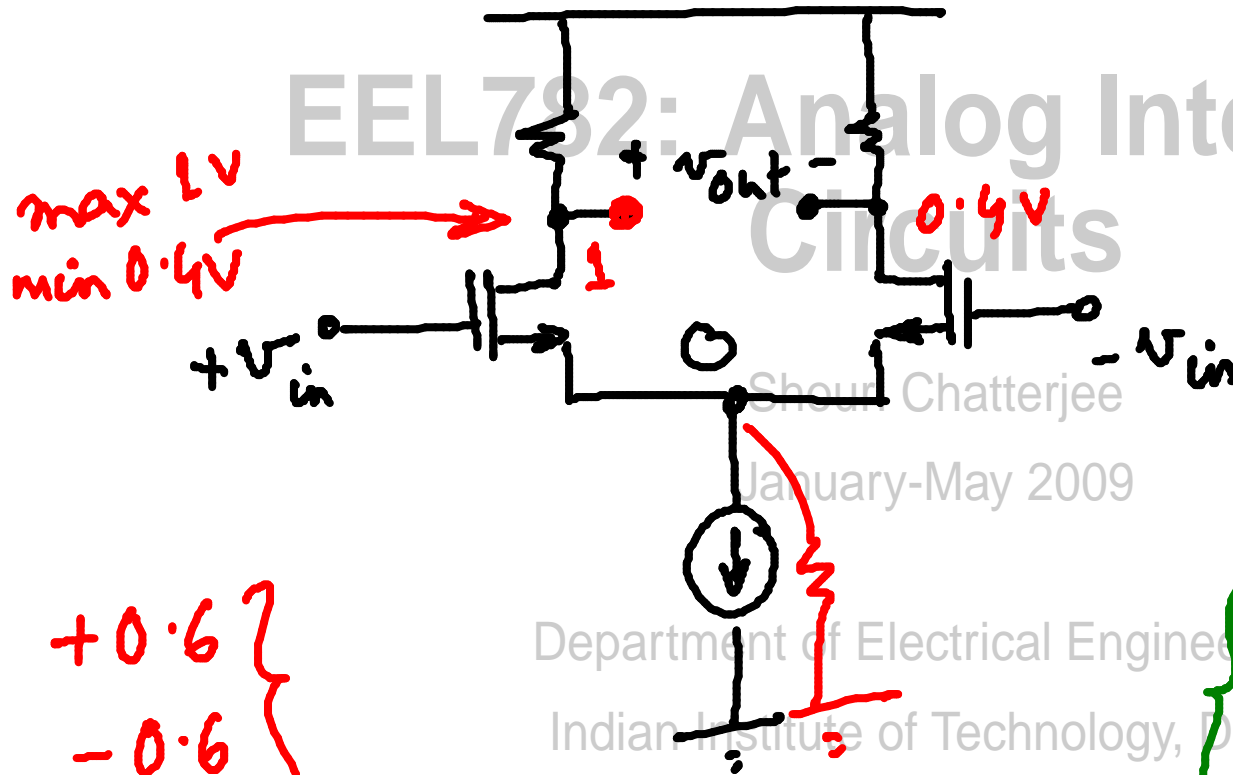


# Differential amplifier



EEL782: Analog Integrated Circuits

Show Chatterjee  
January-May 2009


Department of Electrical Engineering,  
Indian Institute of Technology, Delhi,  
Hauz Khas, New Delhi 110016



Why?

1. More immune to interference.
2. Swing is 2x
3. Power is 2x
4. Only odd harmonics


# EEL782: Analog Integrated Circuits

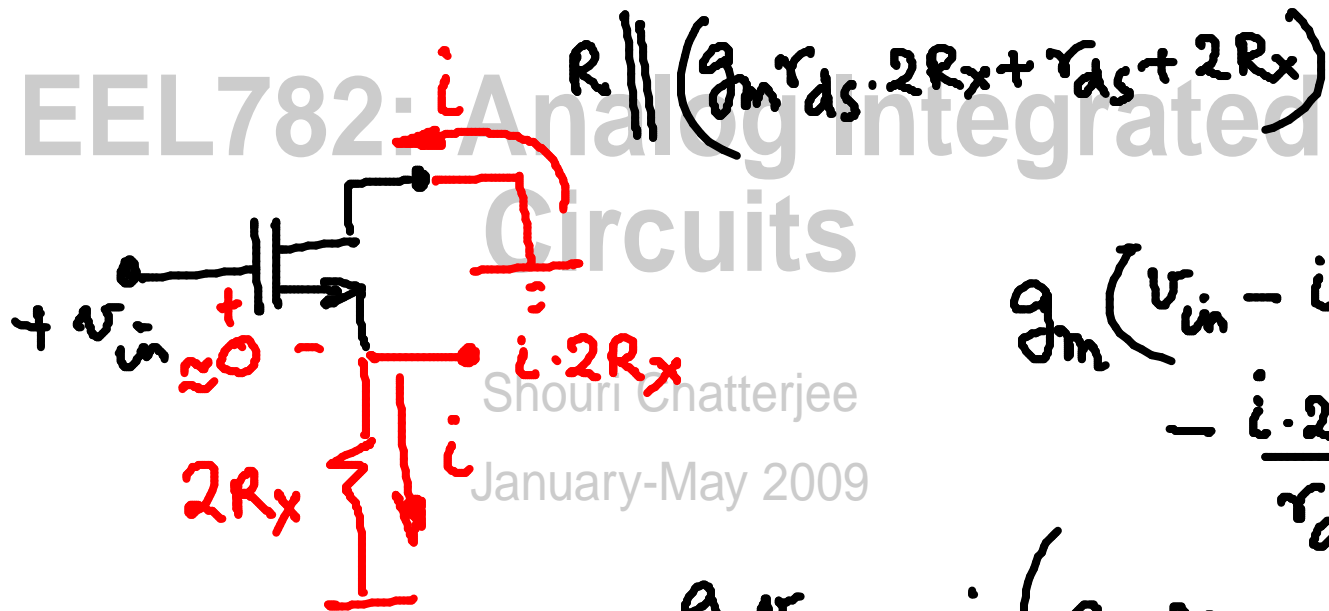

$$g_m (v_{in} - i \cdot 2R_x) - \frac{i \cdot 2R_x}{r_{ds}} = i$$


$$g_m v_{in} = i \left( g_m \cdot 2R_x + 1 + \frac{2R_x}{r_{ds}} \right)$$
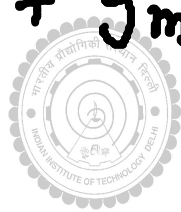
$$i = v_{in} \cdot \frac{g_m}{1 + 2R_x/r_{ds} + g_m \cdot 2R_x} \approx \frac{v_{in}}{2R_x}$$




Department of Electrical Engineering,  
 Indian Institute of Technology, Delhi,  
 Hauz Khas, New Delhi 110016

Shouri Chatterjee  
 January-May 2009

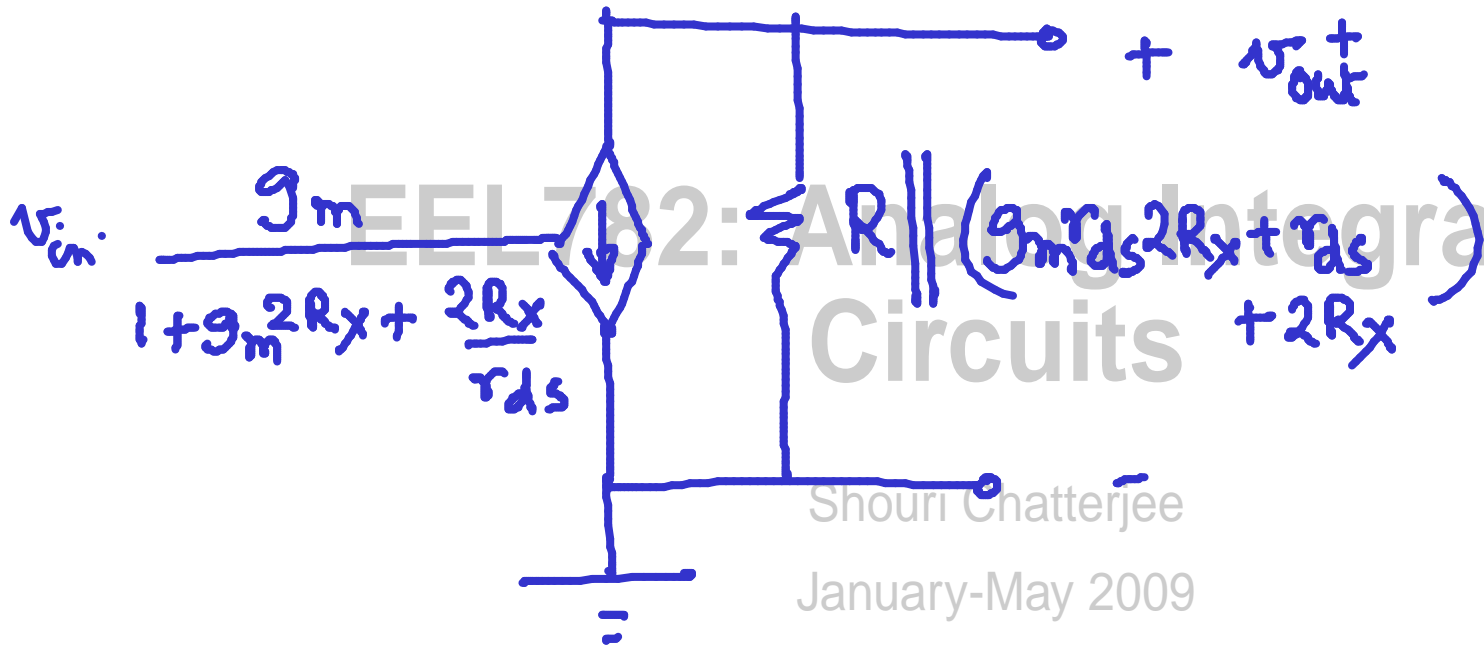

$$\text{Gain} = - \frac{g_m}{1 + \frac{2R_x}{r_{ds}} + 2g_m R_x} \cdot \frac{R \cdot r_{ds} \cdot \left(1 + \frac{2R_x}{r_{ds}} + g_m 2R_x\right)}{R + r_{ds} + 2R_x + g_m r_{ds} \cdot 2R_x}$$
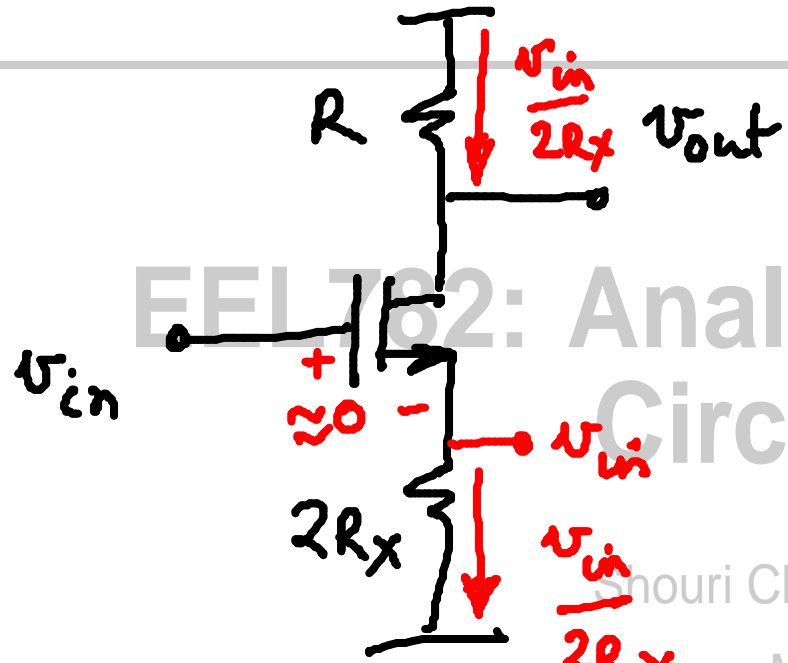
$$= - \frac{g_m \cdot R \cdot r_{ds}}{R + r_{ds} + 2R_x + g_m r_{ds} \cdot 2R_x} \approx - \frac{R}{2R_x}$$



$$v_{out} \approx -\frac{R}{2R_x} \cdot v_{in}$$

# EEL 782: Analog Integrated Circuits

Shouri Chatterjee  
January-May 2009


## Common-mode half circuit

Department of Electrical Engineering,  
Indian Institute of Technology, Delhi,  
Hauz Khas, New Delhi 110016



# EEL 782: Analog Integrated Circuits

Shouri Chatterjee  
January-May 2009

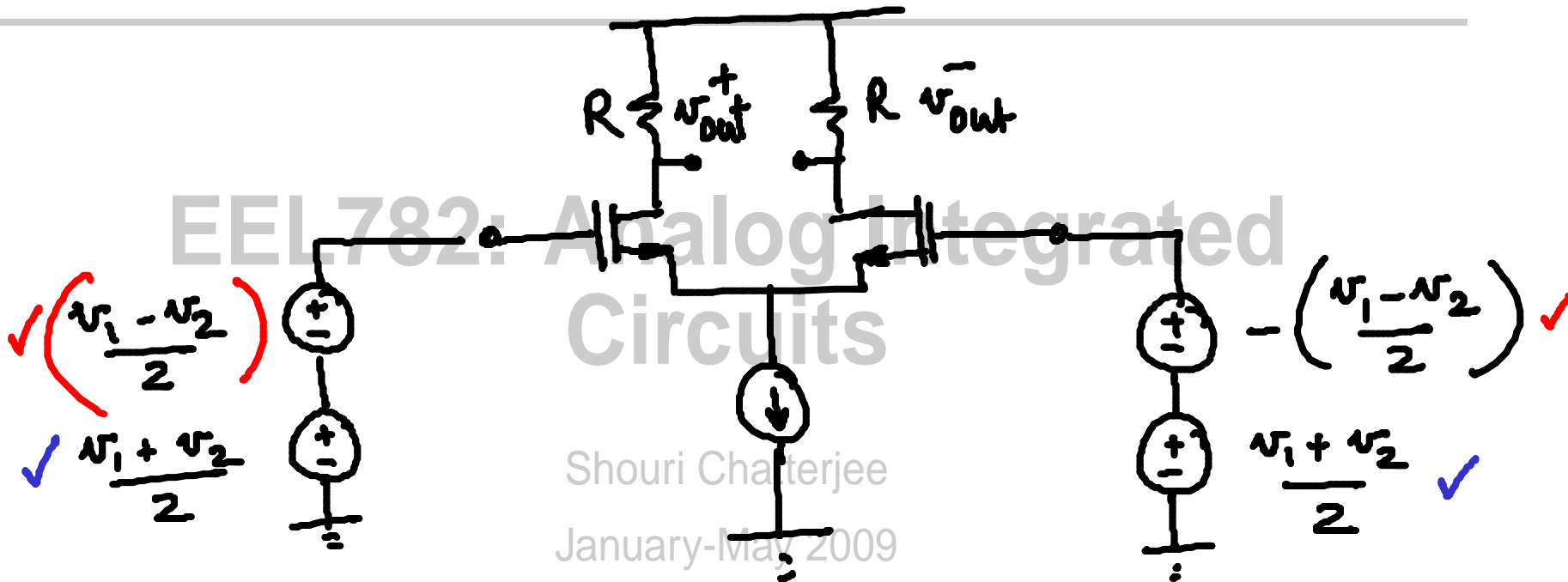

$$v_{out}^+ = -g_m(r_{ds} \parallel R) \left( \frac{v_1 - v_2}{2} \right)$$

$$v_{out}^- = +g_m \dots \dots \dots$$

$$v_{out}^+ - v_{out}^- = -g_m(r_{ds} \parallel R) (v_1 - v_2)$$



Department of Electrical Engineering,  
Indian Institute of Technology, Delhi,  
Hauz Khas, New Delhi 110016

$$1) \frac{v_{out}^+ - v_{out}^-}{v_1 - v_2}$$

$$v_1 + v_2 = 0$$

$$2) \frac{v_{out}^+ - v_{out}^-}{v_1 + v_2}$$

$$v_1 - v_2 = 0$$

$$3) \frac{v_{out}^+ + v_{out}^-}{v_1 - v_2}$$

$$v_1 + v_2 = 0$$

$$4) \frac{v_{out}^+ + v_{out}^-}{v_1 + v_2}$$

$$v_1 - v_2 = 0$$

# EEL782: Analog Integrated Circuits

Shouri Chatterjee

January-May 2009

Department of Electrical Engineering,

Indian Institute of Technology, Delhi,

Roza Khos, New Delhi 110016



---

# EEL782: Analog Integrated Circuits

Shouri Chatterjee

January-May 2009

Department of Electrical Engineering,  
Indian Institute of Technology, Delhi,  
Hauz Khas, New Delhi 110016

