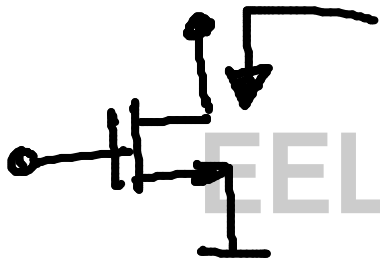


# Current sources



Sat  $I_D = f(V_{GS}, V_{DS})$


Lin  $I_D = f(V_{GS}, V_{DS})$

EEL782: Analog Integrated Circuits


Shouri Chatterjee

January-May 2009

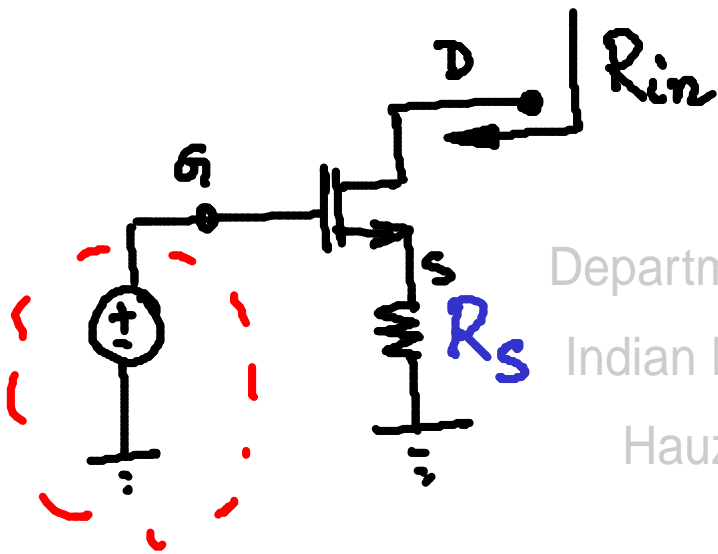Department of Electrical Engineering,  
Indian Institute of Technology, Delhi,  
Hauz Khas, New Delhi 110016



$$\frac{v - iR_s}{r_{ds}}$$

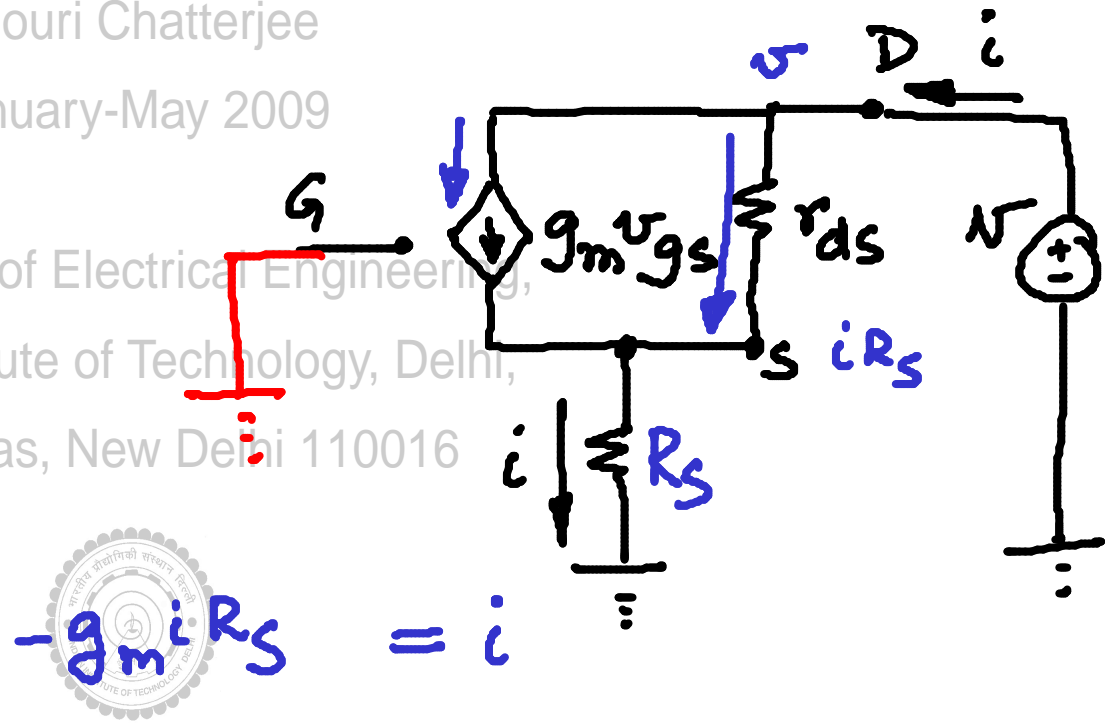


$$-g_m i R_s = i$$



$$\frac{v}{r_{ds}} = i \left( 1 + g_m R_s + R_s / r_{ds} \right)$$
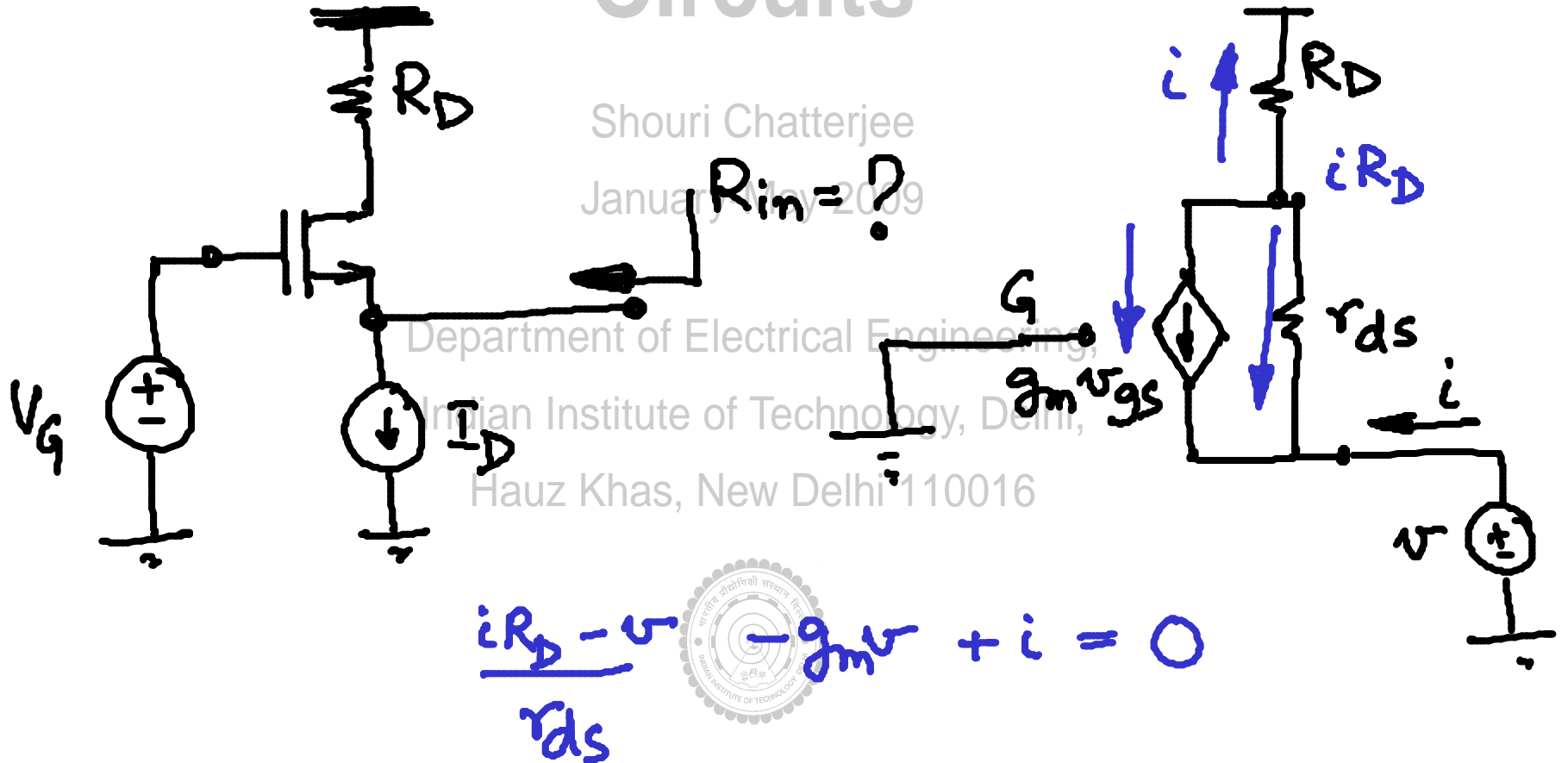
$$R_{in} = v/i = r_{ds} + R_s + g_m R_s r_{ds}$$



---

$$i \left( \frac{R_D}{r_{ds}} + 1 \right) = v \left( g_m + \frac{1}{r_{ds}} \right)$$



$$R_{in} = \frac{v}{i} = \frac{R_D + r_{ds}}{1 + g_m r_{ds}}$$

Shouri Chatterjee

January-May 2009

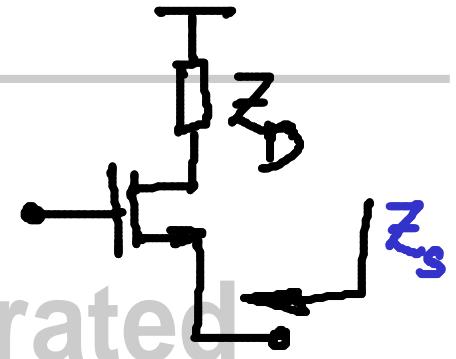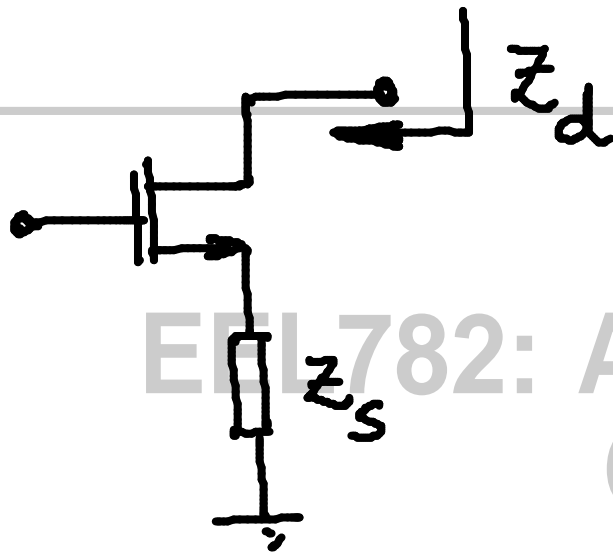Department of Electrical Engineering,  
Indian Institute of Technology, Delhi,  
Hauz Khas, New Delhi 110016





# EEL782: Analog Integrated Circuits

$$Z_s = \frac{r_{ds} + Z_D}{1 + g_m r_{ds}}$$

$$Z_d = r_{ds} + Z_s + g_m r_{ds} Z_s$$


if  $|Z_s| \gg r_{ds}$ ,  $Z_d \approx g_m r_{ds} Z_s$

Look in from drain  
 → Large impedance

Look in from source

→ Small impedance



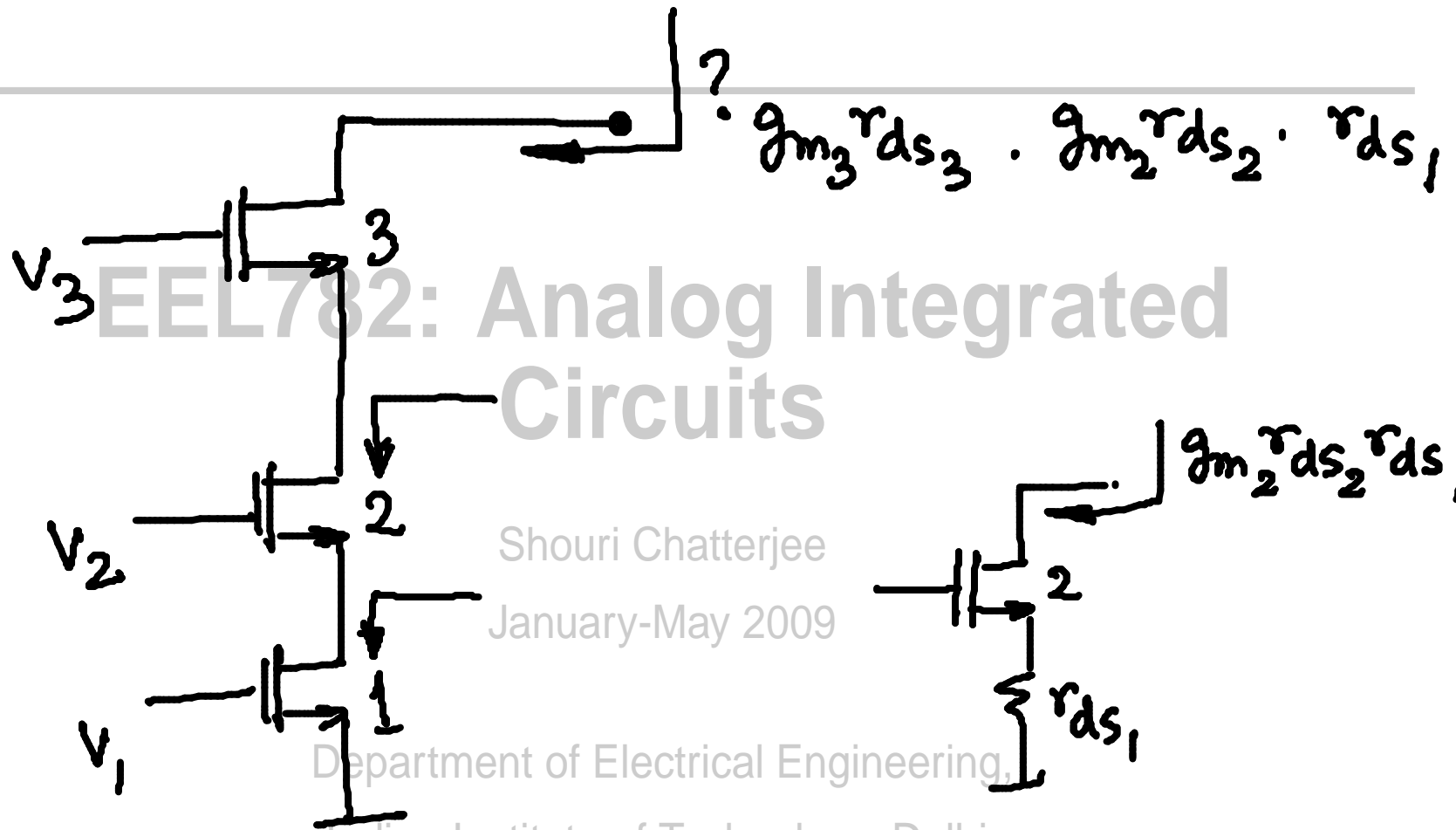

# EEL782: Analog Integrated Circuits

Shouri Chatterjee  
January-May 2009

Department of Electrical Engineering,  
Indian Institute of Technology, Delhi,  
Hauz Khas, New Delhi 110016

