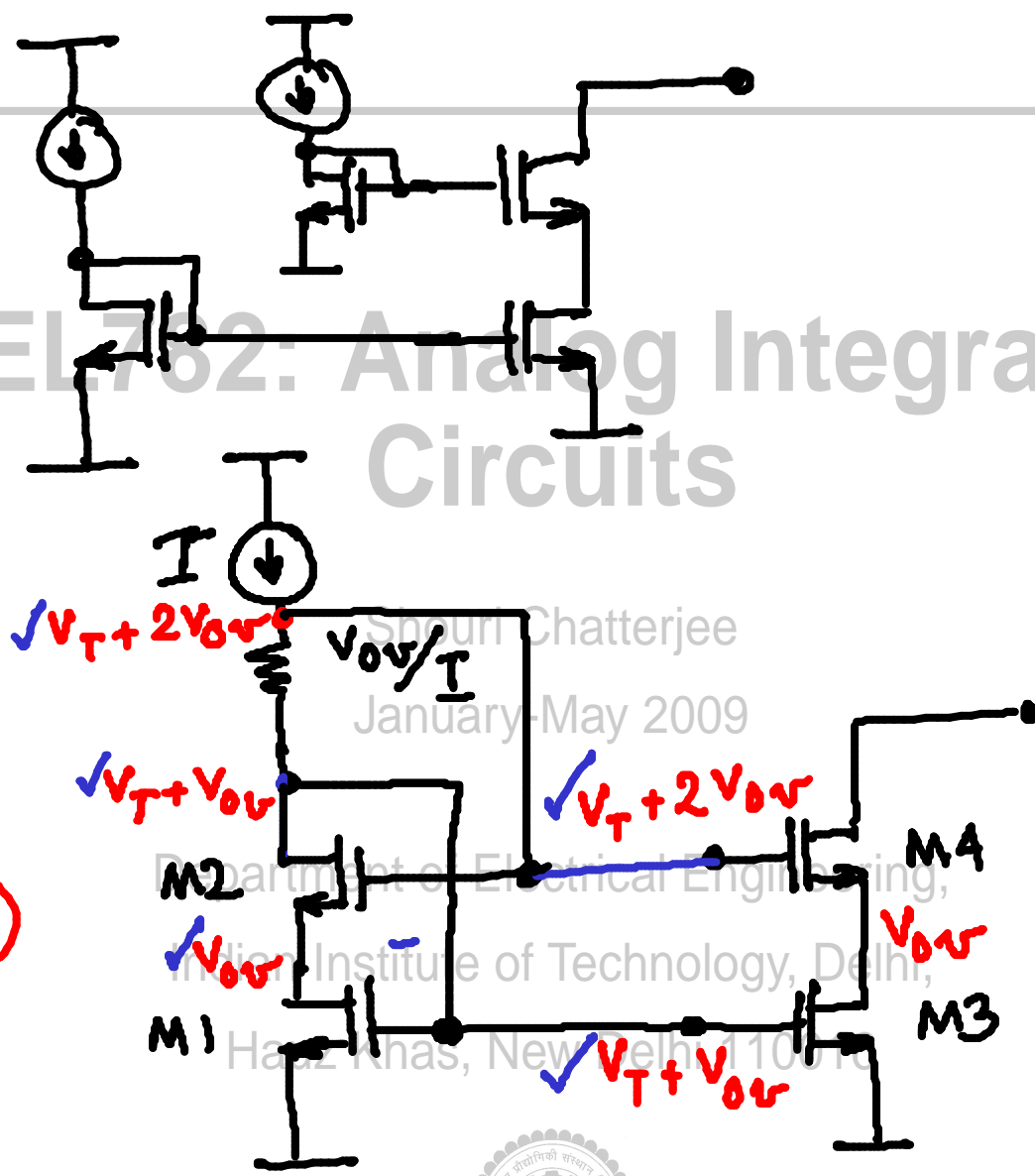


EEL762: Analog Integrated Circuits



$$\sqrt{V_T + 2V_{OV}}$$

$$\sqrt{V_T + V_{OV}}$$

$$\sqrt{V_T + 2V_{OV}}$$

$$V_{OV}$$

$$\sqrt{V_T + V_{OV}}$$


$$(V_T > V_{OV})$$



Shouni Chatterjee
January-May 2009
Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016

Common source

EEL782: Analog Integrated Circuits

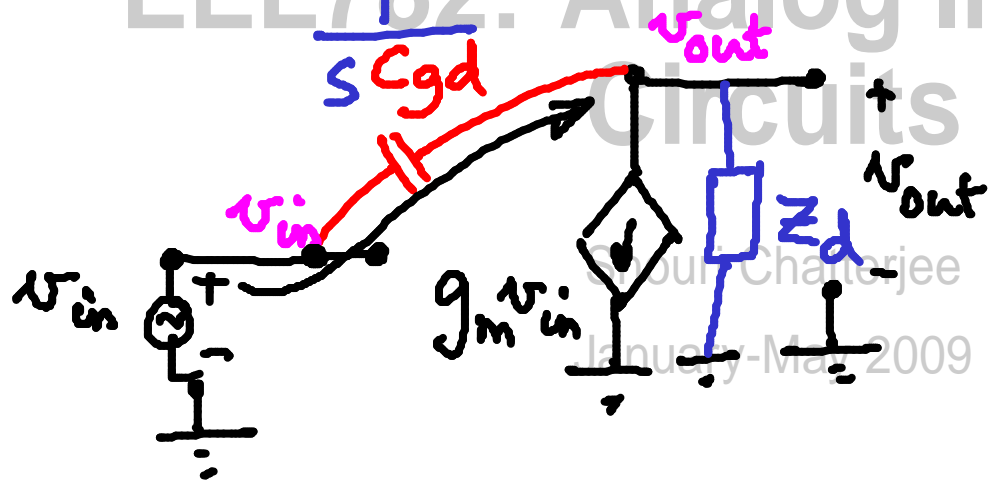

$$v_{out} = -g_m v_{in} r_{ds}$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m r_{ds}$$

Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016


$$Z_d = \frac{r_{ds}}{sC_{db} + \frac{1}{r_{ds}}} = \frac{r_{ds}}{1 + sC_{db}r_{ds}}$$

$$1 + s r_{ds} (C_{db} + C_{gd})$$

$$\frac{v_{out}}{Z_d} + v_{out} s C_{gd} = -g_m v_{in} + v_{in} s C_{gd}$$

$$\frac{v_{out}}{v_{in}} = \frac{-g_m + s C_{gd}}{1/Z_d + s C_{gd}}$$



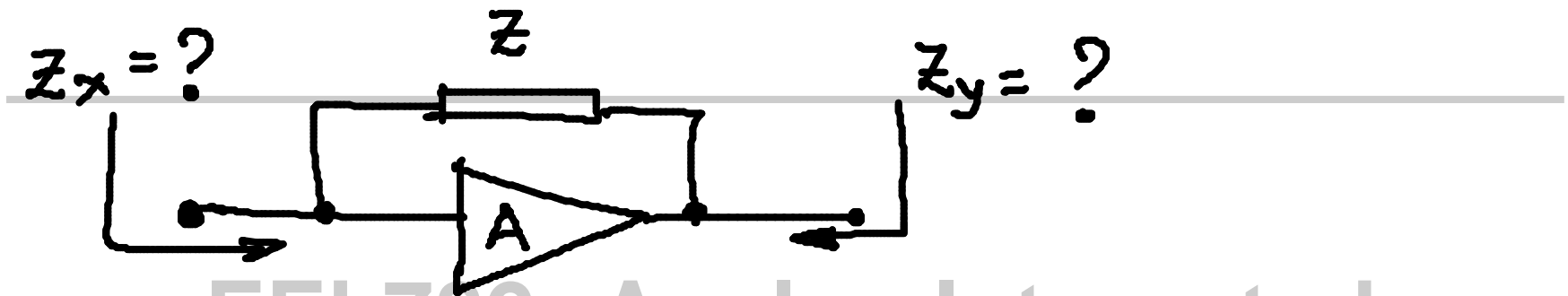


EEL782: Analog Integrated Circuits

$$Z_x = \frac{Z}{(1-A)}$$

$$Z_y = \frac{Z}{(1-1/A)}$$

Shouri Chatterjee

January-May 2009

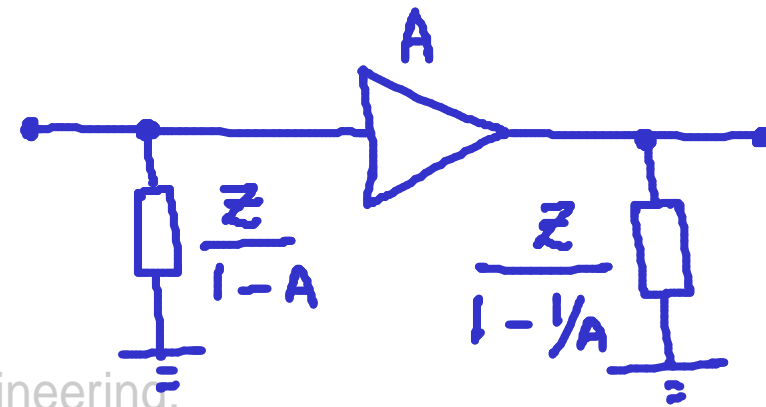


Department of Electrical Engineering,


Indian Institute of Technology, Delhi,

Hauz Khas, New Delhi 110016



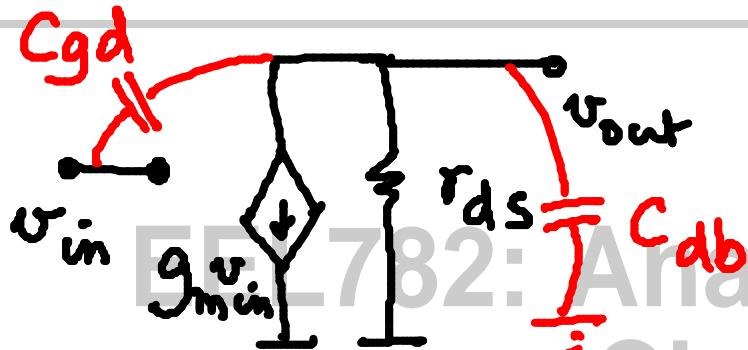

$$\frac{v_{out}}{v_{in}} = -g_m r_{ds}$$

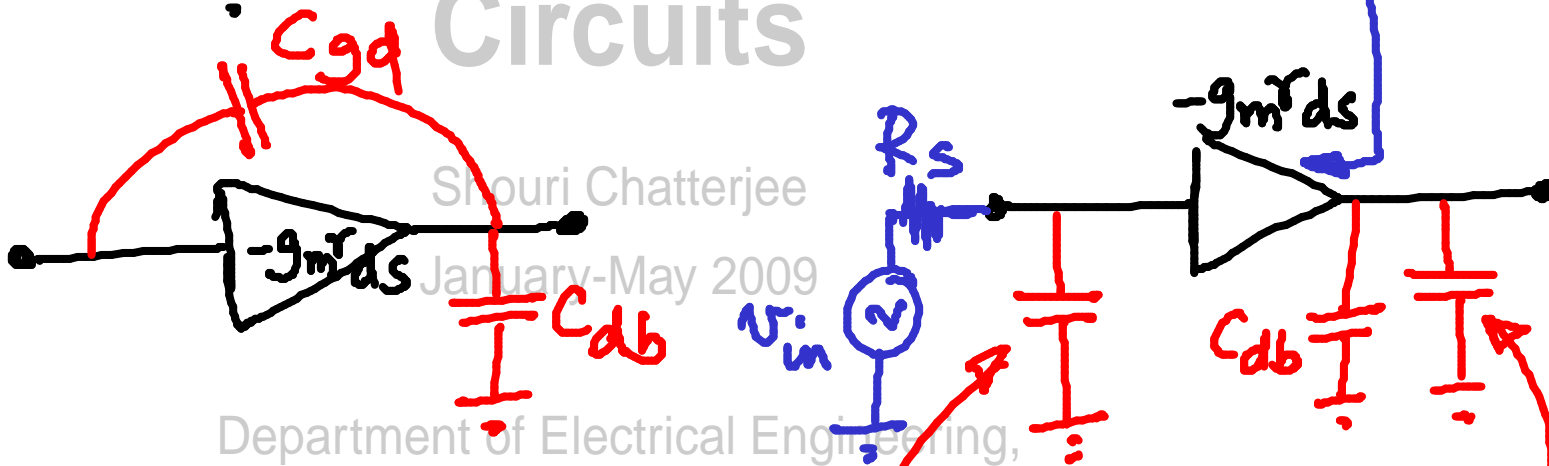

$$C_{gd}(1 + g_m r_{ds})$$


$$C_{gd} \times \left(1 + \frac{1}{g_m r_{ds}}\right)$$

....

$$1 + s r_{ds} \left(C_{db} + \left(1 + \frac{1}{g_m r_{ds}}\right) C_{gd} \right)$$



Sriouri Chatterjee
 January-May 2009
 Department of Electrical Engineering,
 Indian Institute of Technology, Delhi,
 Hauz Khas, New Delhi 110016

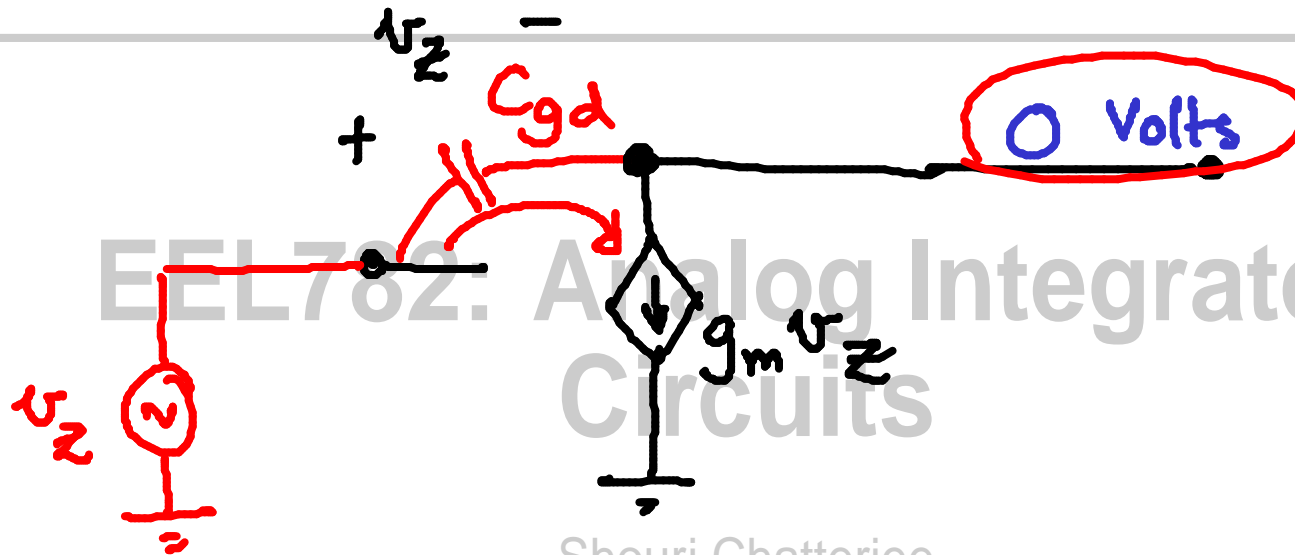

EEL782: Analog Integrated Circuits

Shouri Chatterjee

January-May 2009


$$1 = \frac{1}{s C_{gd}} \cdot g_m$$

$$s_z = g_m / C_{gd}$$

Department of Electrical Engineering,
 Indian Institute of Technology, Delhi,
 Hauz Khas, New Delhi 110016



Common gate

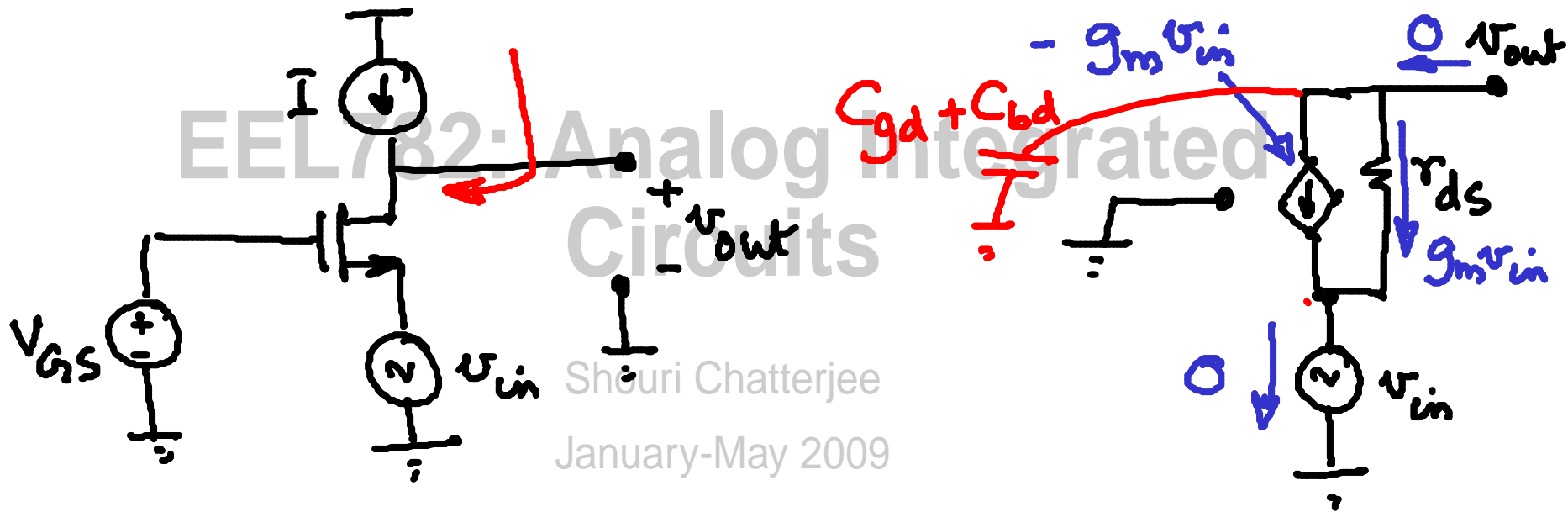

$$v_{out} = v_{in} (1 + g_m r_{ds})$$

$$\frac{v_{out}}{v_{in}} = 1 + g_m r_{ds}$$

Pole at : $\frac{1}{r_{ds}(C_{gd} + C_{bd})}$

$$\frac{v_{out}}{v_{in}} = (1 + g_m r_{ds}) \cdot \frac{1}{1 + s r_{ds}(C_{gd} + C_{bd})}$$

EEL 762: Analog Integrated Circuits



Shubri Chatterjee


January-May 2009

Department of Electrical Engineering

Indian Institute of Technology, Delhi,



Hauz Khas, New Delhi 110016

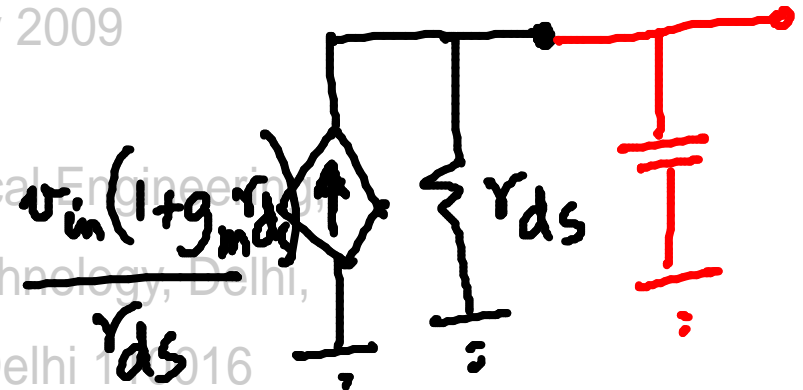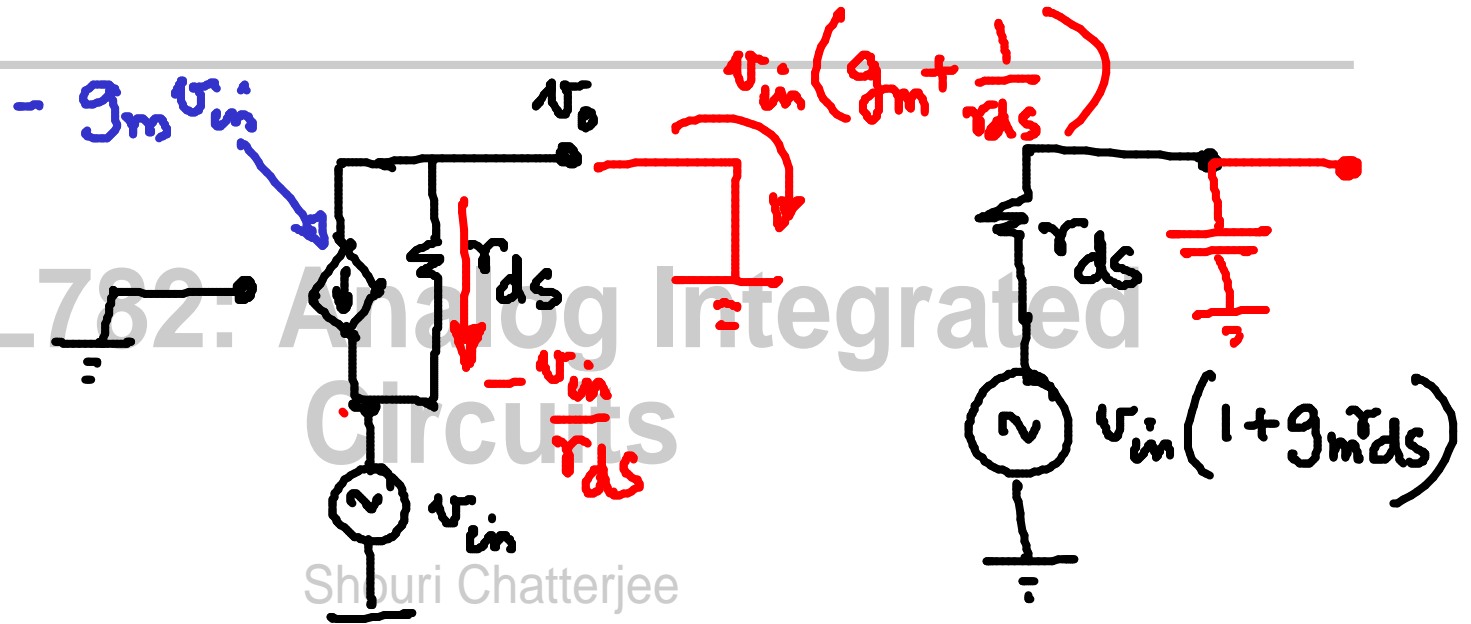

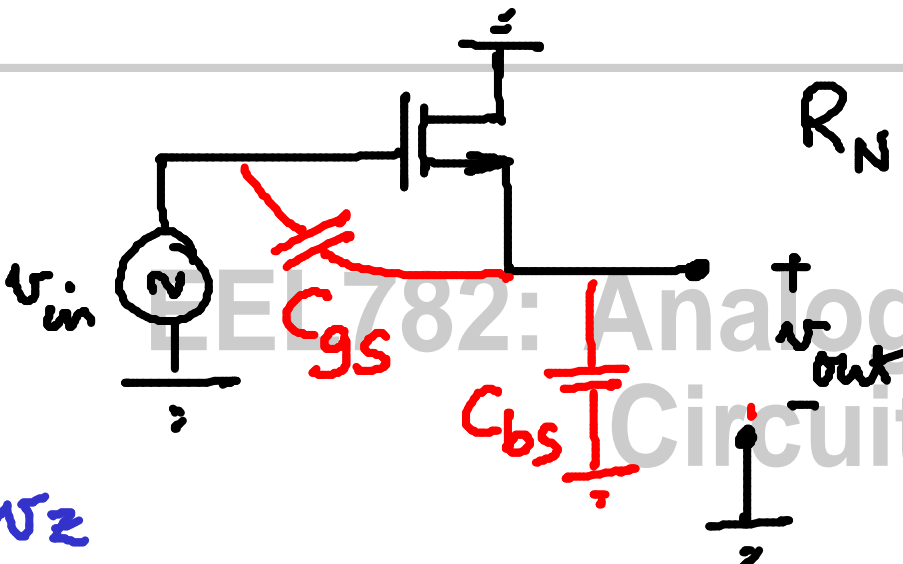

$$R_N = 1/g_m \parallel r_{ds}$$

$$I_N = g_m v_{in}$$

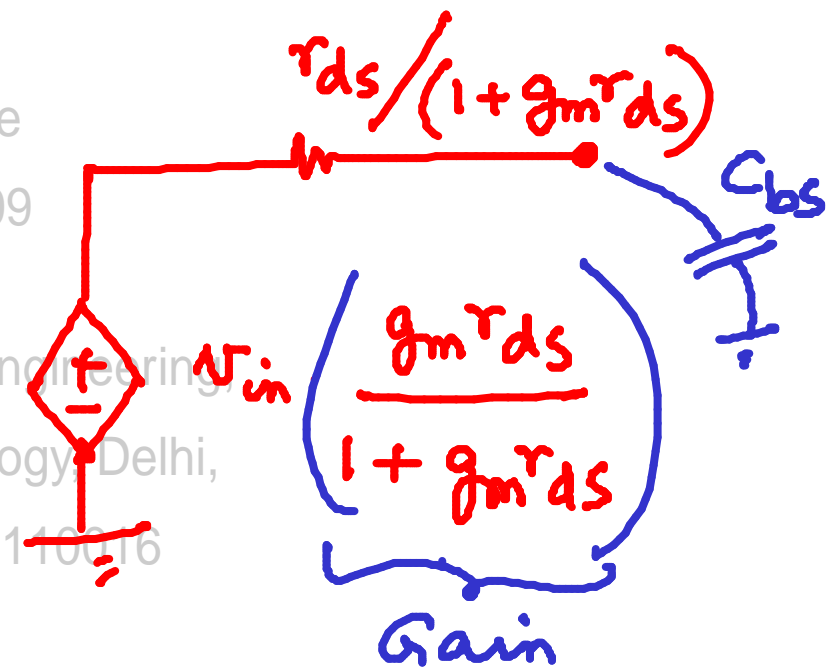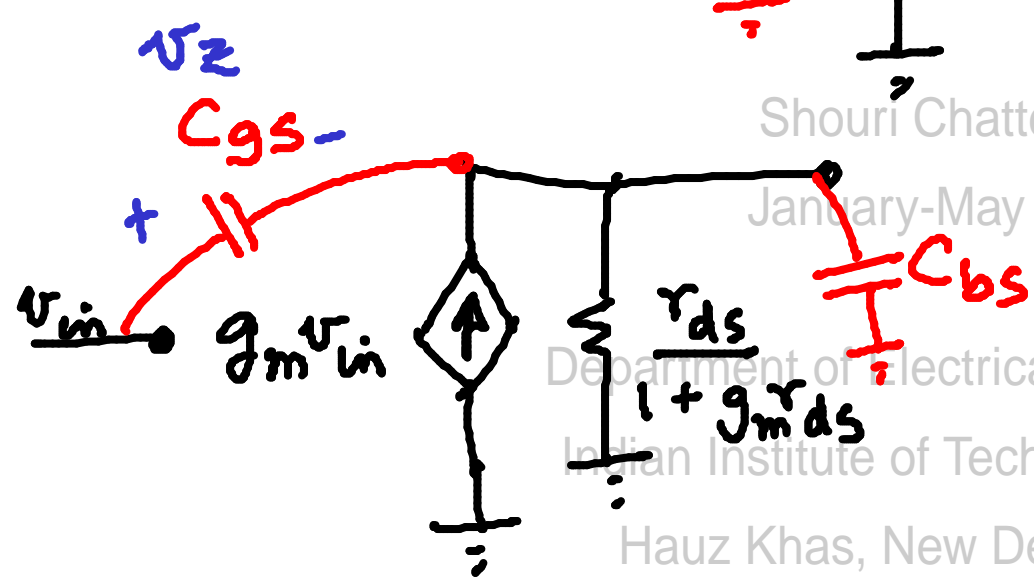

$$v_z \cdot s_z C_{gs} = -g_m v_z$$

$$s_z = -g_m / C_{gs}$$

EE782: Analog Integrated Circuits


Shouri Chatterjee
January-May 2009

Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016




$$s_{pole} = - \frac{1 + g_m r_{ds}}{(C_{gs} + C_{bs}) \cdot r_{ds}}$$
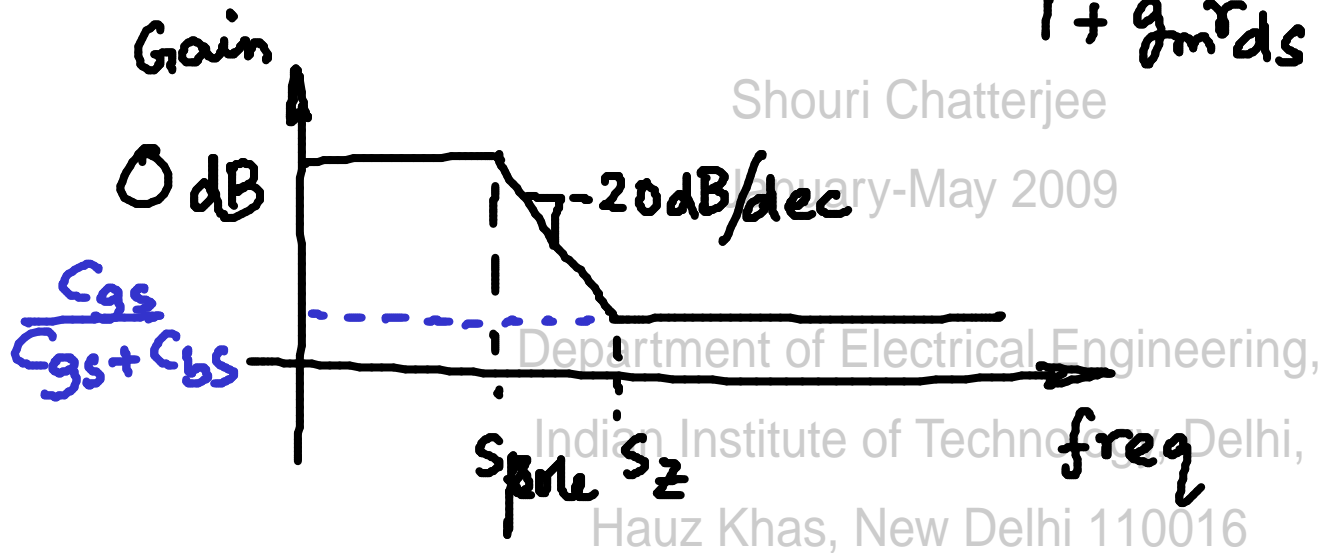
$$\frac{v_{out}}{v_{in}} = \left(\frac{g_m r_{ds}}{1 + g_m r_{ds}} \right) \left[\frac{1 + s C_{gs} / g_m}{1 + s (C_{gs} + C_{bs}) r_{ds}} \right] \underset{s \rightarrow \infty}{\approx} \frac{C_{gs}}{C_{gs} + C_{bs}}$$



Differential amplifier

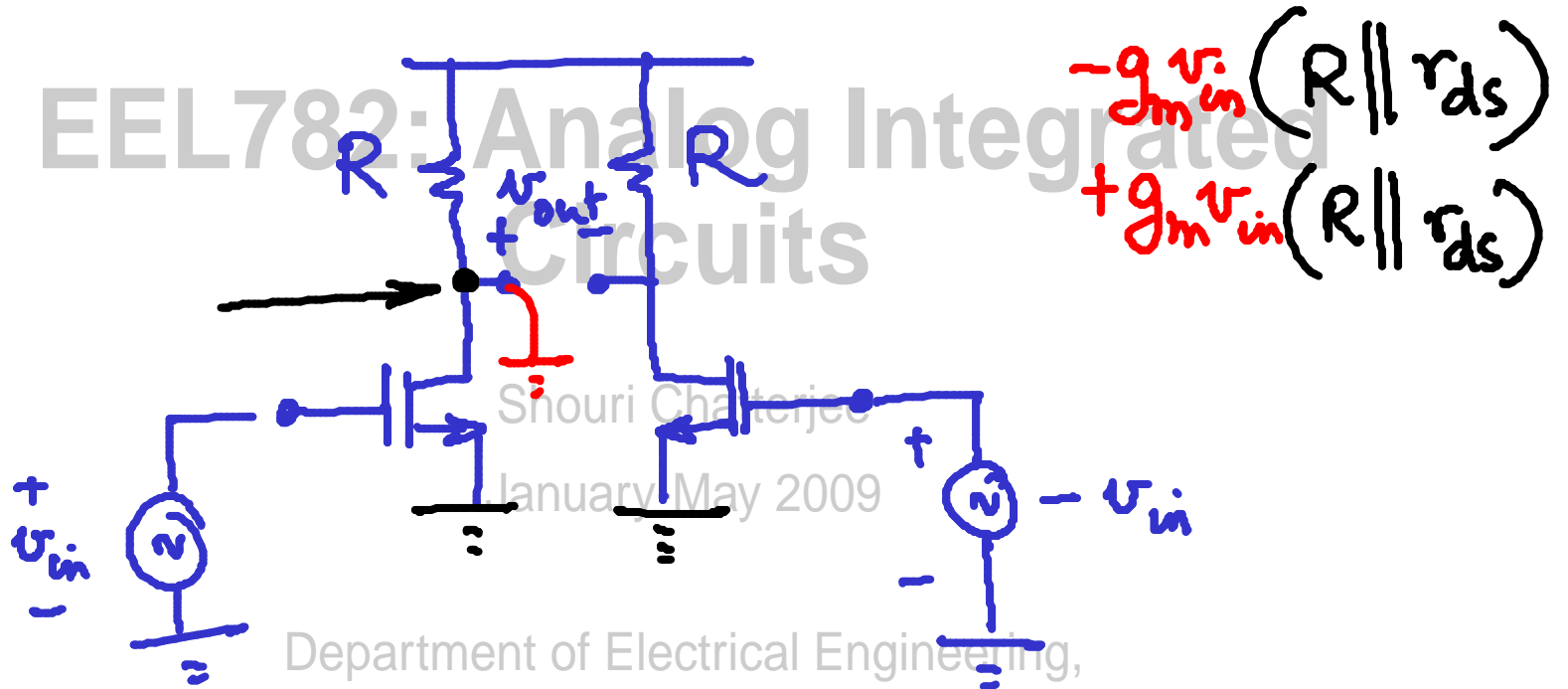

Department of Electrical Engineering,

Indian Institute of Technology, Delhi,



Hauz Khas, New Delhi 110016

$$v_{out} = -2g_m v_{in} (R \parallel r_{ds})$$



EEL 782: Analog Integrated Circuits

Shourya Chatterjee
January-May 2009

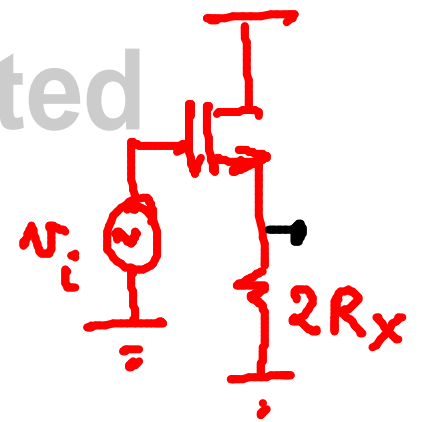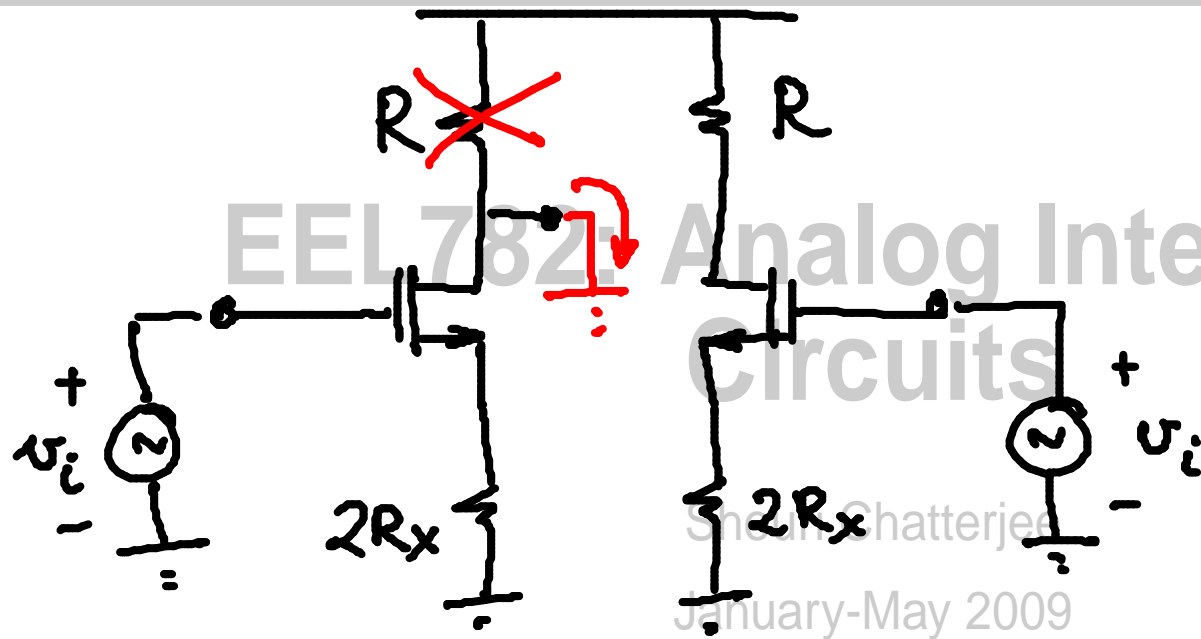

$$R \parallel (g_m r_{ds} 2R_x + r_{ds} + 2R_x)$$

Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016

