

EEL752: Analog Integrated Circuits

Shouri Chatterjee
January-May 2009

$P_1 \rightarrow$ Use Miller
 $P_2 \rightarrow 1/g_{m2}, C_x + C_y$

$$C_1 = \frac{g_{m1}}{g_{m2}} \cdot (C_x + C_y) \tan \phi$$

Zero at input node: g_{m1}/C_{gd1}
 Zero at int. node: g_{m2}/C_1



BAD NEWS! = $\frac{g_{m2}}{g_{m1} \tan \phi} \cdot \phi_2$

Department of Electrical Engineering,
 Indian Institute of Technology, Delhi,
 Hauz Khas, New Delhi 110016


Desired scenario


$$P_1 \ll P_2 \ll \overset{\times}{Z_1}, \overset{\checkmark}{Z_2}$$

EEL782: Analog Integrated Circuits

Shouri Chatterjee
January-May 2009

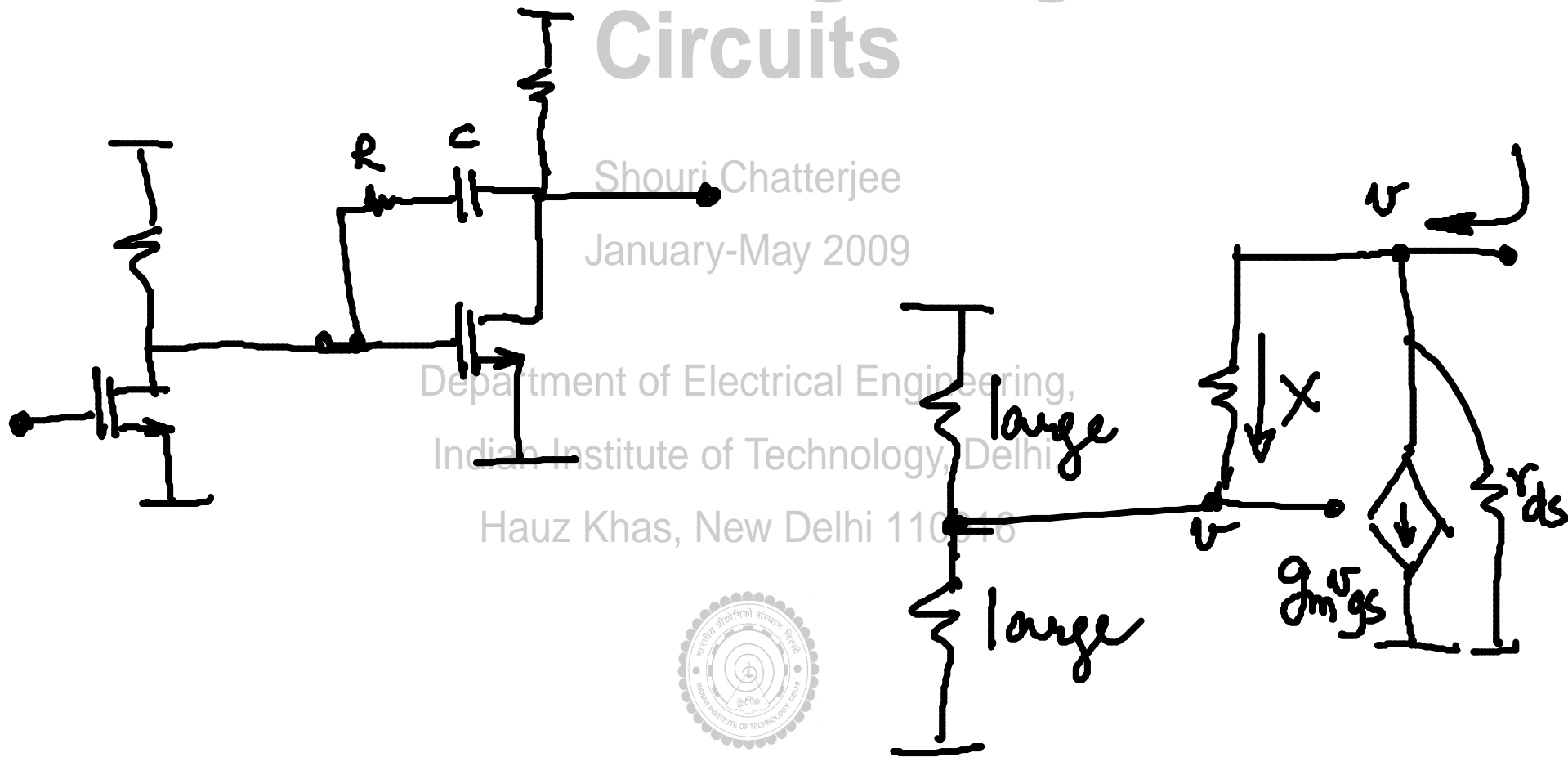Department of Electrical Engineering,
Indian Institute of Technology, Delhi
Hauz Khas, New Delhi 110016



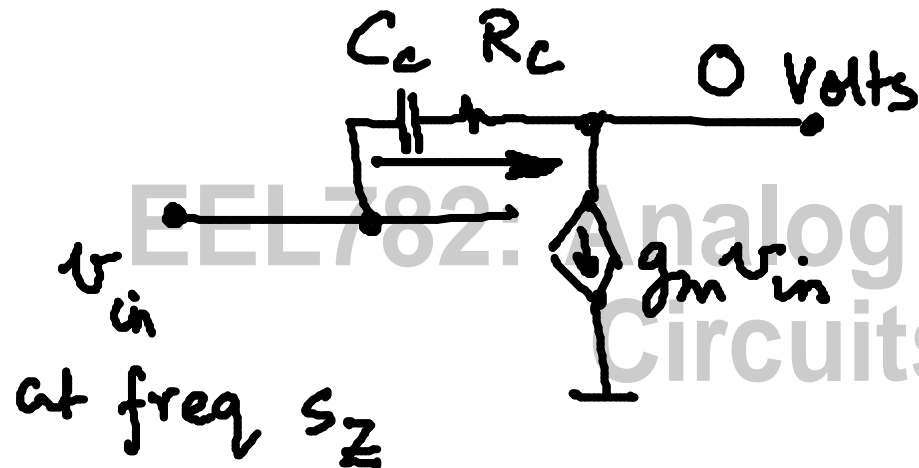

$$v_{in} = g_m v_{in} \left(R_C + \frac{1}{s_Z C_C} \right)$$

$$s_Z = \frac{1}{\left(\frac{1}{g_m} - R_C \right) C_C}$$

$R_C < \frac{1}{g_m}$ RHP zero

$R_C = \frac{1}{g_m} \rightarrow$ no zero

$R_C > \frac{1}{g_m} \rightarrow$ LHP zero





"bleed" current through M_3 .

EEL782: Analog Integrated Circuits

Shouri Chatterjee
January-May 2009

Department of Electrical Engineering,
Indian Institute of Technology, Delhi,
Hauz Khas, New Delhi 110016

Low freqs :
Two stages
High DC gain

High freqs :
One stage
low output R
low gain

