

# EEL782 : Solutions to final exam

## Objective type questions

1.  $g_m r_{ds} \approx 20$
2.  $C_{junction}$
3. 2
4. Area, perimeter
5. 
$$\left. \begin{array}{l} W \cdot L = 200 \\ 2(W+L) = 80 \end{array} \right\} \left[ \begin{array}{l} W + \frac{200}{W} = 40 \\ W^2 - 40W + 200 = 0 \end{array} \right] 34 \mu m \times 6 \mu m$$
6. 2.5 mV
7. Common centroid
8.  $V/\sqrt{Hz}$
9. False


10. True

11. Siemens, Ohms. Increase, increase

12. DC, even harmonics. Fundamental, odd harmonics.


### Regular questions

13

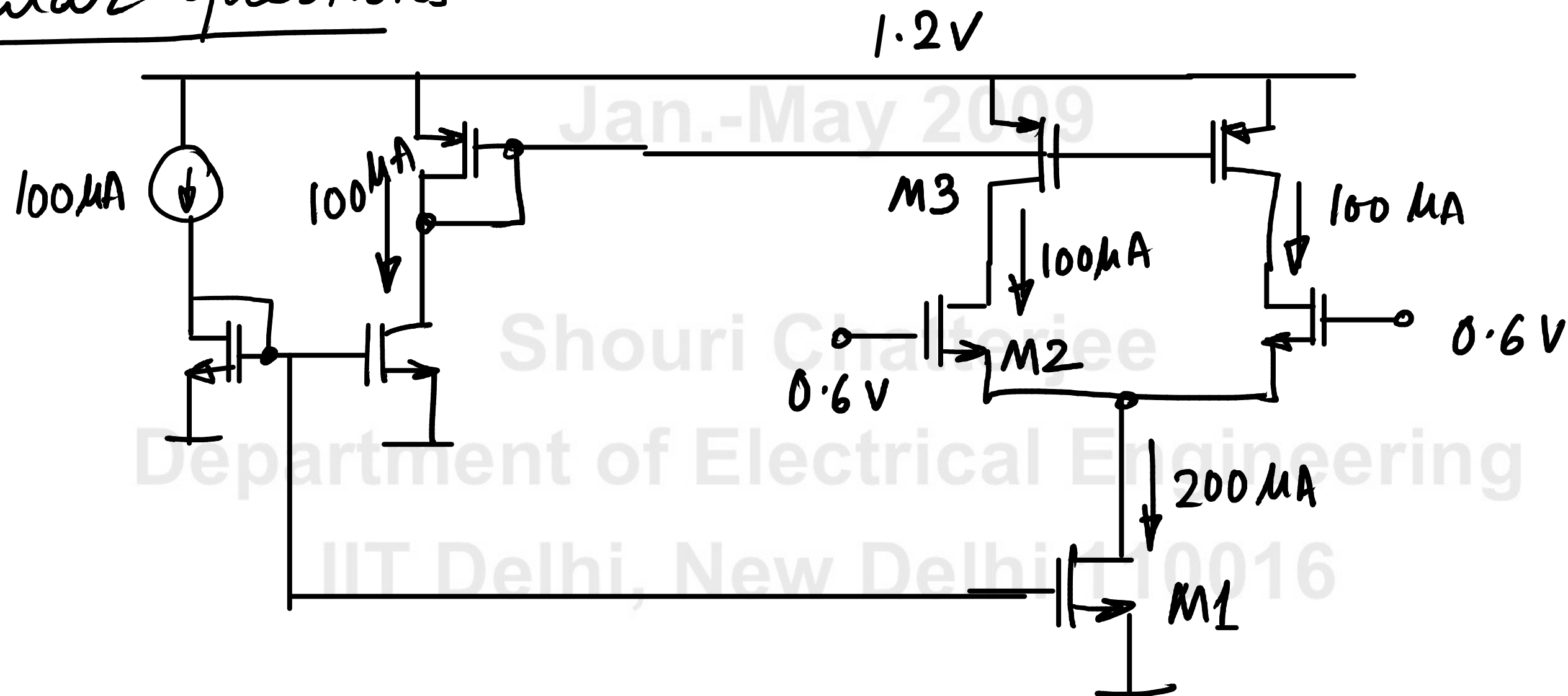

Step 1: recognised all the current mirrors.

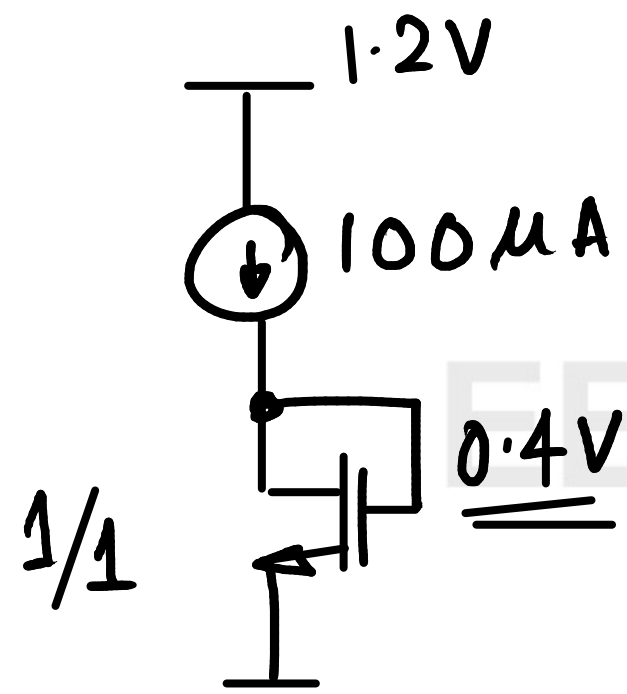M1 drawing 200µA ; M2 having 100µA ;  
M3, M4, M5




$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Assume the effect of  $1 + \lambda V_{DS}$  is small.

$$I_D \approx \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$100\mu = 10m \cdot 1 \cdot (V_{GS} - 0.3)^2$$

$$\therefore V_{GS} = 0.4V$$

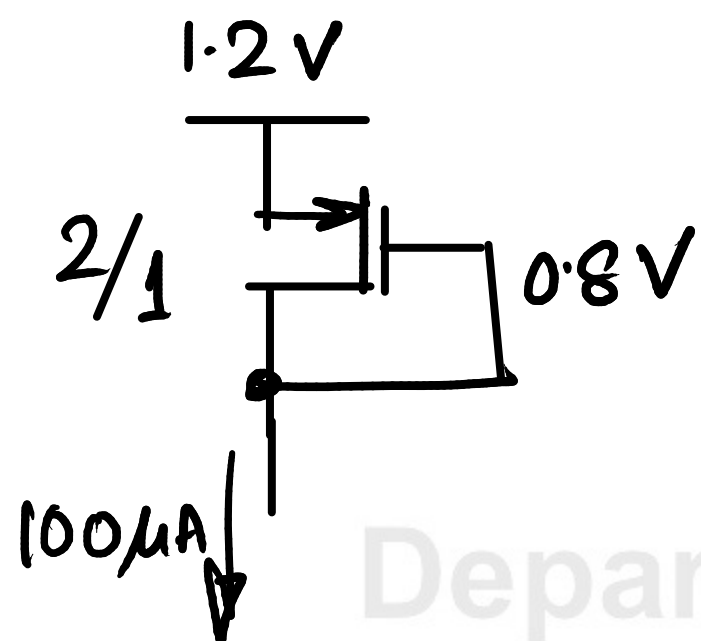

$$V_{SG} = 0.4V$$

Also, for MA,  $V_{SG}$  must be 0.4V for it to conduct  $100\mu A$ .



	$V_{GS}$	$V_{DS}$	$I_D$	$g_m$	$r_{ds}$
M1	0.4V	0.2V	200 $\mu$ A	4mS	10k $\Omega$
M2	0.4V	0.6V	100 $\mu$ A	2mS	20k $\Omega$
M3	-0.4V	-0.4V	100 $\mu$ A	2mS	20k $\Omega$
M4	-0.4V	-0.6V	100 $\mu$ A	2mS	20k $\Omega$
M5	0.4V	0.6V	100 $\mu$ A	2mS	20k $\Omega$


$$g_m = \frac{\partial I_D}{\partial V_{GS}} \approx \sqrt{4 \cdot \frac{\mu_{Cox}}{2} \cdot \frac{W}{L} \cdot I_D}$$

$$g_{ds} = \frac{\partial I_D}{\partial V_{DS}} \approx \lambda \cdot I_D$$

$$r_{ds} = \frac{1}{\lambda I_D}$$

14

# Small signal differential half-circuit

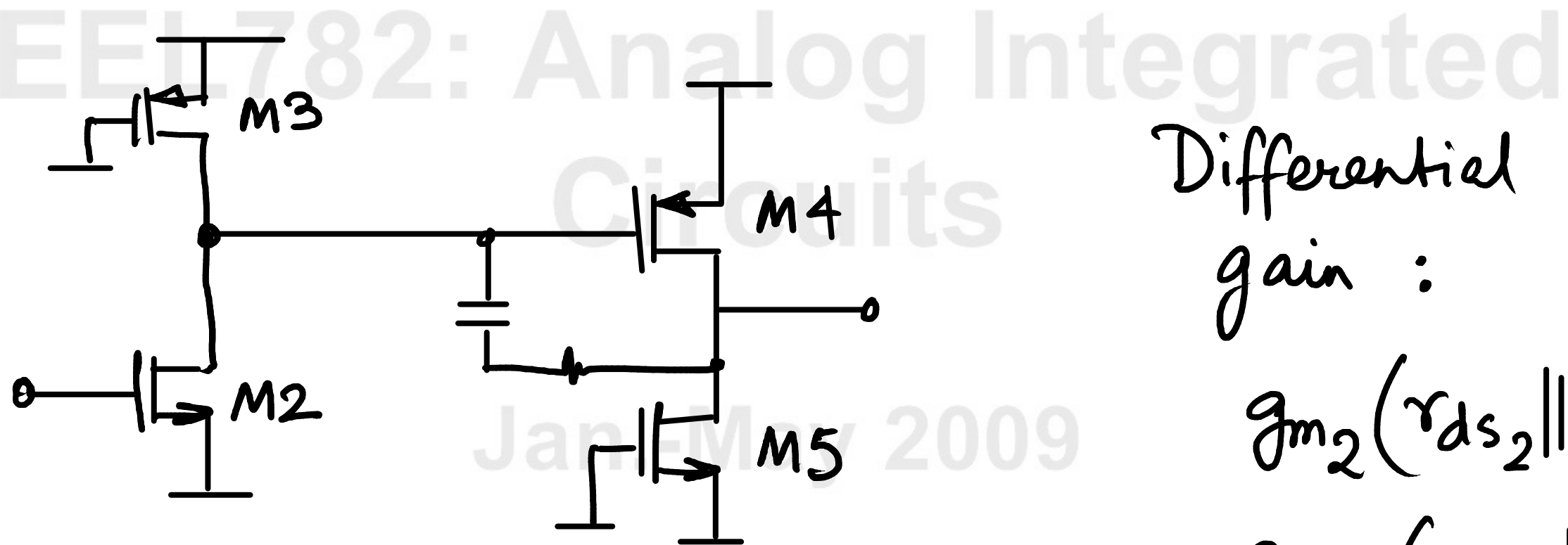

Differential mode gain :

$$g_{m2} (r_{ds2} \parallel r_{ds3}) \times g_{m4} (r_{ds4} \parallel r_{ds5})$$

$$= 2\text{mS} \cdot (20\text{k} \parallel 20\text{k}) \cdot 2\text{mS} \cdot (20\text{k} \parallel 20\text{k})$$


$$= 400$$

Shouri Chatterjee

Department of Electrical Engineering

IIT Delhi, New Delhi 110016

15

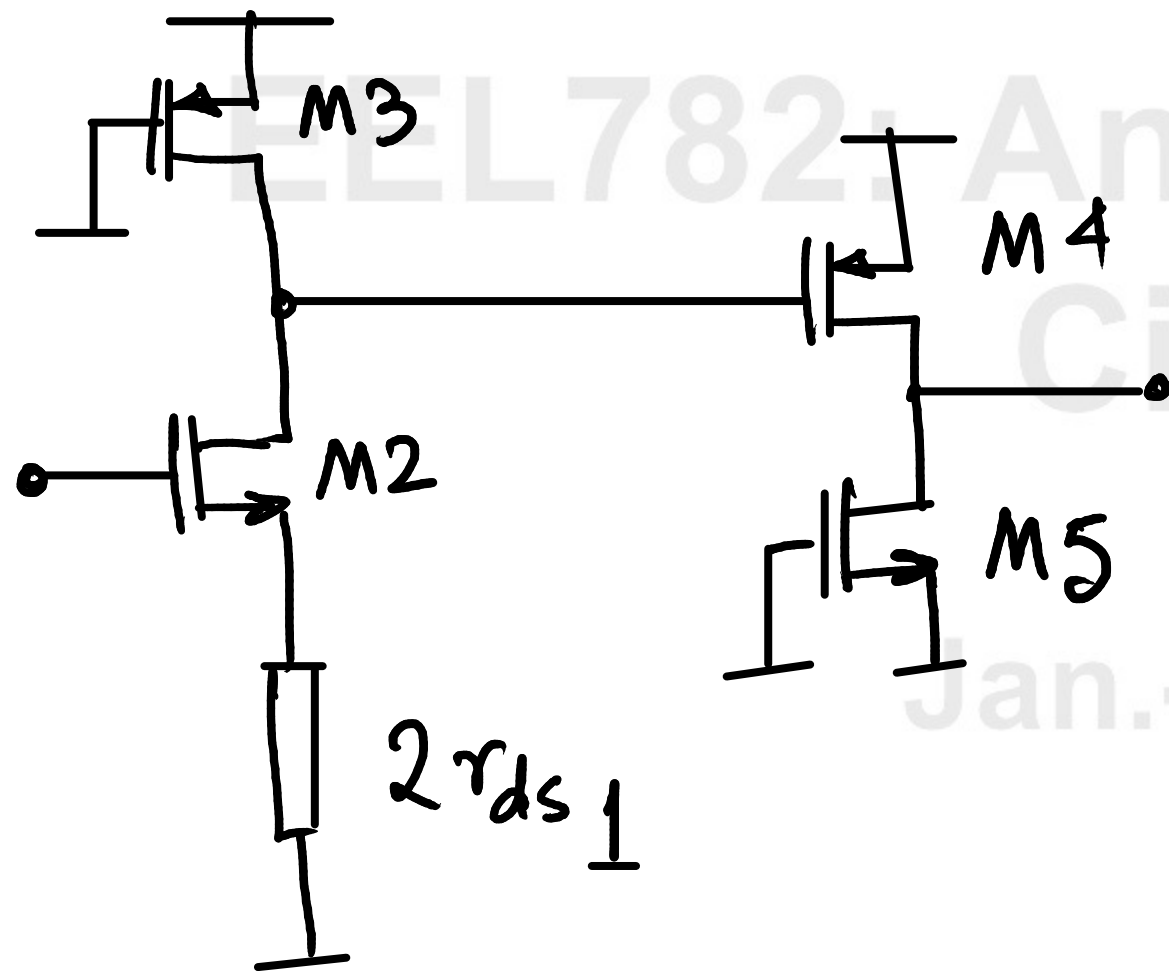Common mode half circuit

Common-mode gain

$$\approx \frac{r_{ds3}}{2r_{ds1}} \times g_{m4} (r_{ds4} \parallel r_{ds5})$$

$$= \frac{20\text{ k}\Omega}{20\text{ k}\Omega} \times 2\text{ mS} (20\text{ k}\Omega \parallel 20\text{ k}\Omega)$$

$$= 20.$$


$$A_c = \frac{v_o^+ + v_o^-}{v_i^+ + v_i^-} \approx 20$$

16

Unity-gain bandwidth  $\approx \frac{g_{m2}}{C} = \frac{2\text{mS}}{13\text{pF}} = 153.85 \text{ Mrad/sec}$

(First-pole at  $24.5\text{MHz} / 400 = 61.25 \text{ kHz}$ )  $= 24.5 \text{ MHz}$

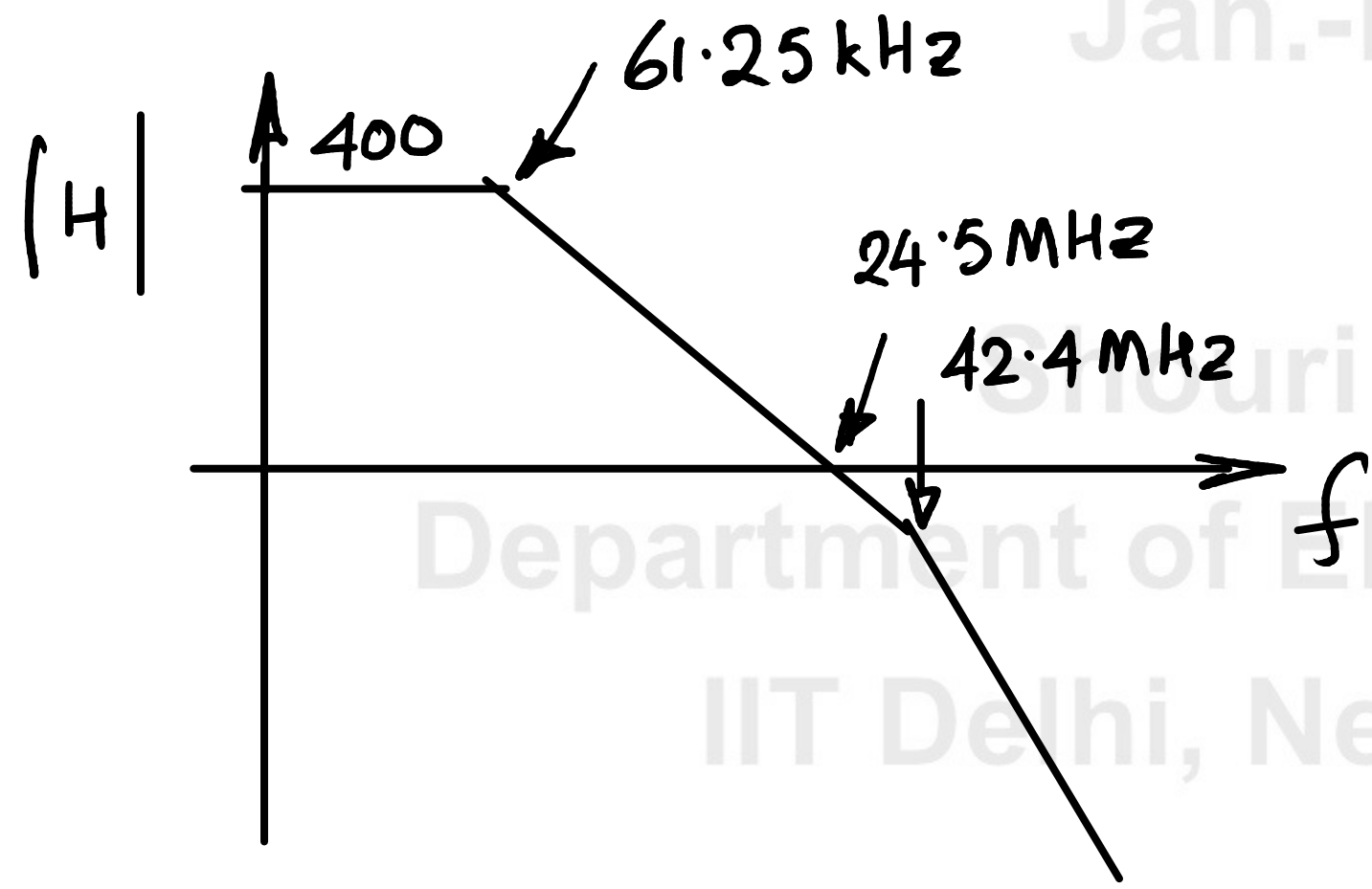Second pole  $\approx \frac{g_{m4}}{C_L} = \frac{2\text{mS}}{7.5\text{pF}} = 266.7 \text{ Mrad/sec}$   
 $= 42.4 \text{ MHz}$



$$H(j\omega) = \frac{A_d}{(1+j\omega/p_1)(1+j\omega/p_2)}$$

$$\angle H(j\omega) = -\tan^{-1} \omega/p_1 - \tan^{-1} \omega/p_2$$

$$p_1 = g_{m2}/C \cdot A_d ; p_2 = g_{m4}/C_L$$



At  $\omega_0 = g_{m2}/C$  (or, at the unity gain bandwidth frequency)

$$\angle H(j\omega_0) = -\tan^{-1}\left(\frac{\omega_0}{P_1}\right) - \tan^{-1}\left(\frac{\omega_0}{P_2}\right)$$

$$= -\tan^{-1}\left(\frac{g_{m2}/C_c}{g_{m2}/C_c/A_d}\right) - \tan^{-1}\left(\frac{g_{m2}/C_c}{g_{m4}/C_L}\right)$$


$$= -\tan^{-1}(A_d) - \tan^{-1}(C_L/C_c)$$

$$= -90^\circ - 30^\circ = -120^\circ$$

$$\therefore \text{phase margin} = -120^\circ - (-180^\circ) = 60^\circ$$


IIT Delhi, New Delhi 110016

# EEL782: Analog Integrated Circuits

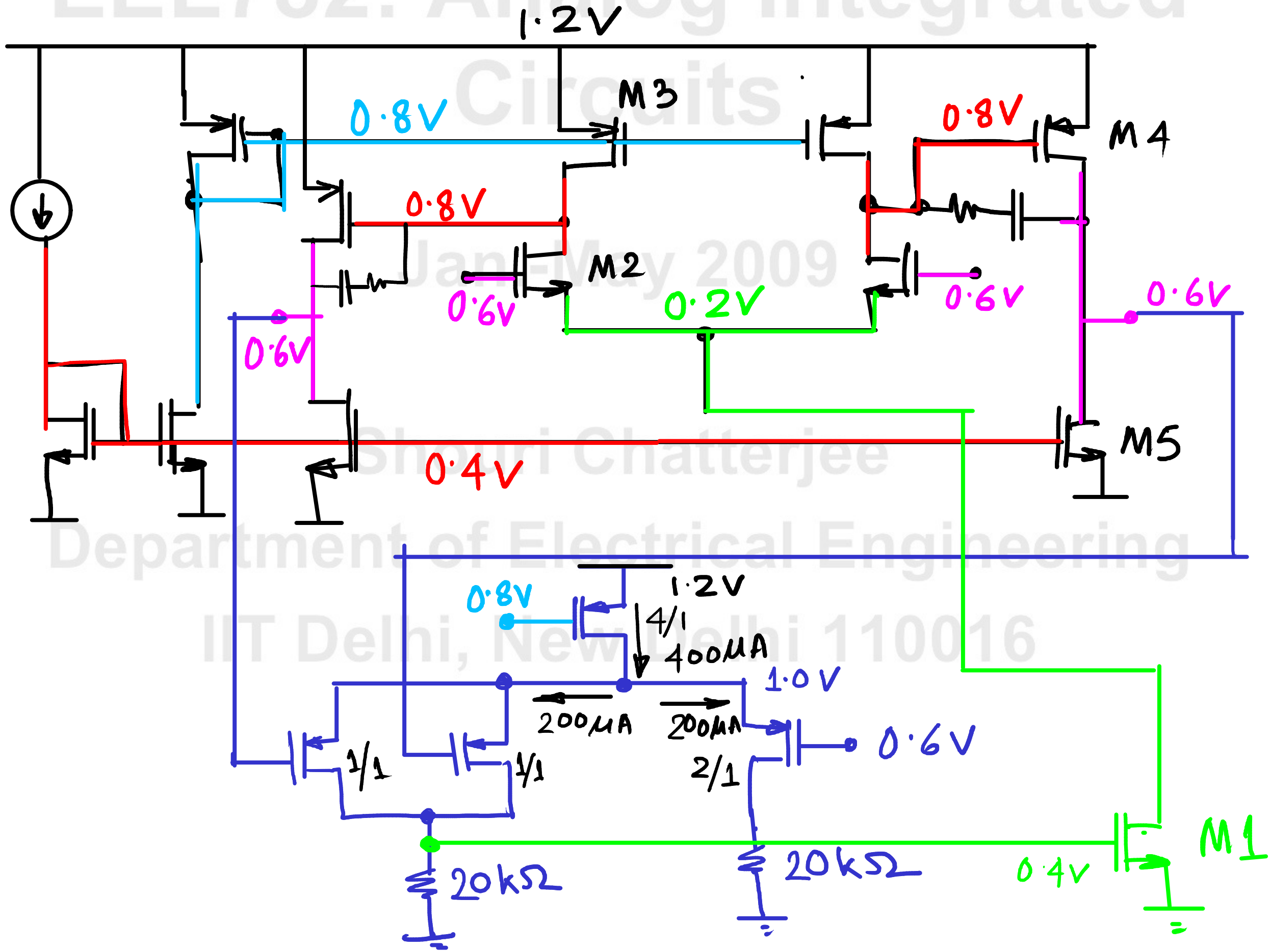

Shreyi Chatterjee  
Department of Electrical Engineering  
IIT Delhi, New Delhi 110016

18) Noise computation

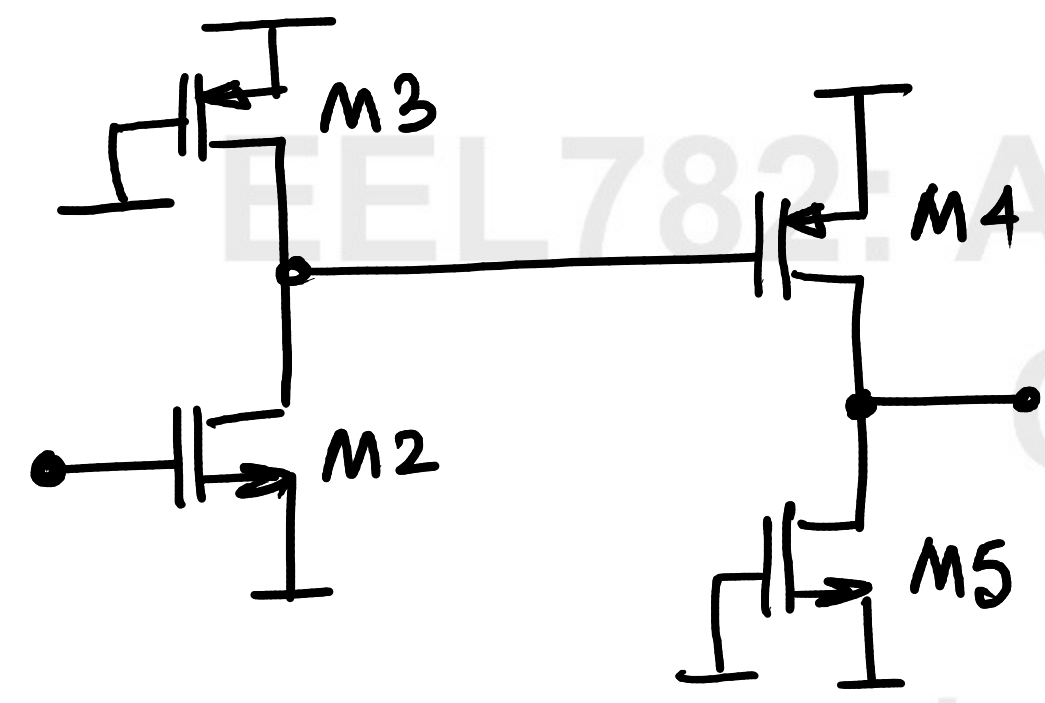

M2 contribution at input :

$$\overline{i_{n_2}^2} / g_{m_2}^2$$

M3 contribution at input :

$$\overline{i_{n_3}^2} / g_{m_2}^2$$

(Noise current  $i_{n_3}$  gets referred back to the input.)

M4 contribution at input :

$$\frac{\overline{i_{n_4}^2} \cdot (r_{ds_4} \parallel r_{ds_5})^2}{g_{m_2}^2 (r_{ds_2} \parallel r_{ds_3})^2 g_{m_4}^2 (r_{ds_4} \parallel r_{ds_5})^2} = \frac{\overline{i_{n_4}^2}}{g_{m_2}^2 (r_{ds_2} \parallel r_{ds_3})^2 g_{m_4}^2}$$

M5 contribution at input :  $\overline{i_{n_5}^2} / g_{m_2}^2 (r_{ds_2} \parallel r_{ds_3})^2 g_{m_4}^2$

Total input referred noise voltage squared :

$$\frac{1}{g_{m2}^2} \left( \overline{i_{n2}^2} + \overline{i_{n3}^2} + \frac{\overline{i_{n4}^2} + \overline{i_{n5}^2}}{g_{m4}^2 (r_{ds2} \parallel r_{ds3})^2} \right)$$

$$= \frac{21.33 \times 10^{-24}}{4 \times 10^{-6}} \times \left( 1 + 1 + \frac{2}{4 \times 10^{-6} \times (10 \times 10^3)^2} \right)$$

$$= \frac{21.33 \times 10^{-24}}{4 \times 10^{-6}} \times 2.005 = 10.7 \times 10^{-18} \text{ V}^2/\text{Hz}$$

Root-mean-squared noise voltage per unit frequency

$$= 3.3 \text{ nV}/\sqrt{\text{Hz}}$$

$$\begin{aligned} \overline{i_{n2}^2} &= \overline{i_{n3}^2} = \overline{i_{n4}^2} = \overline{i_{n5}^2} \\ &= \frac{8}{3} \cdot 0.025 \times 1.6 \times 10^{-19} \times 2 \times 10^{-3} \\ &= 21.33 \times 10^{-24} \text{ A}^2/\text{Hz} \end{aligned}$$