

Minor 1 Solutions

EEL 782 Analog ICs

$$\textcircled{1} \quad I_{DS} = I_0 \exp\left(\frac{|V_{GS}|}{\xi \nu_T}\right) \left(1 - \exp\left(-\frac{|V_{DS}|}{\eta \nu_T}\right)\right)$$

For nMOS, $V_{GS}, V_{DS} > 0$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = \frac{I_0}{\xi \nu_T} \left(1 - \exp\left(-\frac{V_{DS}}{\eta \nu_T}\right)\right) \cdot \exp\left(\frac{V_{GS}}{\xi \nu_T}\right) = \frac{I_{DS}}{\xi \nu_T}$$

For pMOS, $V_{GS}, V_{DS} < 0$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = \frac{I_{DS}}{\xi \nu_T}$$

Similarly, for nMOS

$$g_{ds} = \frac{\partial I_{DS}}{\partial V_{DS}} = \frac{I_0}{\eta \nu_T} \exp\left(\frac{V_{GS}}{\xi \nu_T}\right) \exp\left(-\frac{V_{DS}}{\eta \nu_T}\right)$$

$$\approx \frac{I_{DS}}{\eta \nu_T} \cdot \exp\left(-\frac{V_{DS}}{\eta \nu_T}\right)$$

Likewise, for pMOS devices, we will arrive at the same result, with sign adjustments.

Current through M5

assuming saturation : $\approx I_0 \exp\left(\frac{0.17V}{25mV}\right) = 1 \times 1nA \times 900 = 0.9 \mu A$

Check : Current through M1

assuming saturation : $\frac{1.8 \mu A}{2} = 0.9 \mu A \rightarrow$ verified

	Current	V_{GS}
M1	$0.9 \mu A$	$0.17V$
M2	$1.8 \mu A$	$0.17V$
M3	$0.9 \mu A$	$0.17V$
M4	$0.9 \mu A$	$0.17V$
M5	$0.9 \mu A$	$0.17V$

This means :

node A is at

$$0.88V + 0.17V$$

$$= 1.05V$$

node B is at

$$0.32V - 0.17V$$

$$= 0.15V$$

node C is at

$$0.6V + 0.17V$$


$$= 0.77V$$

Device	I_D	$ V_{DS} $	g_m	g_{ds}	r_{ds}
M1	$0.9\mu A$	$0.45V$	$36\mu S$	$2.22nS$	$450M\Omega$
M2	$1.8\mu A$	$0.15V$	$72\mu S$	$1.8\mu S$	$550k\Omega$
M3	$0.9\mu A$	$0.45V$	$36\mu S$	$2.22nS$	$450M\Omega$
M4	$0.9\mu A$	$0.45V$	$36\mu S$	$2.22nS$	$450M\Omega$
M5	$0.9\mu A$	$0.15V$	$36\mu S$	$0.9\mu S$	$1.1M\Omega$

$$g_m = I_{DS} / 25mV$$

$$g_{ds} = \frac{I_{DS}}{50mV} \cdot \exp\left(-\frac{V_{DS}}{50mV}\right)$$

③ Differential mode half circuit :

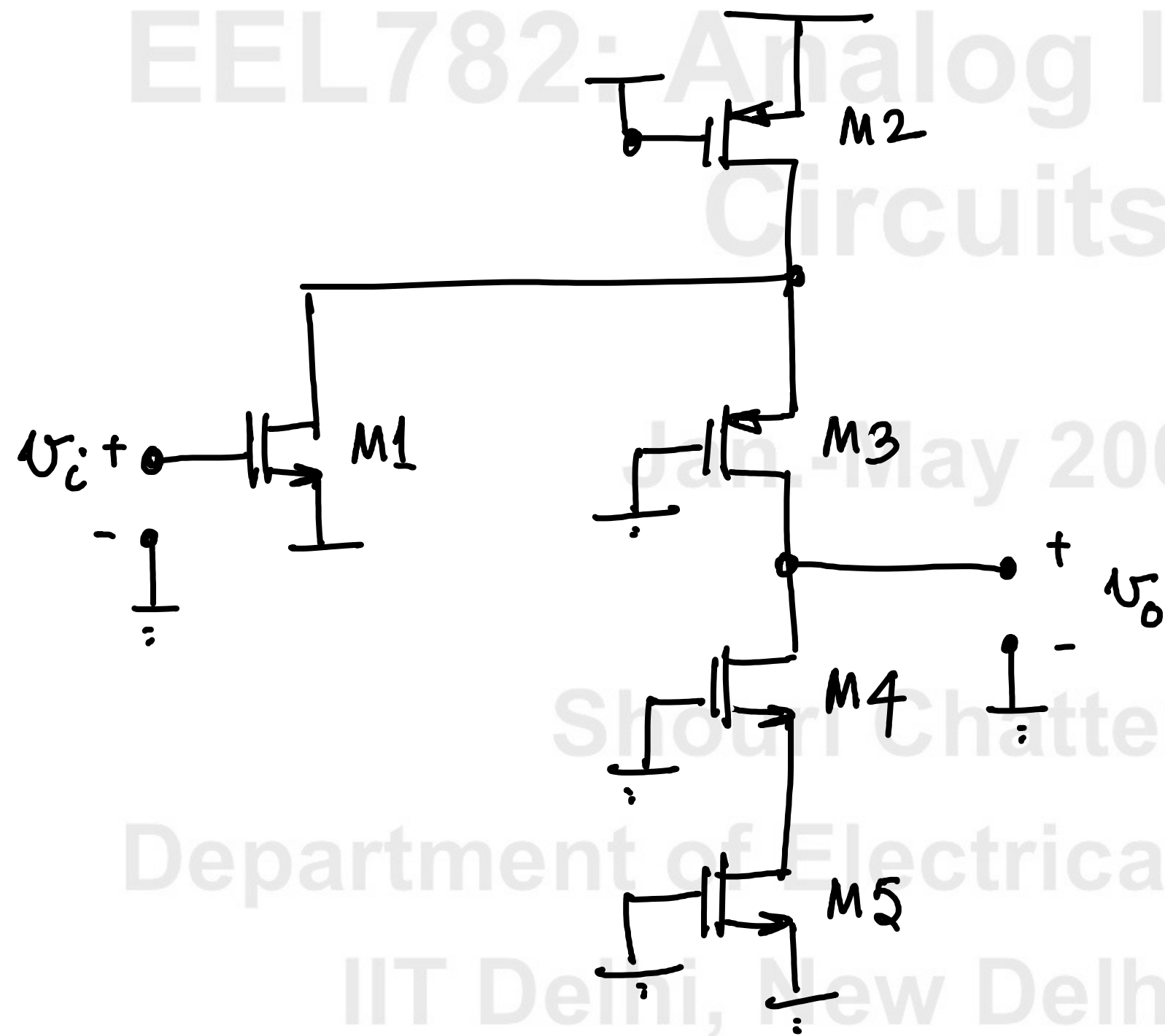

EEL782: Analog Integrated Circuits


Jan-May 2009

Shourj Chatterjee

Department of Electrical Engineering

IIT Delhi, New Delhi 110016

For R_{out} :

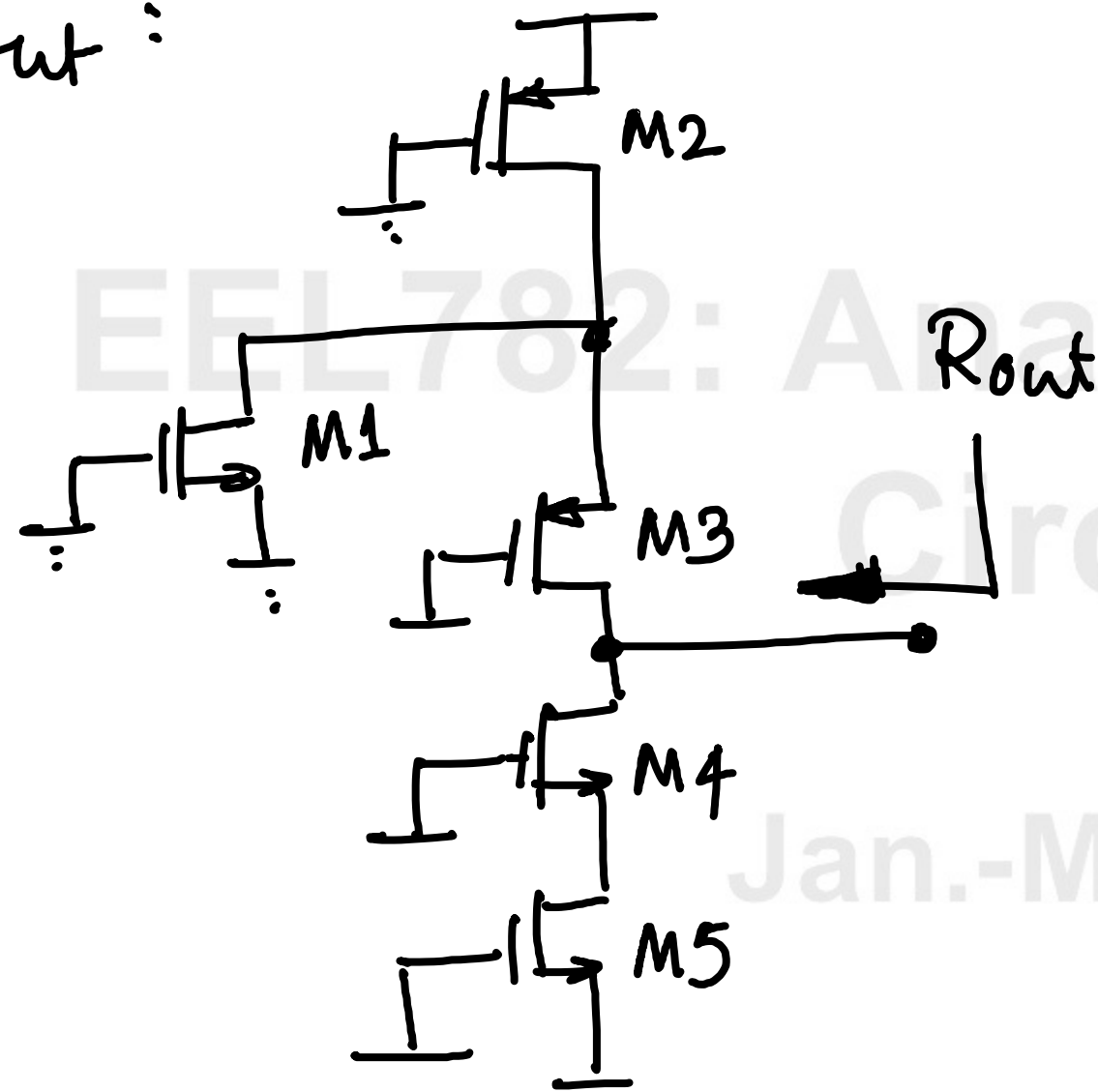

Looking into drain of M4:

$$\approx g_{m4} r_{ds4} r_{ds5}$$

Looking into drain of M3:


$$\approx g_{m3} r_{ds3} (r_{ds2} \parallel r_{ds1})$$

$$R_{out} \approx (g_{m4} r_{ds4} r_{ds5}) \parallel (g_{m3} r_{ds3} (r_{ds2} \parallel r_{ds1}))$$

$$= (36 \mu\text{S} \cdot 450 \text{M}\Omega \cdot 1.1 \text{M}\Omega) \parallel (36 \mu\text{S} \cdot 450 \text{M}\Omega \cdot (1.1 \text{M}\Omega \parallel 550 \text{k}\Omega))$$

$$= 17.8 \text{G}\Omega \parallel 5.94 \text{G}\Omega = \boxed{4.45 \text{G}\Omega}$$

For G_m :

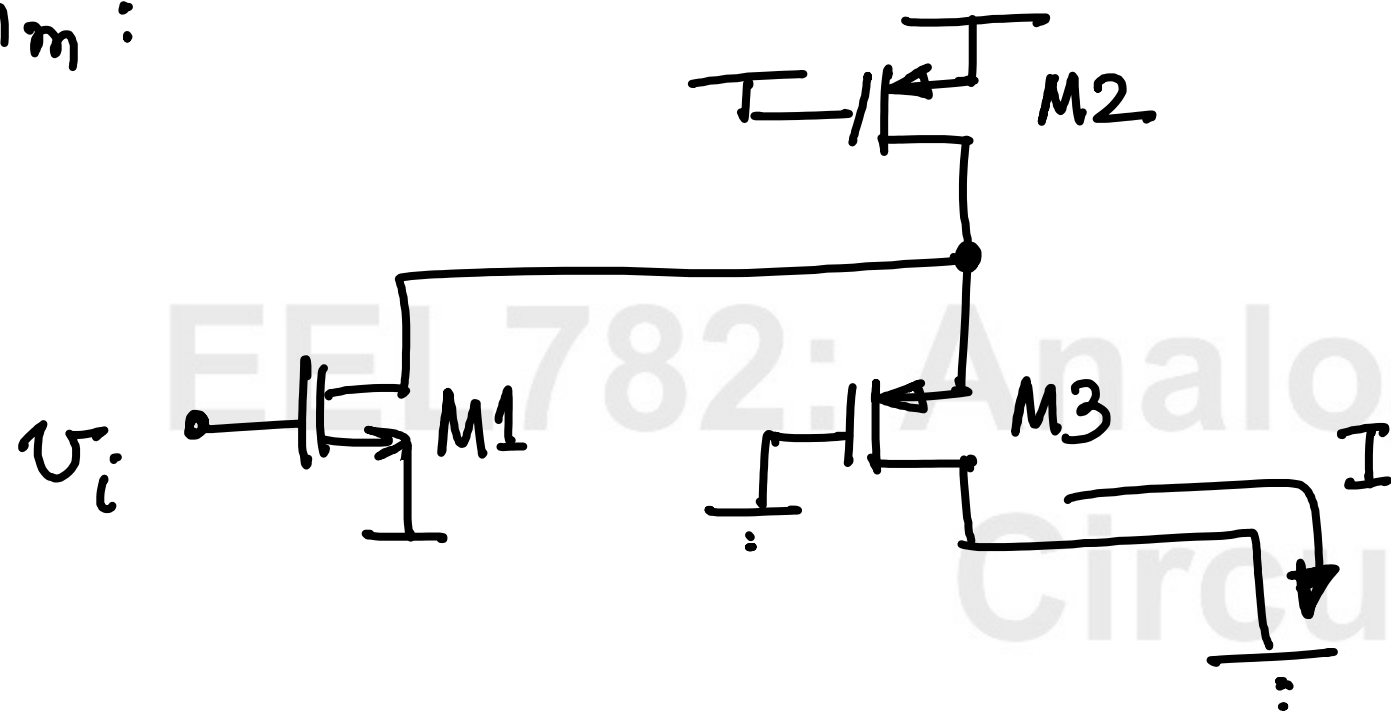

Current $g_{m1} v_i$ sees r_{ds2} ,

$1/g_{m3}$ and r_{ds3} .

$r_{ds2} = 550 \text{ k}\Omega$; $r_{ds3} = 450 \text{ M}\Omega$;

$1/g_{m3} = 27.78 \text{ k}\Omega$

Jan.-May 2009

→ almost all the current goes through M3.

$\therefore I \approx -g_{m1} v_i$


$\therefore G_m \approx -g_{m1} = -36 \mu\text{S}$

Gain = $G_m R_{out} = 160,000 = A_v$


IIT Delhi, New Delhi 110016

4

Common-mode half circuit

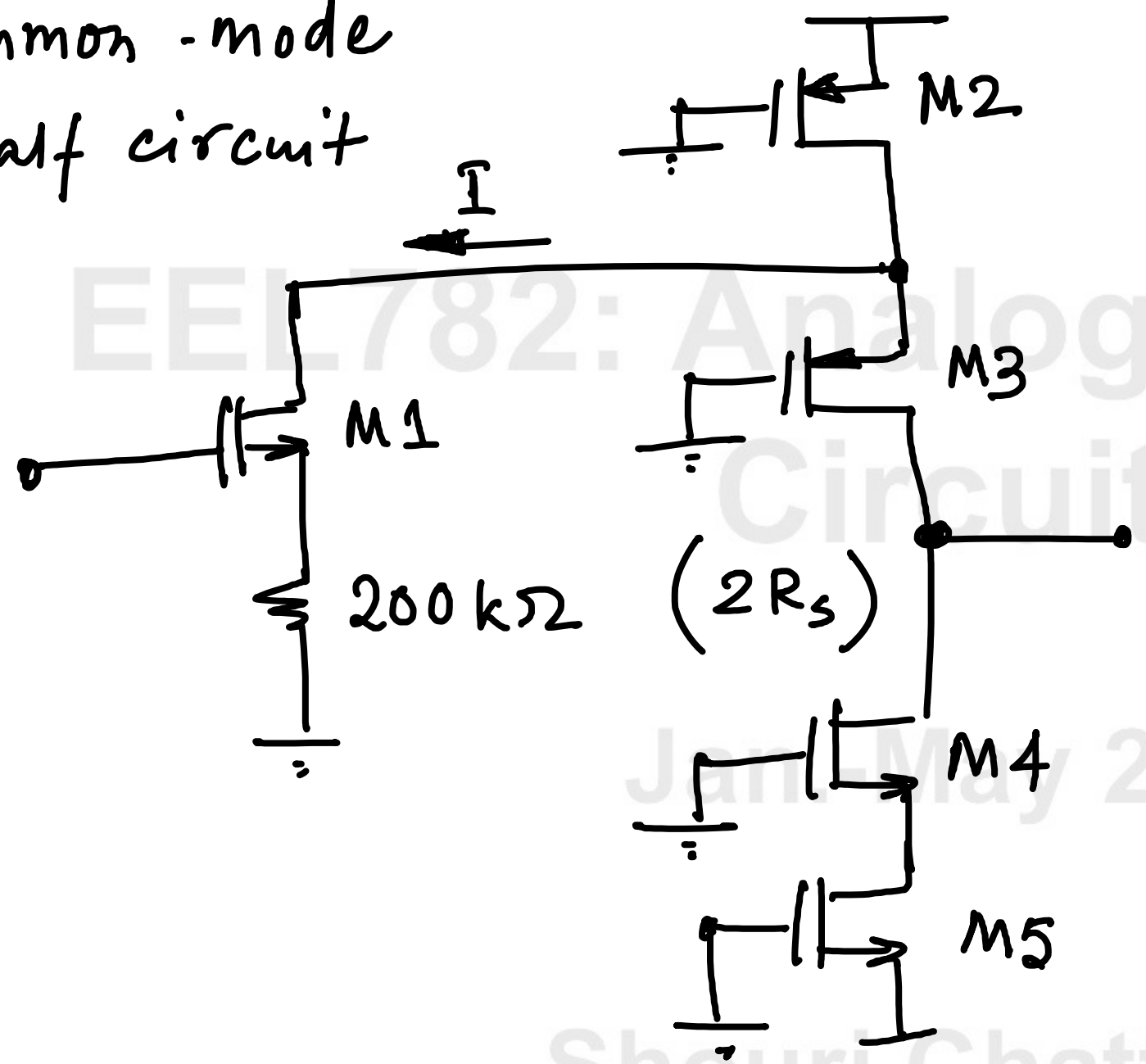

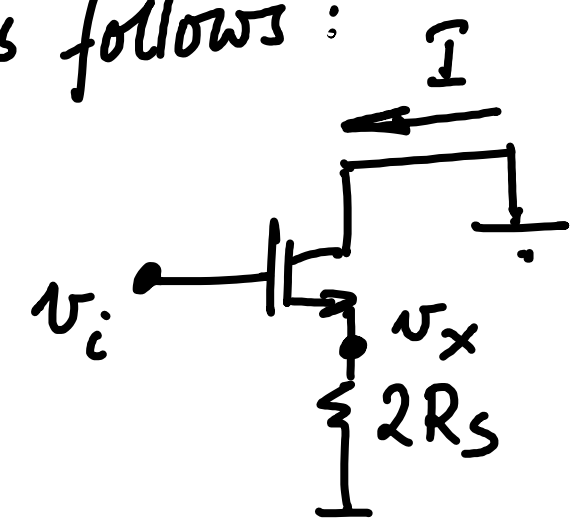A model for the first stage transconductance is as follows:



$$I = g_{m1}(v_i - v_x) = \frac{v_x}{2R_s}$$

$$\therefore v_x = \frac{g_{m1}}{g_{m1} + \frac{1}{2R_s}} \cdot v_i$$

$$\text{and } I = \frac{g_{m1}}{1 + 2R_s \cdot g_{m1}} \cdot v_i$$

So, common-mode $G_m \approx \frac{\text{diff-mode } G_m}{1 + 2R_s g_{m1}}$

$$\Rightarrow A_c \approx \frac{A_v}{8.2}$$

5)

$$V_{DS4} = |V_{DS3}| = 0.45V$$

$$|V_{DS2}| = V_{DS5} = 0.15V$$

So output node can increase by upto 0.3V,
decrease by upto 0.3V] pk-pk swing of 0.6V

differential pk-pk swing of 1.2V

Shouri Chatterjee

Department of Electrical Engineering

IIT Delhi, New Delhi 110016