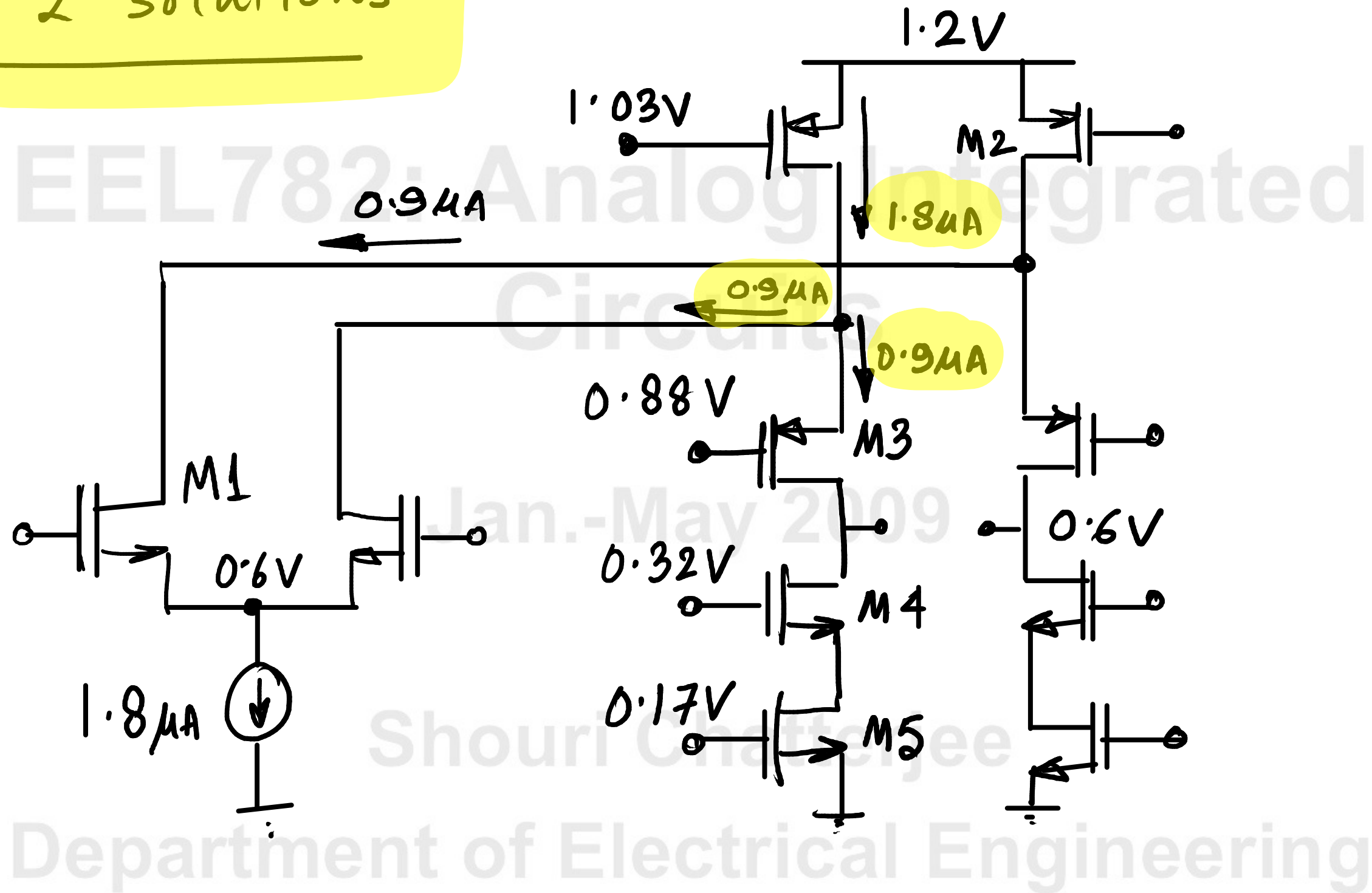



Minor 2 solutions



$$\text{Current through } M2 \Rightarrow I_2 = 4 \times 0.5 \text{ nA} \times \exp\left(\frac{0.17}{0.025}\right) \approx 1.8 \mu\text{A}$$

So, by KCL, current through M3, M4, M5 = 0.9 μA

①

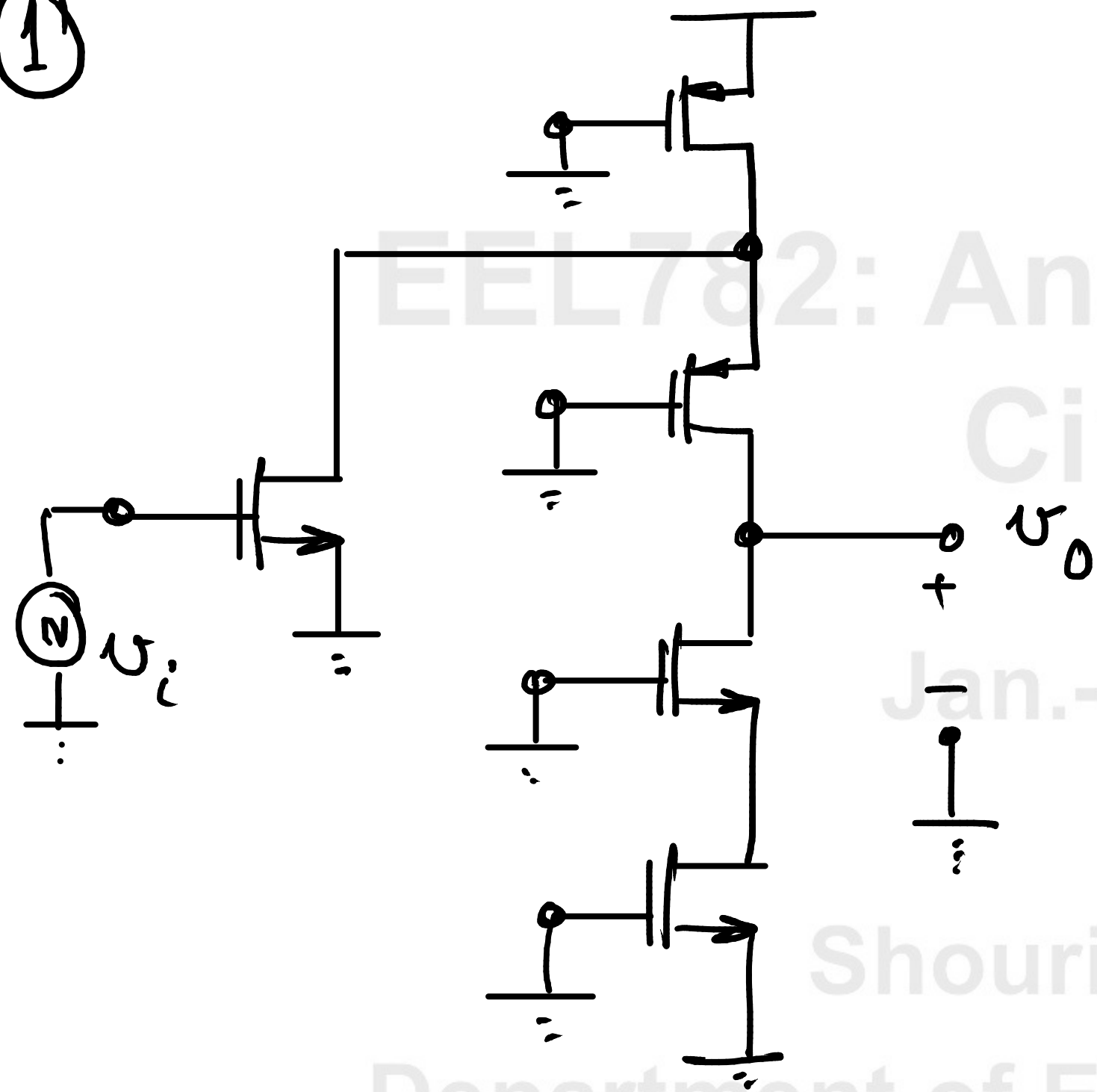

Small signal
differential mode
half circuit

Jan.-May 2009

Shouri Chatterjee

Department of Electrical Engineering

IIT Delhi, New Delhi 110016

② $C_{GS} = C_{GD} = \frac{1}{2} W \cdot L \cdot 8 \text{ fF/sq.}\mu\text{m}$

	W	L	C_{GS}	C_{GD}
M1	1 μm	1 μm	4 fF	4 fF
M2	4 μm	1 μm	16 fF	16 fF
M3	2 μm	1 μm	8 fF	8 fF
M4	1 μm	1 μm	4 fF	4 fF
M5	1 μm	1 μm	4 fF	4 fF

Capacitance at X

$$C_{GD1} + C_{GD2} + C_{GS3} = 28 \text{ fF}$$

Capacitance at Z

$$C_{GD5} + C_{GS4} = 8 \text{ fF}$$

Capacitance at output


$$C_{GD3} + C_{GD4} + C_L = 1.012 \text{ pF}$$

Resistance at output

$$\begin{aligned} & (g_{m4} r_{ds4} r_{ds5}) \parallel (g_{m3} r_{ds3} (r_{ds1} \parallel r_{ds2})) \\ &= (36 \mu \cdot 10 \text{ M} \cdot 1.2 \text{ M}) \parallel (36 \mu \cdot 10 \text{ M} \cdot (10 \text{ M} \parallel 0.6 \text{ M})) \\ &= 430 \text{ M}\Omega \parallel 200 \text{ M}\Omega = 136 \text{ M}\Omega \end{aligned}$$

Resistance at X :
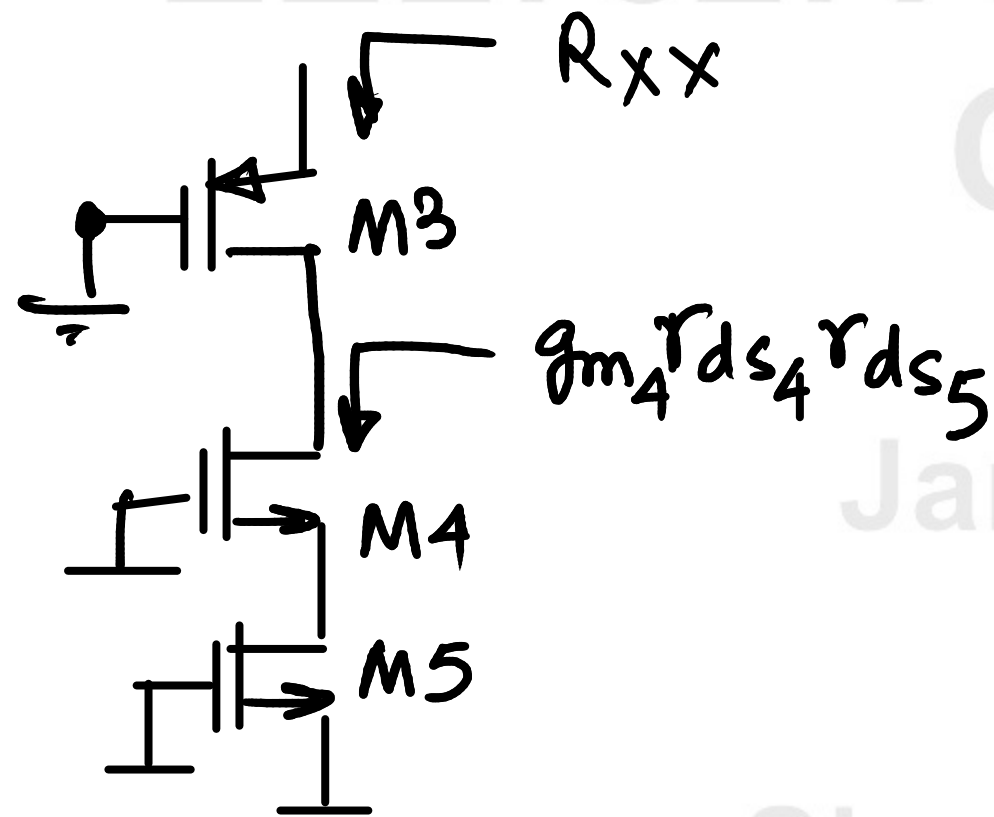
$$R_x = r_{ds1} \parallel r_{ds2} \parallel \text{Resistance looking into source of } M3$$



$$R_{xx} = \frac{r_{ds3} + g_{m4} r_{ds4} r_{ds5}}{1 + g_{m3} r_{ds3}}$$


$$= \frac{10\text{M}\Omega + 430\text{M}\Omega}{1 + 36\mu \cdot 10\text{M}}$$

$$= 1.2\text{M}\Omega$$

$$R_x = 10\text{M}\Omega \parallel 0.6\text{M}\Omega \parallel 1.2\text{M}\Omega = 380\text{k}\Omega$$

Resistance at Z (Similar to X)
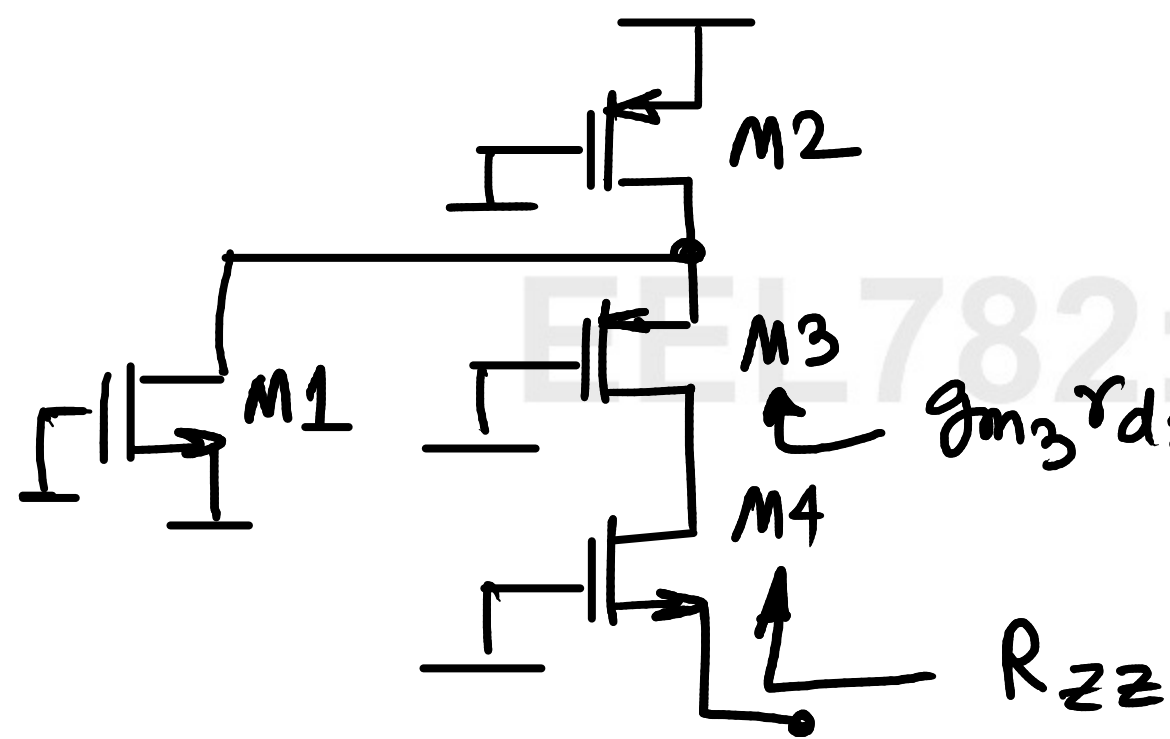
$$R_z = r_{ds5} \parallel \text{Resistance looking into source of } M4$$



$$R_{zz} = \frac{r_{ds4} + g_{m3}r_{ds3}(r_{ds2} \parallel r_{ds1})}{1 + g_{m4}r_{ds4}}$$


$$= \frac{10\text{M}\Omega + 200\text{M}\Omega}{1 + 36\mu \cdot 10\text{M}} = 580\text{k}\Omega$$

$$R_z = 1.2\text{M}\Omega \parallel 580\text{k}\Omega = 390\text{k}\Omega$$

Pole frequencies

	Cap	Res	Pole	
X	28 fF	380 kΩ	94 Mrad/sec	15 MHz
Z	8 fF	390 kΩ	320 Mrad/sec	51 MHz
Output	1.012 pF	136 MΩ	7.2 krad/sec	1.15 kHz


3

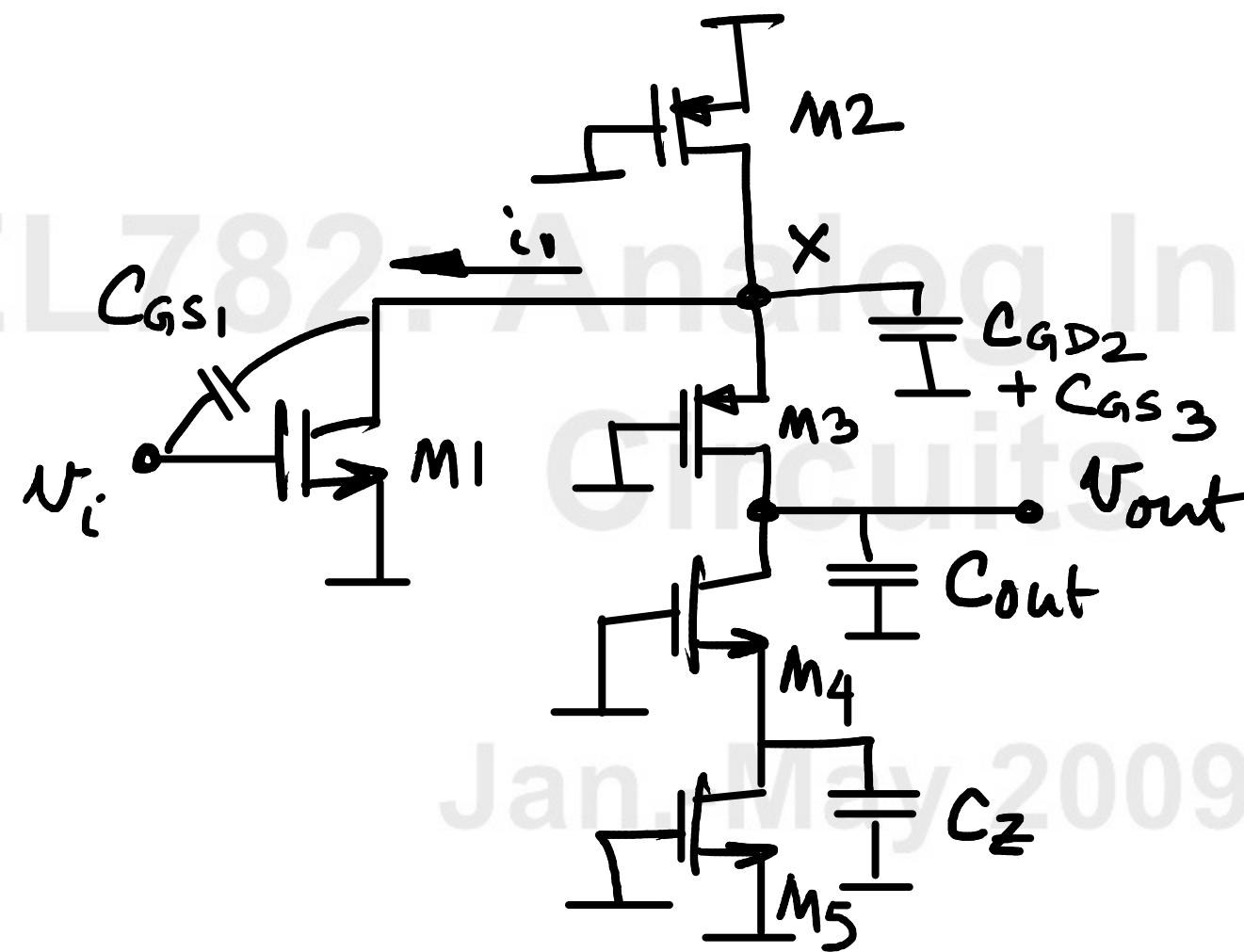

Zero in the transfer function means that at some complex frequency, say ' s_z ', $v_{out} = 0$

Consider applying v_i at the input. If $i_1 = 0$ at ' s_z ', then $v_x = 0$ ($v_x = i_1 \cdot \text{some impedance}$), which means $v_{out} = 0$.

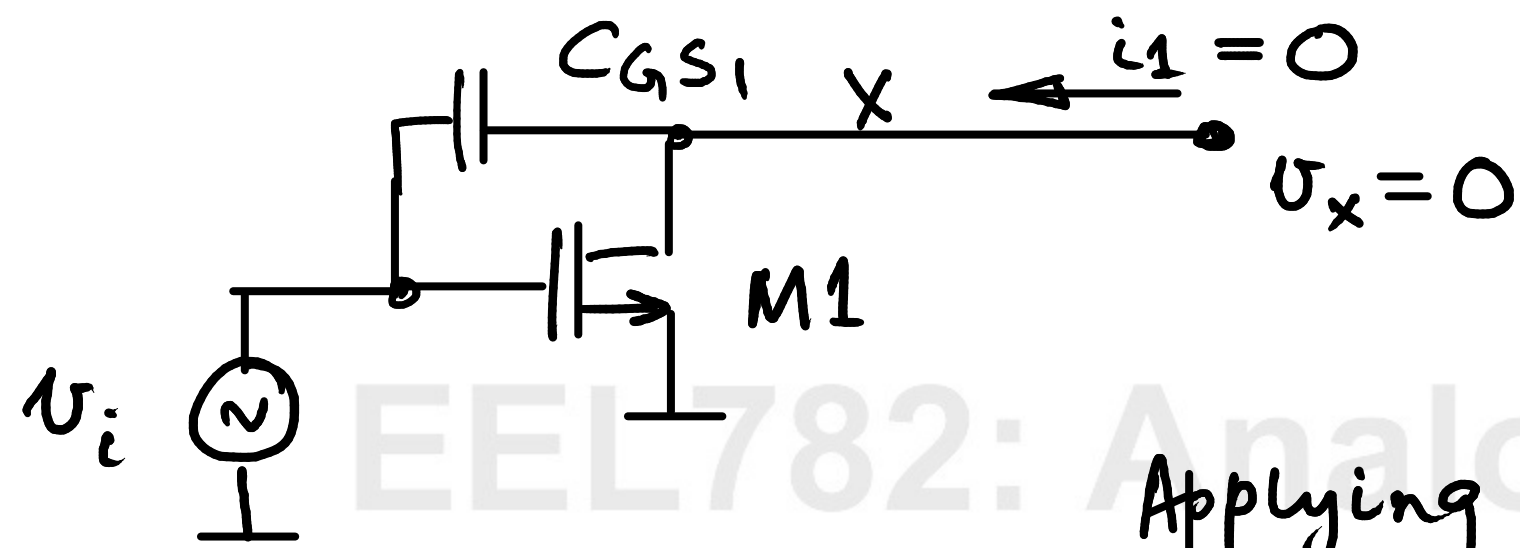So is there a frequency ' s_z ' at which $i_1 = 0$?



Applying KCL at X,

$$g_m v_i = v_i \cdot s_z C_{GS1}$$

$$\therefore s_z = g_{m1} / C_{GS1}$$

There exists an RHP zero at g_{m1} / C_{GS1} or at $\frac{36 \text{ pS}}{4 \text{ fF}}$

Shouri Chatterjee


$$= 9 \text{ GRad/sec}$$

Department of Electrical Engineering

$$= 1.4 \text{ GHz}$$

IIT Delhi, New Delhi 110016

4

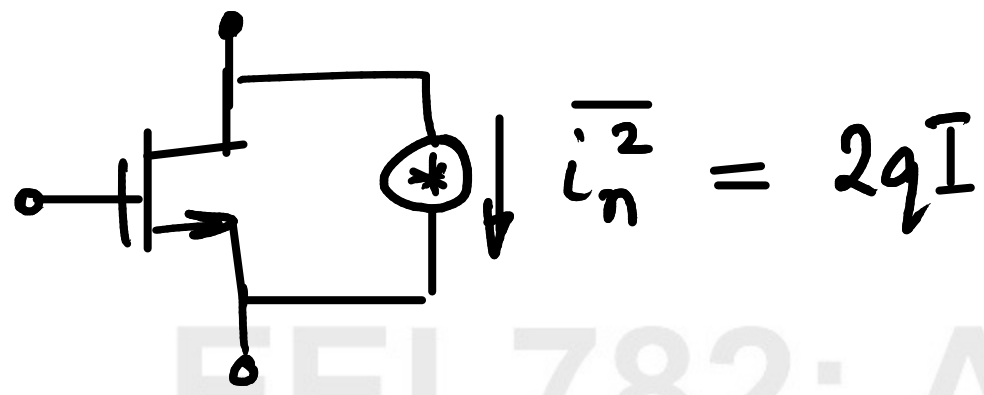


M1

Noise current sq. = $\overline{i_n^2}$

Input refd. noise voltage sq. = $\frac{\overline{i_n^2}}{g_{m1}^2}$

$$= \frac{2q \cdot 0.9 \mu A}{36 \mu S \cdot 36 \mu S}$$

$$= 222 \times 10^{-18} \frac{V^2}{Hz}$$

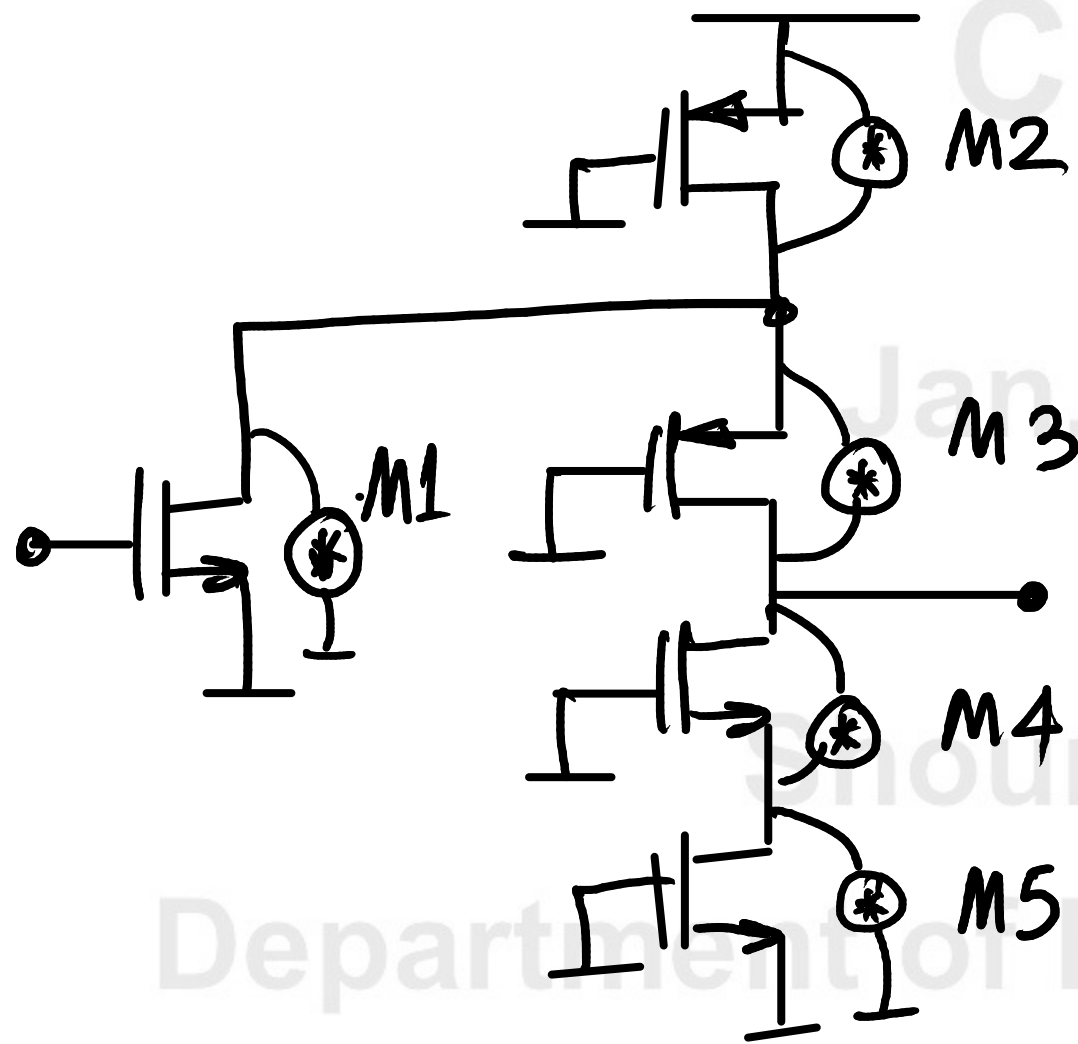

M2

Any noise current will go to the output (source of M3 is low impedance)

$$V_{out} \approx i_{n2} \cdot R_{out}$$

$$\text{Input referred noise voltage sq.} = \frac{V_{out}^2}{G_m^2 R_{out}^2} = \frac{i_{n2}^2 \cdot R_{out}^2}{G_m^2 \cdot R_{out}^2}$$

$$= \frac{i_{n2}^2}{G_m^2} \approx i_{n2}^2 / g_{m1}^2$$

$$i_{n2}^2 / g_{m1}^2 = \frac{29 \cdot 1.8 \mu A}{36 \mu s \cdot 36 \mu s} = 222 \times 10^{-18} \text{ V}^2 / \text{Hz}$$

For M5

All the noise current will go to the output node
(source of M4 is low impedance compared to r_{ds5})

$$\therefore v_{out}^2 \approx i_{n5}^2 \cdot R_{out}^2$$


$$\text{Input referred noise voltage} = \frac{v_{out}^2}{G_m^2 R_{out}^2} = \frac{i_{n5}^2}{G_m^2} \approx \frac{i_{n5}^2}{g_{m1}^2}$$

$$= \frac{29 \cdot 0.9 \mu A}{36 \mu s \cdot 36 \mu s} = 222 \times 10^{-18} \text{ V}^2 / \text{Hz}$$

For M3

Let us consider the equivalent noise voltage of the device M3 (as opposed to noise current)

$$v_n^2 = i_n^2 / g_m^2 = 29I / g_m^2$$

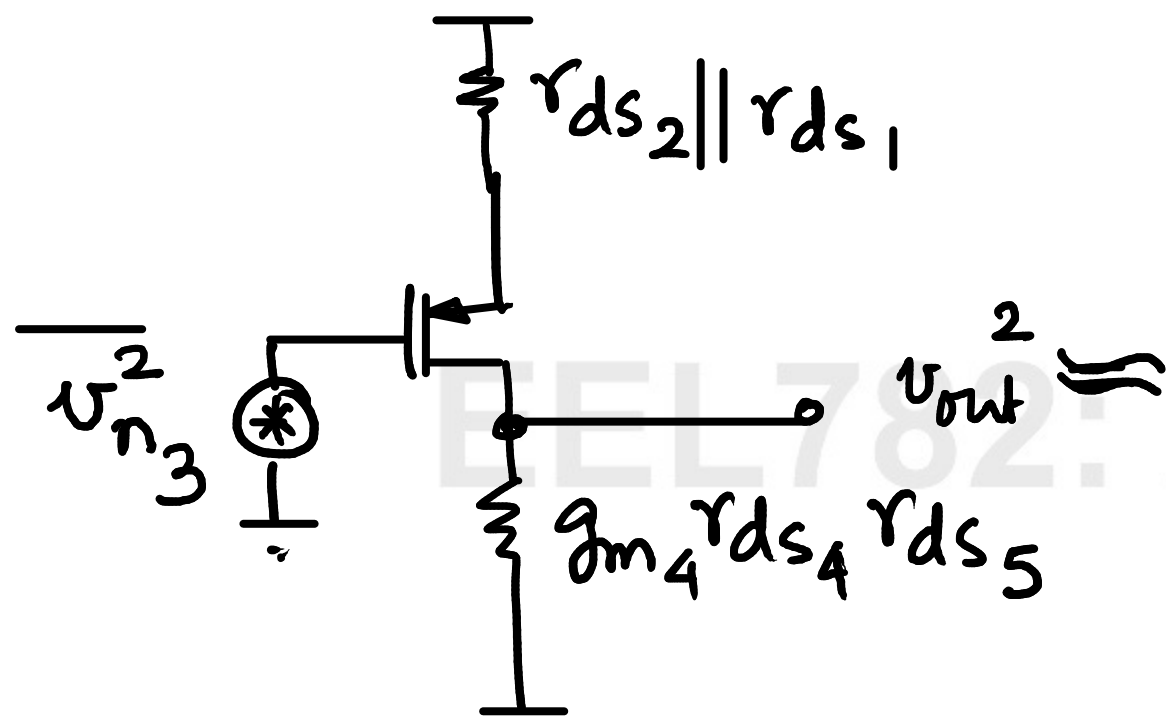

$$v_{out}^2 \approx \frac{v_{n3}^2 (g_{m4} r_{ds4} r_{ds5})^2}{(r_{ds2} || r_{ds1})^2}$$

Input referred noise :

$$\frac{v_{out}^2}{G_m^2 R_{out}^2} = 5.4 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$G_m \approx g_{m1} = 36 \mu\text{S}$$

$$R_{out} \approx 136 \text{ M}\Omega$$


$$g_{m4} r_{ds4} r_{ds5} = 432 \text{ M}\Omega$$

$$r_{ds2} || r_{ds1} = 566 \text{ k}\Omega$$

$$v_{n3}^2 = \frac{2q \cdot 0.9 \mu\text{A}}{36 \mu\text{S} \cdot 36 \mu\text{S}} = 222 \times 10^{-18} \frac{\text{V}^2}{\text{Hz}}$$

M4

Consider the equivalent noise voltage

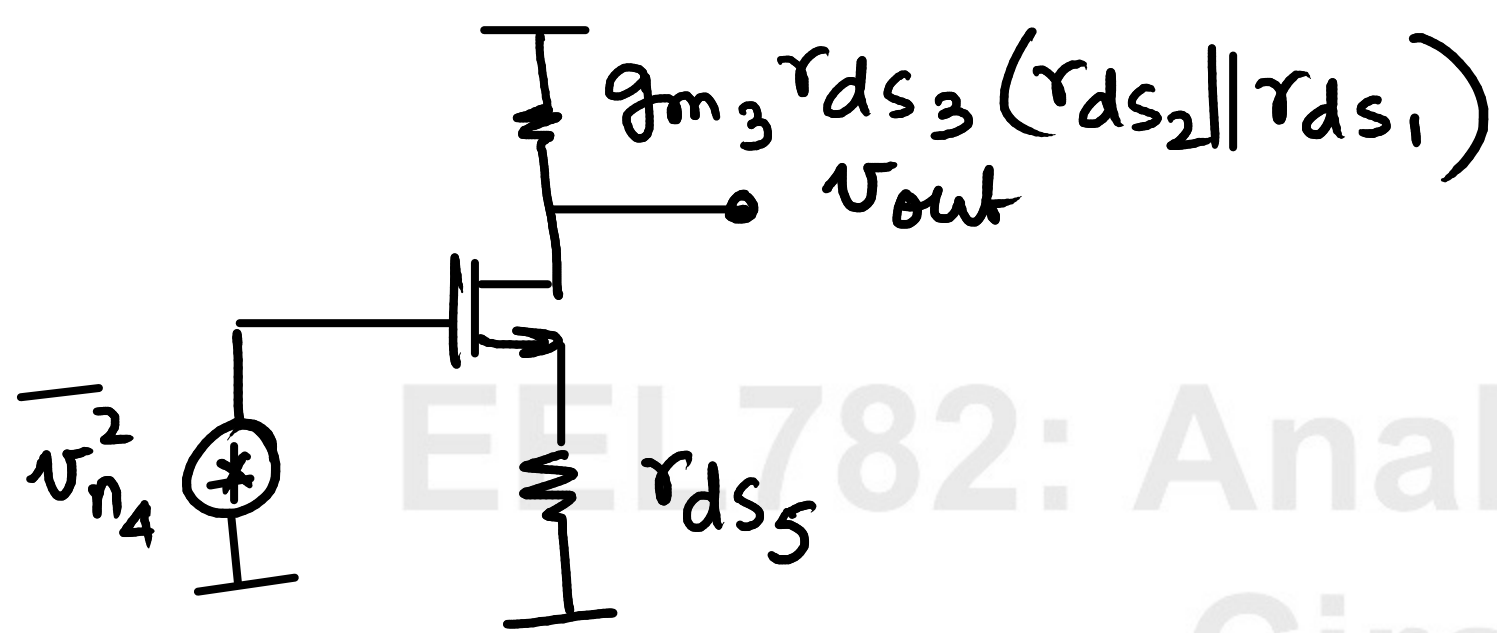

$$\overline{v_{out}^2} = \frac{\overline{v_{n4}^2}}{r_{ds5}^2} \left[g_{m3} r_{ds3} (r_{ds2} \parallel r_{ds1}) \right]^2$$

$$\text{Input refd. noise} = \frac{\overline{v_{out}^2}}{G_m^2 R_{out}^2}$$

$$= 0.25 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$G_m \approx 36 \mu\text{S}$$

$$R_{out} = 136 \text{ M}\Omega$$

$$g_{m3} r_{ds3} (r_{ds2} \parallel r_{ds1}) = 200 \text{ M}\Omega$$

$$r_{ds5} = 1.2 \text{ M}\Omega$$

$$\overline{v_{n4}^2} = \frac{29 \cdot 0.9 \mu\text{A}}{36 \mu\text{S} \cdot 36 \mu\text{S}} = 222 \times 10^{-18} \frac{\text{V}^2}{\text{Hz}}$$

Total input referred noise

$$222 \times 10^{-18} \text{ (M1)} + 444 \times 10^{-18} \text{ (M2)} + 222 \times 10^{-18} \text{ (M5)} + 5.4 \times 10^{-18} \text{ (M3)} + 0.25 \times 10^{-18} \text{ (M4)} \text{ V}^2/\text{Hz}$$

$$= 894 \times 10^{-18} \text{ V}^2/\text{Hz}$$

⑤ Input signal : 0.1 V amplitude

Gain - Bandwidth of design : $1.2 \text{ kHz} \times 36 \mu\text{s} \times 136 \text{ M}\Omega = 5.9 \text{ MHz}$

Noise voltage within GBW : $\sqrt{v_n^2 \times 5.9 \text{ MHz}}$

$= 73 \mu\text{V}$

Out of a 0.1 V signal,
input referred 73 μV noise \rightarrow SNR of about 63 dB
not bad

Shouri Chatterjee

Department of Electrical Engineering

IIT Delhi, New Delhi 110016