

Indian Institute of Technology, Delhi
ELL112/EEL 202: Circuit Theory
Tutorial 2, August 4, 2014 (Revised Aug 6, 2014)

1. In Fig 1, the element X is a $2\ \Omega$ resistor. Find the power supplied by the $6\ \text{V}$ source.
2. In Fig 1, the element X is a $6\ \text{A}$ source with arrow to the right. Find the power supplied by the $6\ \text{V}$ source.
3. In Fig 1, the element X is a dependent current source with its arrow to the right, and a current of $i/3$, where i is the upward current through the $6\ \text{V}$ source. Find i .
4. In Fig 2, S_1, S_2, S_3 are $30, 14,$ and $-2\ \text{V}$ sources, all with positive reference symbols on top. Setup equations for i) mesh analysis, and ii) node analysis.
5. In Fig 2, S_1, S_2, S_3 are $-9, -1.5,$ and $6\ \text{Amp}$ current sources, all flowing upwards. Setup equations for i) mesh analysis, and ii) node analysis.
6. In Fig 3, compute the power supplied by the $24\ \text{V}$ source and the $18\ \text{A}$ source.
7. In Fig 4, when $R_L = 2\ \Omega$, v_1 is $8\ \text{V}$, i_1 is $-2\ \text{A}$, v_L is $2\ \text{V}$. When $R_L = 4\ \Omega$, v'_1 is $12\ \text{V}$, i'_1 is $-2.4\ \text{A}$. Compute v'_L .

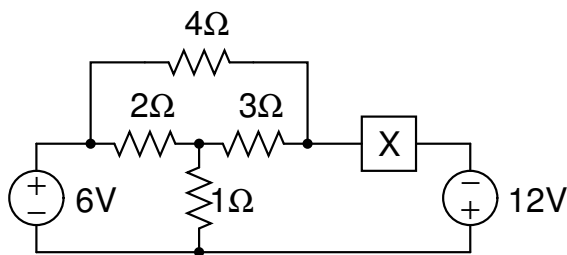


Figure 1

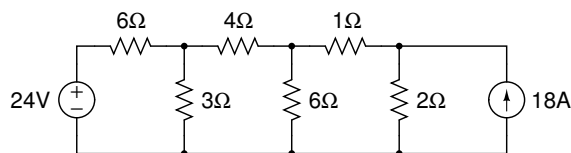


Figure 3

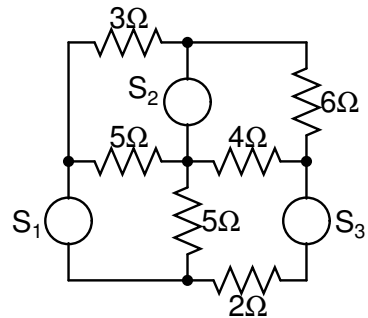


Figure 2

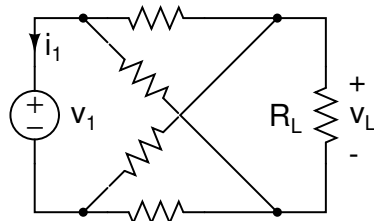


Figure 4