

**Indian Institute of Technology, Delhi**  
**ELL112/EEL 202: Circuit Theory**  
**Tutorial 2 Solution Key**

1. 30 Watts.
2. 37.56 Watts.
3. 18 Watts.
4. NA.
5. NA.
6. Voltage source: 48 Watts; Current source: 456 Watts.
7. 9.6 Volts.