

**Indian Institute of Technology, Delhi**  
**ELL112/EEL 202: Circuit Theory**  
**Tutorial 5, September 1, 2014**

Find the two-port parameters for the circuits below. Choose any one convenient two-port parameter set for each.

