

Indian Institute of Technology, Delhi
ELL304 Analog Circuits
Tutorial 5, 3 September 2015

Find expressions for the (small signal) voltage gain in the circuits shown below. Assume $\lambda \neq 0$ for all devices, except in circuit (i). The operating points of the devices are established through appropriate bias voltages V_b, V_{b_1}, V_{b_2} .

