

# Special Topics in Design I

## DSL 810

### Topic 6

## Output Devices

Instructor: Jay Dhariwal,  
Asst. Prof., Dept. of Design,  
IIT Delhi

4<sup>th</sup> September 2019

# Project reimbursements


- Get approval for your purchases from me/Tas.
- Low cost projects without compromising quality
- Any purchase beyond 5000 ₹ can't be through cash.
- Online purchase fine with GST and credit card/debit card statement for a purchase > 5000 ₹. Use credit card/debit cards for any purchase.
- Local purchase = GST bill mentioning IITD GSTIN = 07AAATI0393L1ZI
- Team meet me for a purchase > 1500 ₹
- Save the bills. Reimbursement procedure – later.

# Output Devices

- LEDs, Displays, Speakers, DC/Servo/Stepper Motors, Relays, Dataloggers
- Sensor vs Actuator


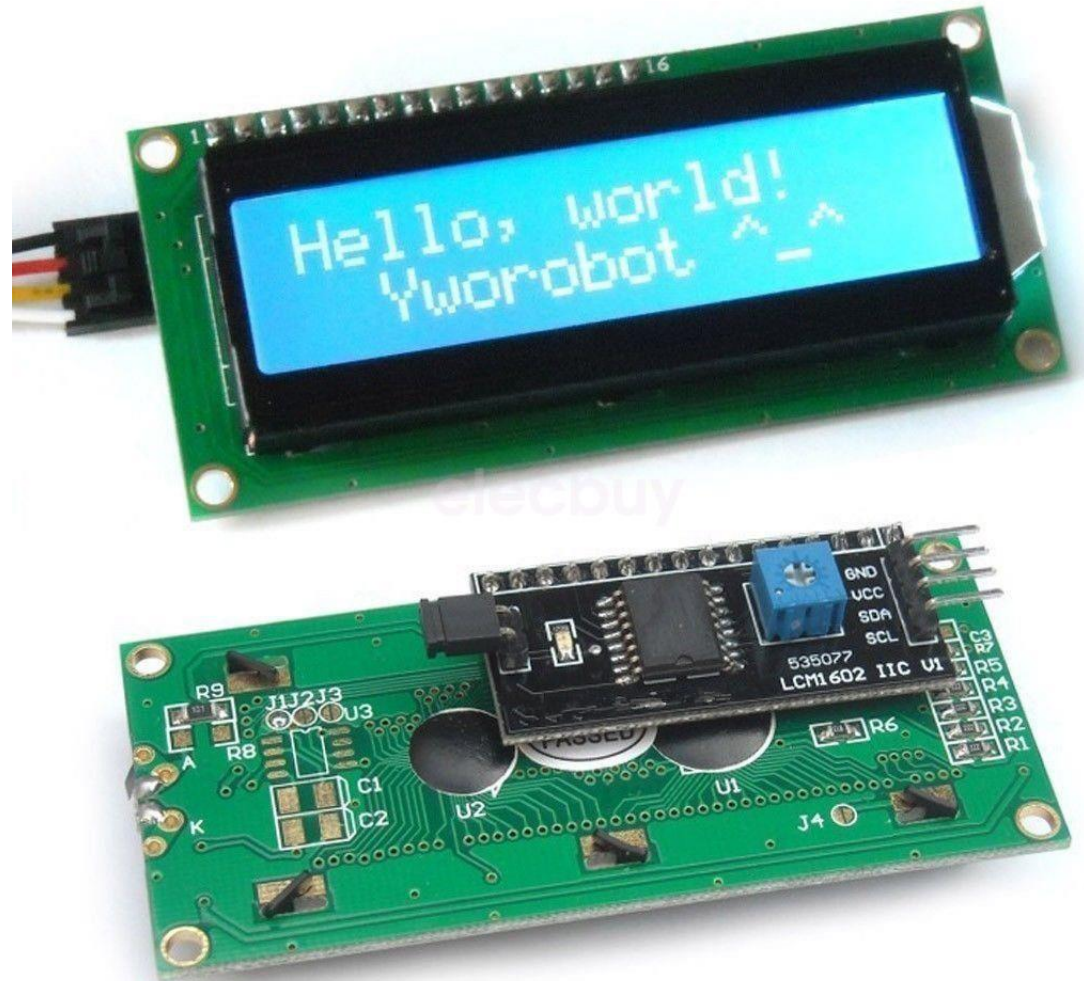
# LCD display

- Lesson 22
  - Adjusting Contrast with a screwdriver.
- # Connections:  
SDA pin to A4 (Uno)  
SCL pin to A5 (Uno)
- [Arduino code](#)
- Other examples


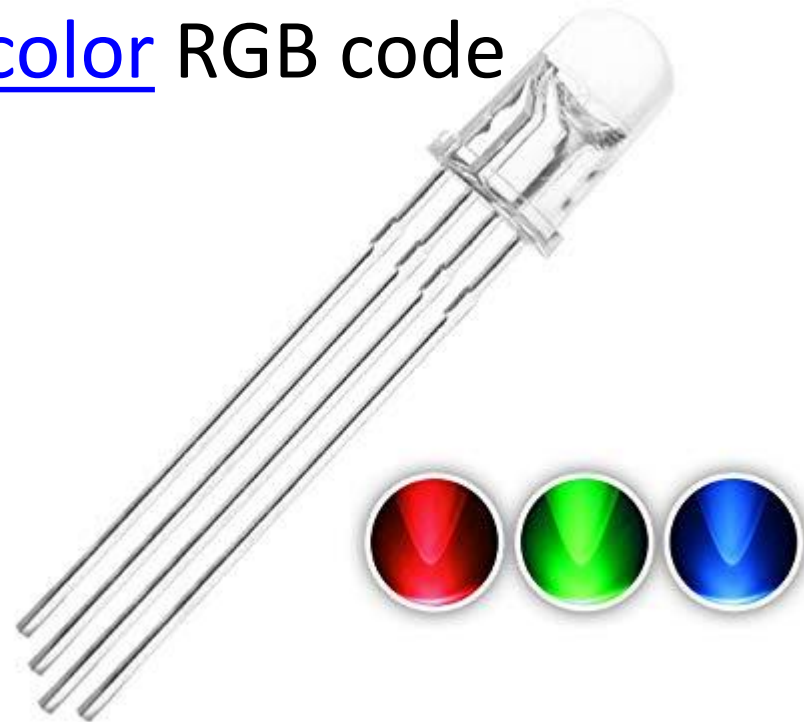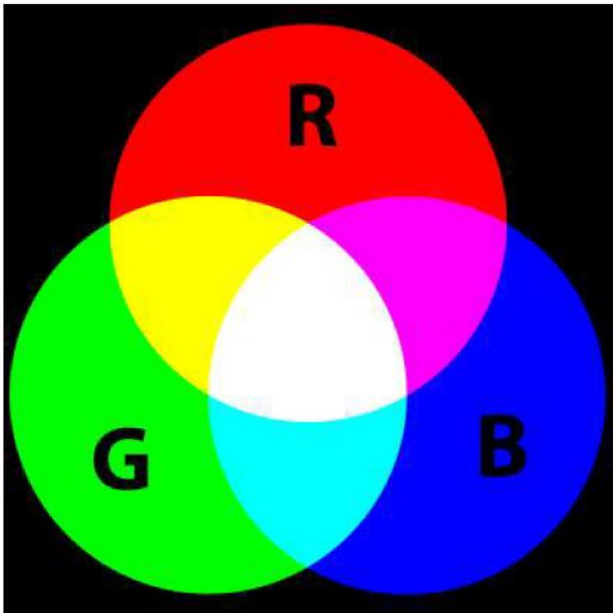
# RGB LED

- PWM with RGB LED with common anode (Lesson 4). NOTE: Longest leg of RGB LED goes to 5V pin.
- [RGB basic](#) [RGB favorite color](#) RGB code




# Stepper Motor

- Stepper motor rotates in steps, Torque
- Basis for many machines
- 28BYJ-48 stepper motor
- ULN2003 Driver Board
- Lesson 31
- Applications: XY plotter

[nema 17 motor with a4988 driver](#)



# High Power Electronics

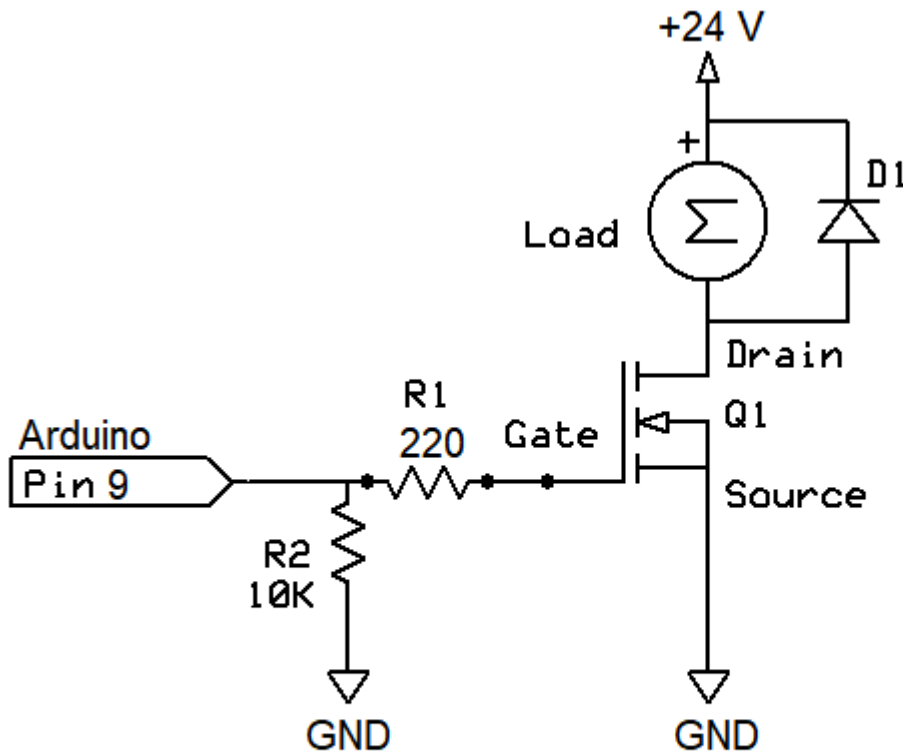

- R1 limits gate current
- R2 is pull-down in case pin hi-impedance
- D1 is flyback protection (Schottky)
- Q1 is N-channel logic-level MOSFET

# Assignment 6

- A. Add an output device to a microcontroller board and program it to do something
- B. Combine an input and output device together and collect data for an activity connected to you. Analyze that data and make sense of it. E.g. – finding the thermal comfort in your room.



# Examples

- Developing a heat stress index [Formula](#) (If hot then LED is RED, If cool LED is BLUE.)
- Dustbin – full vs. half vs. empty, LED is RED, YELLOW, GREEN.
- Display the sensor value on the LCD display.

# Summary

- Output devices
- Examples: LCD display, RGB LED, Stepper Motor
- Fab Academy [webpage](#) [video](#)
- Think of applications as a designer
- Explore other input and output devices